

VDSL

Driver Side Protection

Solution Products



2038-110-SM-RPLF



TISP4P015L1NR-S



CD143A-SR70

Design Kit



PN-DESIGNKIT-36

Objective

VDSL provides fast data transmission, usually over a twisted pair of copper wires. This solution protects these ports against surge and power contact threats.

Solution

1 GDT: 2038-110-SM-RPLF
1 Thyristor: TISP4P015L1NR-S
1 Diode Bridge: CD143A-SR70

Compliance

ITU-T Basic and Enhanced
GR-1089-CORE

Alternate Recommendations


Other PortNote® Solutions:

- VDSL: Line Side Protection

Variations of this circuit are available depending on specific design constraints; contact your local Bourns technical representative for more information.

Benefit

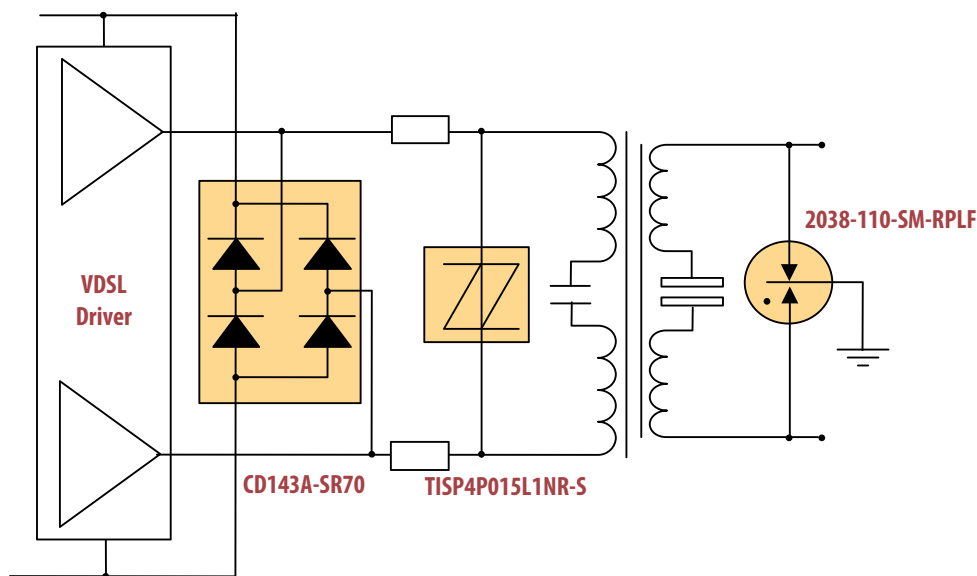This solution provides protection on the driver side without impairing the VDSL 17 MHz signal.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.

BOURNS®

Americas: Tel +1-951 781-5500
Fax +1-951 781-5700

Europe: Tel +41-(0)41 768 55 55
Fax +41-(0)41 768 55 10

Asia-Pacific: Tel +886-2 256 241 17
Fax +886-2 256 241 16

Bourns® PortNote® solutions provide protection recommendations for typical port threats.

For more information, go to:

www.bourns.com

or email: protection@bourns.com