



Introduction

This application note discusses how to select optimal power devices and control circuitry for alternating plasma display panel applications, concentrating on power circuits used to sustain plasma discharge on the panel.

Plasma Display Panels (PDP) are emerging as the leading candidate for large area wall-hanging color TVs and HDTVs [1]. Its large screen, wide viewing angle, and thinness have given it the edge over conventional displays. Scan, Energy Recovery (ERC) and Sustain (discharge) circuits are important blocks that fulfill important energy saving requirements.

Contents

1	PDP Module structure	4
2	PDP basic	5
2.1	PDP cell structure	5
2.2	Panel memory characteristic	6
2.3	PDP driving sequence	8
3	PDP Sustain circuit	9
3.1	Sustain circuit operations	12
3.1.1	Positive pulse of V_{yx}	12
3.1.2	Positive discharge and clamping phase	13
3.1.3	V_{yx} back to zero	14
3.1.4	Clamping to ground	14
3.2	Symmetrical Y - X phase	15
3.3	Reset phase	16
4	PDP Power Devices characteristics	17
4.1	Power devices from ST	17
4.1.1	Measurement set-up	18
4.1.2	Energy recovery section	19
4.1.3	Discharge section	20
4.1.4	Path section	20
4.1.5	Set - reset section	21
4.2	Driving section	22
4.3	Gate driver devices	22
4.3.1	Totem pole	23
4.4	Input buffer section	24
5	Bill of material and schematics	25
6	Conclusions	28
7	References	28
8	Revision history	29


List of figures

Figure 1.	PDP module structure.	4
Figure 2.	Cell structure.	5
Figure 3.	Memory effect - no charges	6
Figure 4.	Memory effect - address phase	6
Figure 5.	Memory effect - Wall charges deposit	6
Figure 6.	Memory effect - discharge	7
Figure 7.	Memory effect - wall charges deposit	7
Figure 8.	Memory effect - discharge with reverse polarity	7
Figure 9.	Subfield structure	8
Figure 10.	Subfield structure – expression of gray level	9
Figure 11.	Sustain circuit	10
Figure 12.	Circuit scheme	11
Figure 13.	Circuit scheme – positive pulse of V_{yx}	12
Figure 14.	Equivalent circuit.	12
Figure 15.	Circuit scheme – positive discharge and clamping	13
Figure 16.	Circuit scheme – V_{yx} back to zero	14
Figure 17.	Circuit scheme – clamping to ground	15
Figure 18.	Circuit scheme – negative pulse of V_{yx}	15
Figure 19.	Circuit scheme – negative discharge and clamping	15
Figure 20.	Circuit scheme – V_{yx} back to zero	16
Figure 21.	Circuit scheme – clamping to ground	16
Figure 22.	Circuit scheme – set and reset	17
Figure 23.	Inductor current.	19
Figure 24.	Gate driver topology with L6385	23
Figure 25.	Gate driver topology – L6388	23
Figure 26.	STS01DTP06 Totem pole.	24
Figure 27.	Board schematic 1	26
Figure 28.	Board schematic 2	27

1 PDP Module structure

Power supply, address buffer, logic and scan buffer boards are the fundamental blocks of a PDP. In particular, the energy recovery and sustain function are performed by the Y and X drive boards. Power MOSFETs, IGBTs, Diodes and Drivers are key products for ERC and sustain both in X and in Y drive boards. These products are also used for the path, set-reset function in the Y drive board only. Path switches are mandatory to isolate ERC and Sustain switches from the negative voltage applied to the display during the scan phase, while, set and reset switches determine identical initial condition of the plasma cells before each address cycle.

Figure 1. PDP module structure

 

ST's extensive portfolio covers the whole solution for an energy recovery circuit (ERC), sustain circuit, path circuit, and set-reset circuit, both from a power device and IC driver perspective.

The ST solution takes into account all fundamental requirements like cost, component count, reliability and power consumption.

Reduced power losses and higher switching frequency are the main benefits of ST's advanced technology.


2 PDP basic

Basic knowledge on Plasma Display Panel encompasses manufacturing issues in cell structure, physics principle in the memory effect, and display algorithms needed to create a range of colors.

2.1 PDP cell structure

Figure 2 shows the structure of a plasma display glass panel, [2].

Figure 2. Cell structure

 

An AC PDP display is composed of front and rear glass substrates sandwiched together and then sealed. The air is vacuumed out and a mixture of inert gases (Ne and Xe) is injected between the glass substrates. The separation between the two opposing substrates is about 100µm and the space between them is filled with a gas mixture of Ne and Xe. The front glass substrate has a first electrode (X electrode) and a second electrode (Y electrode) which operate as sustain electrodes. The X and Y electrodes are coated with bus electrodes, dielectric layer, and MgO layer in sequence. The MgO protects the dielectric from plasma damage and also aids the plasma in sustaining a discharge through secondary electron emission from its surface. In addition, equivalent capacitor exists between the X and Y electrodes. On the surface of the rear glass substrate, as opposed to the front glass substrate, a third electrode operating as an address electrode (A electrode) is formed to be orthogonal to the X and Y electrodes. Electrically, the entire assembly can now be considered as a three-electrode capacitor. A cross point is formed where the X, Y and A electrodes meet. Three adjacent red, blue and green cross points form a color picture element (pixel) of the panel. In operation, an AC voltage sufficiently high will ionize the gas to create the plasma. Then, the ultraviolet light from the plasma excites the phosphor to create the color image.


Each pixel can be independently controlled and can assume different color gradations. The number of pixels available determines the resolution of the glass panel vertically and horizontally.

2.2 Panel memory characteristic

The AC PDPs provide inherent memory characteristics [3], [4], as explained in the following figures.


In general, the AC sustain square pulse voltage (V_{xy}), whose voltage V_s is smaller than the gas breakdown voltage V_{bd} , cannot initiate a discharge, as shown in [Figure 3](#).

Figure 3. Memory effect - no charges

 


If data pulses V_d are applied to the address electrodes, while scan pulses $-V_y$ are sequentially applied to each Y electrode, the voltage ($V_d + V_y$) is higher than V_{bd} and a weak discharge ignites, as shown in [Figure 4](#).

Figure 4. Memory effect - address phase

 


Charges, called wall charges (or wall voltage V_w), deposit on the dielectric layer and reduce the effective voltage across the gap. Then, the discharge ceases after a short time, as shown in [Figure 5](#).

Figure 5. Memory effect - Wall charges deposit

 


When the polarity of the sustain pulse is reversed, the potential difference across the gap becomes larger than V_{bd} by an amount determined by the wall charges, and a new large discharge of different polarity occurs, as shown in [Figure 6](#).

Figure 6. Memory effect - discharge

 


The build-up of wall charges again terminates the discharge, as shown in [Figure 7](#).

Figure 7. Memory effect - wall charges deposit

 

The next discharge starts as the polarity of the sustain pulse is reversed, as shown in [Figure 8](#).

Figure 8. Memory effect - discharge with reverse polarity

 

Once the discharge is initiated, it continues as long as the sustain pulse is applied. Due to this memory characteristic of AC PDPs, lower sustain voltage ($< V_{bd}$) pulses can maintain the ac PDPs to light.

In other words, the process of panel image displaying depends on a former process of panel addressing. In fact, during the address phase a small amount of charges (wall charges) deposit on the selected electrodes without any visible light emission. This reduces the

threshold voltage for discharge, and consequently, during sustain phase only selected cells ignite and emit light.


2.3 PDP driving sequence

The most common method of displaying one picture field is using the Address Display-Separation method (ASD).

All X electrodes are bused together and connected to a sustain driver, while the Y electrodes are connected to sustain driver through several scan ICs. One TV field is divided into 10 subfields (SFs) in a 10-bit codification case, and each consists of a reset period, an address period, and a display period (*Figure 9*).

On every subfield, each cell is addressed, sustained and erased.


Figure 9. Subfield structure

 

During the reset period a slow ramping positive voltage up to 400 V followed by slow ramping negative voltage down to -150 V is applied across the X and Y electrodes to put out ionization and to set an identical initial condition for all the panel cells. In the address period, the Y electrodes receive scan pulses, along with data pulses on the address electrodes, in order to control wall charges in appropriate cells according to the image to be displayed. Note that reset period and address period have the same duration in each subfield, only the number of sustain pulses varies among different subfields.

During sustain period, selected cells are sustained in order to display the whole image on the panel. Gray scales are expressed by using the binary-coded light-emission-period method. The display periods are filled with trains of constant width and constant period pulses, and their lengths are arranged according to the binary sequence, 1: 2: 4: 8: 16: 32: 64: 128: 256: 512. Therefore, gray levels of 2^{10} for each color (R, G, and B) can be expressed with an 10-bit sequence. This means that each color element has 1024 color possible graduations and each pixel has $1024 \times 1024 \times 1024 = 1$ billion colors. *Figure 10* shows a simplified 8-bit system with 8 subfields. The subfields are weighted according to their binary values and a typical TV field is 1/50 of a second.

Figure 10. Subfield structure – expression of gray level

 

3 PDP Sustain circuit

In a Plasma Display Panel, frequent discharges are made to occur by alternately charging each side of the panel to a critical voltage, allowing images to be displayed. This alternating voltage is called the sustain voltage, and the sustain circuit (or sustainer) is needed to provide it to the display [5].

If a pixel has been driven "ON" during address period, the sustainer maintains the "ON" state of that pixel by repeatedly discharging that pixel cell during the whole sustain period. If a pixel has been driven "OFF" by an address driver, the voltage across the cell is never high enough to cause a discharge, and the cell remains "OFF" during the sustain period.

The sustain circuit must drive all panel pixels at once. This means that the capacitance as seen by the sustainer is typically very large. In a 42-inch panel with 852x480 pixels, the total capacitance of all the pixel cells, C_p , could be as much as 80 nF.

The key parameters in the sustainer study are:

- C_p - Panel equivalent capacitance
- V_s - Sustain Voltage
- f - Sustainer Switching frequency
- f_{av} - average sustainer switching frequency


Conventional sustain circuit (half bridge topology) drives the panel directly, and thus $1/2 C_p V_s^2 f_{av}$ is dissipated in the sustainer when the panel is subsequently discharged to ground.

In a complete sustain cycle, each side of the panel is charged to V_s and subsequently discharged to ground. Therefore, a total of $2 C_p V_s^2 f_{av}$ power is dissipated in a complete sustain cycle.

Conventional sustain circuit (half bridge topology) drives the panel directly, and thus $1/2 C_P V_S^2 f_{av}$ is dissipated in the sustainer when the panel is subsequently discharged to ground.

In a complete sustain cycle, each side of the panel is charged to V_S and subsequently discharged to ground. Therefore, a total of $2 C_P V_S^2 f_{av}$ is dissipated in a complete sustain cycle.

Figure 11. Sustain circuit

 

The power dissipation in the sustainer is then $2 C_P V_S^2 f_{av}$, where f_{av} is the average sustain cycle frequency.

For $C_P = 80 \text{ nF}$, $V_S = 200 \text{ V}$, and $f_{av} = 100 \text{ kHz}$, the power dissipation in the sustainer, resulting from driving the capacitance of the panel, could be as high as 640 W.


If an inductor is placed in series with the panel, then C_P can be charged and discharged through the inductor. This would ideally result in zero power dissipation since the inductor would store all of the energy otherwise lost in the output resistance of the sustainer and transfer it to or from C_P . However, switching devices are needed to control the flow of energy to and from the inductor, as C_P is charged and discharged, respectively, and this leads to power losses.

The "ON" resistance, output capacitance, and switching transition time are characteristics of these switching devices that can result in significant energy loss. The amount of energy that is actually lost due to these characteristics, and hence the efficiency, is determined largely by how well the circuit is designed to minimize these losses. In addition to charging and discharging C_P , the sustainer must also supply the large gas discharge current for the plasma panel. This current, I , is proportional to the number of pixels that are "ON" in the same TV frame. The resulting instantaneous power dissipation is $I^2 R$, where R is the output resistance of the sustainer. Thus, the power dissipation due to the discharge current is proportional to I^2 , or the square of the number of pixels that are simultaneously "ON".

There are two ways to minimize this dissipation. The first is to reduce the output resistance of the sustainer by using very low resistance output drivers, and the second is to minimize the number of pixels that are "ON" at any time.

The switching power losses due to the panel capacitance during sustain period in AC PDP driving system can be minimized using a specific energy recovery circuit. The most common sustain/energy recovery circuit topology refers to Weber topology ([Figure 12](#)).

Figure 12. Circuit scheme

 

Weber topology provides a new sustainer circuit that recovers the energy otherwise lost in charging and discharging the panel capacitance, C_p . The efficiency with which the sustainer recovers this energy is defined as the "recovery" efficiency. In particular, when C_p is charged to V_s and then discharged to zero, the energy that flows into and out of C_p is $E = C_p V_s^2$.

The recovery efficiency is defined by:

Equation 1

$$Eff = 100 \cdot \frac{C_p V_s^2 - E_{LOST}}{C_p V_s^2} = 100 \cdot \left(1 - \frac{E_{LOST}}{C_p V_s^2} \right)$$

where E_{LOST} is the energy lost in charging and discharging C_p in the sustain circuit without energy recovery.

It is worth noting that the recovery efficiency is not the same as the conventional power efficiency defined in terms of the power delivered to a load, since no power is delivered to the capacitor C_p . It is simply charged and then discharged. The recovery efficiency is a measure of the energy loss in the sustainer, and could reach a value higher than 90%.

Summarizing, the panel's pixels are connected in parallel and can be represented as an equivalent panel capacitor C_p . A proper switching sequence, together with the energy recovery circuit, allows this circuit to produce an AC voltage required to illuminate, recover residual energy and reset the cells of the panel.

Referring to the schematic in [Figure 12](#), Power devices in the Sustain circuit topology can be grouped into four circuit sub-functions:

1. Energy recovery circuit (ERC) which consists of T1, T2, T11, T12, D1, D2, D3, D4, D5, D6, D7, D8
2. Sustain circuit (discharge circuit or sustainer) which consists of T3, T4, T9, T10
3. Path circuit which consists of T5, T6
4. Set and Reset circuit which consists of T7, T8

3.1 Sustain circuit operations


Sustain circuit operations describe the way to generate a square waveform on the panel capacitor. This section describes how to charge and discharge the panel capacitor in order to perform the sustain phase.

3.1.1 Positive pulse of V_{yx}

After the reset period, we can suppose that all cells on the panel have been already addressed during the address period. This means that the cells to be displayed have accumulated enough wall charge to be ignited, due to cell memory effect. We can assume also that CS1 and CS2 have already their steady state voltage value, this means they have initial voltage of $V_s/2$ from previous sustain cycles.


In order to produce a positive voltage across the panel (V_{yx} positive), T1, T5, T6 and T10 are turned ON and D1 is forward biased. CS1 charges and raises the voltage across the panel capacitor C_p in a resonant way. This step is a part of the energy recovery phase since it recovers the energy stored in the capacitor CS1 from previous sustain cycles back to the panel.

Figure 13. Circuit scheme – positive pulse of V_{yx}

 

The equivalent circuit during the LC resonant period of the energy recovery circuit is:

Figure 14. Equivalent circuit

 

In [Figure 14](#), R represents the parasitic resistance including on-resistances of switches and V_{ON} represents the diode forward drop. Based on this figure, the panel voltage V_{yx} can be obtained as follows:

Equation 2

$$V_{yx} = \left(\frac{V_s}{2} - V_{ON} \right) \left[1 - e^{-\frac{t}{\tau}} \left(\cos \alpha t + \frac{R}{\omega L} \sin \alpha t \right) \right]$$

Where $\tau = \left(\frac{\omega R}{L}\right)$ and $\omega = \sqrt{\left(\frac{1}{LCp}\right) - \left(\frac{R}{2L}\right)^2}$

If $(2L/R)^2$ and $(\omega R/L)$ can be ignored, the equation ([Equation 2](#)) can be simply re-written as:

Equation 3

$$V_{yx} = \left(\frac{V_s}{2} - V_{ON}\right) \left[1 - e^{-\frac{t}{\tau}} \cos \omega t\right]$$

Where $\omega = \sqrt{\frac{1}{LCp}}$

If $\omega = \Pi$ then the peak value is:

Equation 4


$$V_{yx, pk} = \left(\frac{V_s}{2} - V_{ON}\right) \left[1 - e^{-\frac{\pi R}{2} \sqrt{\frac{C_p}{L}}}\right]$$

[Equation 4](#) states that an increase of the parasitic resistance causes the recovery efficiency to be degraded. Naturally, it is necessary to reduce the parasitic resistance by designing the circuit board optimally as well as choosing switching devices with small on-resistance and low on-drop voltage to minimize the hard-switching stress and improve the recovery performance. On the other hand, reduction of the inductor value produces similar results and, thus, using a too small value of L is not desirable with respect to driving loss.

3.1.2 Positive discharge and clamping phase

[Figure 15](#) shows both panel discharge and the clamping current paths. In the first phase the ionized gas could be represented as a non linear resistor and the peak current during this period is higher than that during energy recovery. The worst condition is represented when all cells in the panel must be ignited (full white screen condition), and in this case the discharge current could be higher than 120 A for a standard definition (SD) 42-inch PDP set. Further increase in the current value is expected in HD PDP as the number of pixels increases.

Figure 15. Circuit scheme – positive discharge and clamping

 

The discharge current has also a sinusoidal profile, and is conducted by T3, T6, T5, Cp, and T10. Once the panel is charged to V_s and visible light is emitted, current stops flowing and the gas inside the glass stops ionizing. (Note that the use of IGBTs in the discharge section requires extra care; indeed power devices requires freewheeling diodes to carry reverse current due to the tank circuit formed between the panel capacitor Cp, L1 and the bus capacitance).

At this time D1 is reverse biased and its reverse current charges the inductance L1. The energy stored in the inductance is removed through the clamping current, and the clamping current path is carried out by T3, D3, and D2. In this phase the reverse current of D1 is a key parameter in power loss reduction. In fact, a lower clamping current means lower conduction losses in T3, D2 and D3. Depending on the topology used, and in particular the clamping diode's position, the time spent to evacuate the energy stored in the inductance can vary significantly.


3.1.3 V_{yx} back to zero

The next phase consists of bringing back to zero the panel capacitor voltage and reverse the polarity of the voltage across Y-X electrodes.

In order to efficiently decrease the voltage on the panel capacitor, the energy stored in Cp could be recovered back in the recovery capacitor CS1. This can be done by turning ON T2, T6, T5, and T10.


The current path is shown in [Figure 16](#). This current stops flowing when the voltage across the panel capacitance V_{yx} and CS1 reach the same value ($V_s/2$). The profile of this current is half sinusoidal and its direction is from the panel Cp back to CS1.

Figure 16. Circuit scheme – V_{yx} back to zero

  

3.1.4 Clamping to ground

In order to bring completely to zero the panel capacitance, T10, T5, T6, and T4 are turned ON, creating a current path across the panel through the equivalent resistances of power devices and parasitic elements of the circuit.


Figure 17. Circuit scheme – clamping to ground

3.2 Symmetrical Y - X phase


A similar switching sequence is applied in order to reverse the polarity across Y-X electrodes (X electrode more positive than Y electrode)

In particular, this can be briefly described as:

- Energy recovery, path and discharge switches, T12, T5, T6, and T4 are turned ON, and the current flows from CS2 to Cp.

 
Figure 18. Circuit scheme – negative pulse of V_{yx} 

- Discharge and Clamp phases: T9, T4, T5, T6 are turned ON and the current flows from Vs to Cp and through T9, L7, D7, D8.

 Figure 19. Circuit scheme – negative discharge and clamping


- c) Energy Recovery phase: T4, T5, T6, and T11 are turned ON, and the current flows from Cp to CS2.

Figure 20. Circuit scheme – V_{yx} back to zero

 

- d) Zero voltage Clamp, T4, T5, T6, T10 are turned ON.

Figure 21. Circuit scheme – clamping to ground

 


It can be noted that during sustain phase, path switches T5 and T6 are always turned ON, and they see both energy recovery current and discharge current which explains the need for low voltage drop devices.

3.3 Reset phase

At the end of each subfield, the cells are reset applying a positive ramp voltage followed by a negative one.

During positive reset, T10, T5, T7 are turned ON. During negative reset T10 and T8 are turned ON.

Figure 22. Circuit scheme – set and reset

 

4 PDP Power Devices characteristics

A clear idea of circuit operation will help us to highlight the main features of the devices involved. In particular the analysis can be split in power devices analysis and driving devices analysis, in order to address specific characteristics of each device.

4.1 Power devices from ST

Power devices in PDP have common characteristics that range from high peak current capability and low forward voltage drop to fast turn-ON capability. The current both in the Energy Recovery Circuit (ERC) and in the Discharge Circuit (DC) follows a half sinusoidal pattern. ERC and DC could be simply classified as soft switching converters. In fact, the circuit can be considered as a series resonant LCR circuit, so the current at turn-ON is zero (zero current switching) and the voltage at turn-OFF is zero (zero voltage switching).

Since a MOSFET has an intrinsic body diode across it, a MOSFET does not require an anti-parallel diode when selected as power devices on the discharge circuit, while an IGBT needs a specific freewheeling diode. For ER circuit, the Power Switch does not require an anti-parallel diode since reverse current is blocked by the diodes in series with the devices (D1, D3, D5 and D7), thus MOSFET or IGBT can be used as power devices on the ER circuit.

Diodes D2, D4, D6 and D8 provide additional protection clamping the voltage on the inductors avoiding damage to devices on the ER circuit.

Path circuit has to carry both ER and Discharge currents, thus it is required to have very low voltage drop. It can be noted that during ER and Discharge cycles, the pass circuit remains on. The Path circuit switches on and off only during reset period which happens at the end of each subfield, which means that the maximum frequency is in the range of 1 kHz. The Path circuit is a bidirectional circuit, so a MOSFET, that can carry current in both directions, could be used for this circuit.

ST has a broad range of products covering the power section ranging from MOSFET and IGBT to dedicated Diodes.

4.1.1 Measurement set-up

Power losses and thermal analysis measurements were performed based on an average switching frequency. In fact, switching performances have to be related to the maximum frequency in the system, usually 250 kHz, whereas power losses and thermal management have to be related to an average frequency. The Average Switching frequency takes into account the fact that during a picture time, the power devices do not switch at the maximum frequency for the whole time, but only during the sustain phases. The sustain duration, and consequently the number of sustain pulses, increases starting from subfield 1 to subfield 10. Average frequency can be calculated starting from sustain duty ratio.

Table 1. 10 subfield / single scan

Scan speed	VGA 480	XGA 768	HD 1080
3 μ sec	-	-	-
2.5 μ sec	0.130	-	-
2 μ sec	0.274	-	-
1.5 μ sec	0.418	0.159	-
1 μ sec	0.562	0.389	0.202

Table 2. 10 subfield / dual scan

Scan speed	VGA 480	XGA 768	HD 1080
3 μ sec	0.418	0.158	-
2.5 μ sec	0.490	0.274	0.040
2 μ sec	0.562	0.389	0.202
1.5 μ sec	0.634	0.504	0.364
1 μ sec	0.706	0.620	0.526

Note: $\text{Sustain duty} = \text{picture time} - \text{reset period} \times \text{SF} - N \times \text{SF} \times \text{scan speed} [\mu\text{s} / \text{line}]$

Picture time = 16.67 ms

Reset period = 250 μ sec

SF = number of sustain pulses

N = number of lines

The sustain duty ratio is carried out for a 10 subfield case in both single scan and dual scan operations, varying the scan speed duration (time needed to scan a single line in the display), for VGA (480 lines), XGA (768 lines) and HD (1080 lines).

According to the following formula,

$$f_{av} = f_{switching} \times \text{SustainDuty}$$

For a VGA display $\rightarrow \text{SustainDuty} = 0.27 \div 0.56 \rightarrow f_{av} = 68 \div 140 \text{ kHz}$

This means that power devices in ERC and discharge circuit need to be designed for an average frequency of 140 kHz (maximum) in terms of power losses and thermal management. Clearly peak current and peak voltage rating do not change when we perform this averaged analysis.

Typical voltage requirements for a PDP are:


- Sustain voltage $V_s = 200\text{ V}$
- Set voltage $V_{set} = 400\text{ V}$
- Reset voltage $V_{reset} = -150\text{ V}$

4.1.2 Energy recovery section

For Energy recovery circuit, the maximum voltage stress is $V_s/2 \approx 100\text{ V}$, and the current stress depends on the device. The clamping diodes have to withstand a current lower than 10 A, whilst the ERC switches and the ERC diodes have to be able to handle a resonant half-sinusoidal current up to 100 A peak.

The typical current waveform in the Energy recovery circuit is shown in [Figure 23](#). The key parameters of the DERC diode for the energy recovery circuit have been optimized in order to decrease power losses.

Figure 23. Inductor current

 

For ER circuit new devices with low voltage drop and very fast turn ON have been developed.

- Energy recovery diodes STTH60P03, STTH40P03

Energy recovery diodes (D1, D3, D5, and D7) have been tailored on this application optimizing key parameters to reduce power losses [6], [7]. They have the ability to handle large repetitive peak current (I_{rp}), in conjunction with a lower reverse current (I_{RM}) and peak forward voltage (V_{FP}).

Table 3. STTH60P03 Features

Symbol	Parameter	Test conditions		Min.	Typ	Max.	Unit
I_{RM}	Reverse recovery current	$T_j = 100^\circ\text{C}$	$I_F = 60\text{ A}$ $V_R = 100\text{ V}$ $di_F/dt = 200\text{ A}/\mu\text{s}$		6	7.5	A
S_{factor}	Softness factor				0.5		
V_{FP}	Peak forward voltage	$T_j = 25^\circ\text{C}$	$I_F = 60\text{ A}$ $di_F/dt = 400\text{ A}/\mu\text{s}$		2.5	3.5	V

- Clamping diodes STTH2003, STTH1003

Diodes D2, D4, D6, and D8 provide additional protection to clamp the voltage on the inductors [8], [9]. Overvoltage is due to ER diodes reverse current that store energy in the inductors. The fact that reverse current I_{RM} of ERC diodes stores energy in the inductors (and can cause overvoltage if we do not use clamping diodes D2, D4, D6, and D8), demonstrates that the I_{RM} in ERC diodes is a key parameter to take into account. In fact, I_{RM} causes power losses both in Clamping diodes and Discharge switches.

Table 4. Clamping diodes features

P/N	I_F [A]	V_{RRM} [V]	T_{rr} [ns]	T_j [°C]	V_F [V]	Package
STTH1003	10	300	13	175	0.9	DPAK, TO-220FP, D ² PAK
STTH2003	2x10	300	35	175	1	DPAK, TO-220FP, D ² PAK, TO220

- Energy recovery MOSFET ST75N20

T1, T2, T11, and T12 are the power switches used in the Energy recovery circuit. Due to the reactive nature of the load, the voltage across the power switch falls rapidly followed by a rapid rise in the current. This explains why a fast turn-ON is needed, and low conduction losses (low drop) can be achieved only reducing the $R_{DS(on)}$. The STW75N20 Power MOSFET in proprietary STripFET™ technology, thanks to its low $R_{DS(on)}$ and low gate charge is perfectly tailored for the application [9].

Table 5. ERC MOSFET features

P/N	V_{DSS} [V]	$R_{DS(on)}$ [Ω]	$I_D/I_{D(MAX)}$ [A]	P [W]	Package
ST75N20	200	0.028	75/300	300	TO-247, TO-220, D ² PAK

4.1.3 Discharge section

When the panel discharges, a sinusoidal shaped current will go through the discharge switches. The current could reach a peak value higher than 120 A in worst condition (full white screen), thus low $R_{DS(on)}$ and fast turn-ON are required.

Maximum voltage stress for discharge circuit is $V_s = 200$ V

- Discharge MOSFET STW52NK25Z

The STW52NK25Z Power MOSFET in property superMESH™ technology, and due to its low $R_{DS(on)}$ and low gate charge is perfectly tailored on the application [10].

Table 6. Sustain MOSFET features

P/N	V_{DSS} [V]	$R_{DS(on)}$ [Ω]	$I_D/I_{D(MAX)}$ [A]	P [W]	Package	P/N
STW52NK25Z	250	0.033	52/208	300	TO-247	STW52NK25Z
STW54NK30Z	300	0.060	54/200	300	TO-247	STW54NK30Z

4.1.4 Path section

For Path circuit, MOSFET is the preferred device since this circuit is required to conduct current in both directions. The switching frequency is low, and the RMS current through this

circuit is very large since it has to conduct both ER and discharge currents. Both STripFET™ and superMESH™ Power MOSFETs technologies from ST are ideal for this application since they allow the die to have very high current density and therefore reduce the number of paralleled devices required to maintain very low voltage drop [9], [10], [11], [12].

For path switch in T6 position, the maximum voltage stress is $(V_s + V_{set}) / 2 \approx 300$ V, while for path switch in T5 position, the maximum voltage stress is $(V_{set} + |V_{reset}|) / 2 \approx 275$ V.

Table 7. Path MOSFET features

P/N	V _{DSS} [V]	R _{DS(on)} [Ω]	I _D /I _{DMAX} [A]	P [W]	Package
ST60NK30ZD1	300	0.045	60/240	450	Die or MAX247
STW52NK25Z	250	0.033	52/208	300	TO-247
ST75N20	200	0.028	75/300	300	TO-247, TO-220, D ² PAK
ST40N20	200	0.045	40/160	160	TO-247 TO-220 D ² PAK TO220FP

4.1.5 Set - reset section

The set and reset circuit applies asymmetrical AC voltage across the panel in order to evacuate any remaining surface charge from the cells. This is usually done at the end of each subfield (or the beginning of the next subfield), and the power devices on this circuit operate in the linear mode. This means that the voltage drop is very large but the current through the device is relatively low. Due to the requirement of asymmetrical Set and Reset voltages, Power switches in the set and reset circuits have to block up to 600 V. Typical voltage value for Set function is 400 V and for Reset function is -150 V. This means that the maximum voltage stress for Set circuit T9 is $(V_s + V_{set}) = 600$ V while the maximum voltage stress for reset circuit T10 is $V_{set} + |V_{reset}| = 550$ V.

ST offers two families of products for this section both appreciable for their ruggedness for linear applications.

Example device is STGP10NB60S in the IGBT Planar technology [13]:

Table 8. Set – reset IGBT features

P/N	V _{CES} [V]	V _{CE(SAT)} [Ω]	I _C [A]	Package
STGP10NB60S	600	1.7	10	D ² PAK

Further examples of devices are superMESHTM devices as follows [14], [15].

Table 9. Set-reset MOSFET features

P/N	V _{DSS} [V]	R _{DS(on)} [Ω]	I _D /I _{DMAX} [A]	P [W]	Package
ST9NK70Z	700	1	7.5/30	115 W	TO-220 D ² PAK TO220FP
ST14NK60Z	600	0.5	13.5/54	160 W	TO-220 D ² PAK TO220FP

4.2 Driving section

Driving section devices range from gate driver devices to input buffer ones. Gate driver function is carried out by a gate driver IC and a push pull amplifier.

Driving section can be split in:

- Gate driver section: L6385 or L6388
- Push pull section: STS01DTP06
- Input buffer section 74VHCT541



4.3 Gate driver devices

ST offers the widest series among the High Voltage Half-Bridge Gate Drivers (the L638x series), manufactured with BCD"OFF-LINE" technology. They are able to work in applications with voltages to 600 V. In the L638x series the two selected drivers are the L6388 [16.] and the L6385 [17.], which can drive two Power MOSFETs or IGBTs, one high-side and one low-side, in a Half-Bridge or different topology. L6388 is especially effective in applications where logic input must be compatible with 3.3 V Logic. Another key feature of the L6388 is that it provides effective anti-shoot-through circuitry which prevents two Power MOSFETs or IGBTs from being turned ON at the same time. This is achieved by introducing a 200 ns time interval, a "dead time" between the moment one of the components is turned OFF and the other is turned ON. L6385 is able to drive asymmetrical half bridge, but its logic input is not compatible with 3.3V Logic.

The main features of these HV Gate Drivers are:

- dV/dt immunity ± 50 V/nsec in full temperature range
- Driver current capability:
 - 400 mA source
 - 650 mA sink
- Switching time 50/30 nsec rise/fall with 1 nF load
- Under voltage lock-out on lower and upper driving section
- Internal bootstrap diode
- Outputs in phase with inputs

Due to different characteristics, the topologies used in Energy Recovery Circuit and Sustain Circuit depend on the driver used as shown in [Figure 24](#) and [Figure 25](#).

  Figure 24. Gate driver topology with L6385**Figure 25. Gate driver topology – L6388**

Due to current value in bootstrap charge, the internal diode cannot be used, thus external diode SMBY01-400 [20.] must be used. Further details on L6585 and L6588 application can be found in [18.] and [19.].


4.3.1 Totem pole

In order to match inherent power devices characteristics, (as high gate charge) with drivers current capability, totem pole STS01DTP06 [21.] in a push pull configuration is used in the application. The STS01DTP06 is housed in the SMD dual island SO-8 package and allows an optimized electronic solutions, by improving circuit efficiency, saving space and reducing component count on the board.

The STS01DTP06 is a hybrid complementary NPN and PNP bipolar transistor manufactured using the latest low voltage planar technology. Extremely efficient performance is obtained by combining high pulse current, excellent gain and fast speed,

resulting in low losses in high frequency applications. The STS01DTP06 offers a 30 V NPN and PNP combination supporting a continuous collector current of 3 A and the minimum gain of the two transistors is 100 at 1 A collector current. The transistor elements are fully independent so that higher assembly flexibility is guaranteed. Concerning PDPs, this means that the turn-ON and the turn-OFF resistors could be different.

Figure 26. STS01DTP06 Totem pole

 

The STS01DTP06 main features are summarized in [Table 10](#):

Table 10. STS01DTP06 Features

Part number		V _{CE0} [V]	I _c [A]	P _{tot} [W]	h _{FE} min	VCE(sat)@ MAX [V]	I _c [A]	I _B [mA]
NPN	PNP							
STS01DTP06		30	3	1.6	100	0.7	2	100

4.4 Input buffer section

The 74VHCT541 is an advanced high-speed CMOS OCTAL BUS BUFFER (3-STATE) fabricated with sub-micron silicon gate and double-layer metal wiring C2MOS technology, available in TSSOP package [22].

In order to enhance PC board layout, the 74VHCT541 offers a pin-out having inputs and outputs on opposite sides of the package. The device is characterized by high speed and low power dissipation. Power down protection is provided on all inputs and 0 to 7 V can be accepted on inputs with no regard to the supply voltage. This device can be used to interface 5 V to 3 V. All inputs and outputs are equipped with protection circuits against static discharge, giving them 2KV ESD immunity and transient excess voltage.

5 Bill of material and schematics

[Table 11](#) gives the BOM and the schematics of the demo board.

Table 11. Bill of material

Item	Qty	Reference	Value & comment
1	5	C1,C4,C23,C26, C44	2.2 μ F 50 V
2	5	C2,C3,C24,C25,C45	100 nF 50 V
3	4	C5,C6, C20,C21	2.2 nF 400 V
4	4	C16,C17,C18,C19	3.3 μ F 250 V
5	1	C22	104 K 250 V
6	8	C27,C28,C29,C30,C48,C49,C50,C51	100 μ F 250 V
7	2	C35,C36	100 μ F 25 V
8	7	C37,C38,C39,C40,C41,C42,C43	100 pF 10 V
9	2	C46,C47	X1 Capacitor modeling the panel
10	4	D1,D7	SMBY01-400
11	2	D2,D10	STTH60P03SW
12	3	D3,D8	STTH2003CG
13	3	D14	DIODE Z.16 V
14	1	F1	5A 250 V Fuse
15	2	F2,F3	1A 125 V
16	1	J1	HEADER 9
17	2	J4,J13	Connector 2 PINS
18	1	J7	GND-STAR Connector
19	1	J18	HEADER 30
20	2	L5,L6	500 nH inductor
21	2	L12,L14	10 μ H inductor
22	2	R2,R19	2,2 Ω SMD resistor
23	8	R7,R8,R9,R10,R17,R18,R21,R22	3.9 Ω SMD resistor
24	2	R1, R20	36 Ω SMD resistor
25	5	R35,R36,R37,R38,R39	200 Ω SMD resistor
26	4	R50, R51	100 K Ω SMD resistor
27	6	R3, R4, R23, R24, R25	1 Ω SMD resistor
28	6	R26,R40,R41,R42,R43,R44	100 Ω SMD resistor
29	3	R27	10 K Ω SMD resistor
30	2	U1,U5	L 6385
31	4	U2,U3,U6,U7	STS01DTP06

Table 11. Bill of material (continued)

Item	Qty	Reference	Value & comment
32	1	U8	74VHCT541
33	4	U11,U12,U14, U16	STW52NK25Z
34	2	U13,U15	STW75N20
35	3	J15, J16, J17	Connector 17 pins

Figure 27. Board schematic 1


 


Figure 28. Board schematic 2

 

6 Conclusions

ST offers its customers a complete product portfolio covering the whole PDP. ST's system approach helps customers design effective energy recover (ERC) and Sustain circuits, improving their time-to-market. PDP power consumption is greatly reduced using ST's dedicated products.

7 References

1. "Plasma displays," IEEE Trans. Plasma Sci., vol. 19, pp. 1032-1047, Dec. 1991.
2. "Cell structure and driving method of a 25-in (64 cm) diagonal high-resolution color ac plasma display," in Proc. Symp. Society for Information Display, vol. 29, 1998, pp. 279-282.
3. "Charge spreading and its effect on AC plasma panel operating margins," IEEE Trans. Electron Devices, vol. ED-24, pp. 870-872, July 1997.
4. "Measurement of wall charges in a surface discharge AC-PDP," in Proc. Int. Display Workshops, 1997, pp. 527-530.
5. "Power efficient sustain drivers and address drivers for plasma panel," U.S. Patent 4 866 349, Sept. 1989 and U.S. Patent 5 081 400, Jan. 1992.
6. STTH60P03SW Datasheet
7. STTH40P03SW Datasheet
8. STTH2003CG Datasheet
9. STW75N20 Datasheet
10. STW52NK25Z Datasheet
11. STP40N20 Datasheet
12. ST60NK30ZD1 Datasheet
13. STGP10NB60S Datasheet
14. STP9NK70Z Datasheet
15. STB14NK60Z Datasheet
16. L 6388 Datasheet
17. L 6385 Datasheet
18. AN994 - L6384, L6385, L6386, L6387 Application guide
19. AN1299 - L6384, L6385, L6386, L6387: TIPS & TRICKS
20. SMBY01-400 Datasheet
21. STS01DTP06 Datasheet
22. 74VHCT541 Datasheet

8 Revision history

Table 12. Revision history

Date	Revision	Changes
02-May-2007	1	First issue

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2007 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com