

AN-1193 LM3477 Evaluation Board

1 Introduction

The LM3477 is a current mode, high-side N channel FET controller. It is most commonly used in buck configurations, as shown in Figure 1. All the power conducting components of the circuit are external to the LM3477, so a large variety of inputs, outputs, and loads can be accommodated by the LM3477.

The LM3477 evaluation board comes ready to operate at the following conditions:

$$4.5\text{ V} \leq V_{IN} \leq 15\text{ V}$$

$$V_{OUT} = 3.3\text{ V}$$

$$0\text{ A} \leq I_{OUT} \leq 1.6\text{ A}$$

The circuit and BOM for this application are given in Figure 1 and Table 1.

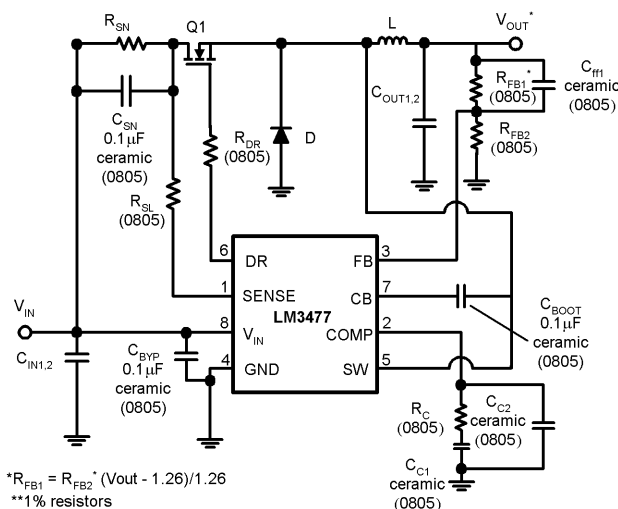


Figure 1. LM3477 Buck Converter


Table 1. Bill of Materials (BOM)

Component	Value	Part Number
C_{IN1}	120 μ F/20 V	594D127X0020R2
C_{IN2}	No connect	
C_{OUT1}	22 μ F/10 V	LMK432BJ226MM (Taiyo Yuden)
C_{OUT2}	22 μ F/10 V	LMK432BJ226MM (Taiyo Yuden)
L	10 μ H, 3.8A	DO3316P-103 (Coilcraft)
R_C	1.8 k Ω	CRCW08051821FRT1 (Vitraron)
C_{C1}	12 nF/50 V	VJ0805Y123KXAAT (Vitraron)
C_{C2}	No connect	
Q1	5A, 30 V	IRLMS2002 (IRF)
D	100 V, 3A	MBRS340T3 (Motorola)
R_{DR}	20 Ω	CRCW080520R0FRT1 (Vitraron)
R_{SL}	1 k Ω	CRCW08051001FRT1 (Vitraron)
R_{FB1}	16.2 k Ω	CRCW08051622FRT1 (Vitraron)
R_{FB2}	10.0 k Ω	CRCW08051002FRT1 (Vitraron)
C_{FF}	470 pF	VJ0805Y471KXAAT (Vitraron)
R_{SN}	0.03 Ω	WSL 2512 0.03 Ω $\pm$ 1% (Dale)

2 Performance

The following are some benchmark data taken from the circuit above on the LM3477 evaluation board. This evaluation board can also be used to evaluate a buck regulator circuit optimized for a different operating point, or to evaluate a trade-off between cost and some performance parameter. For example, the conversion efficiency may be increased by using a lower $R_{DS(ON)}$ MOSFET, ripple voltage may be lowered with lower ESR output capacitors, and the hysteretic threshold may be changed as a function of the R_{SN} and R_{SL} resistors.

The conversion efficiency can be increased by using a lower $R_{DS(ON)}$ MOSFET, however it drops as input voltage increases. The efficiency reduces because of increased diode conduction time and increased switching losses. Switching losses are due to the $V_{ds} \cdot I_d$ transition losses and to the gate charge losses, both of which can be lowered by using a FET with low gate capacitance. At low duty cycles, where most of the power loss in the FET is from the switching losses, trading off higher $R_{DS(ON)}$ for lower gate capacitance will increase efficiency.

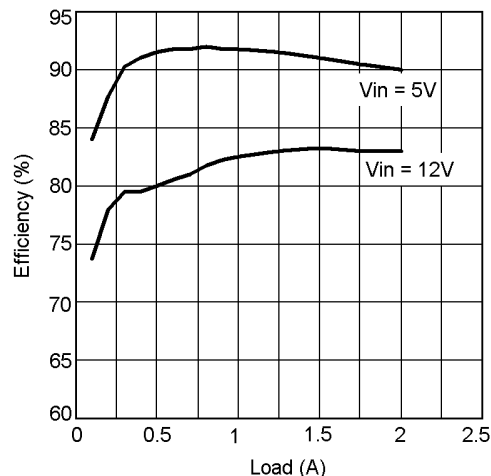
Figure 2. Efficiency vs Load $V_{OUT} = 3.3$ V


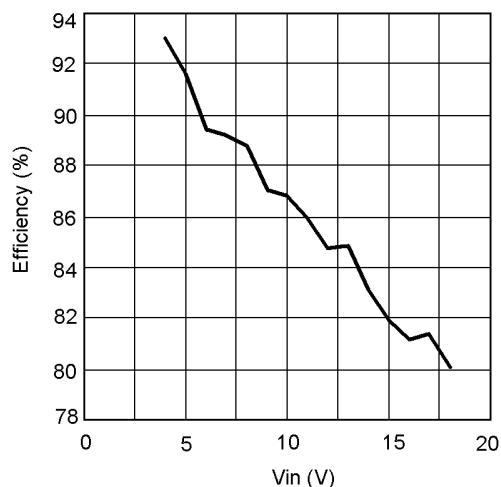


Figure 3. Efficiency vs V_{IN}
V_{OUT} = 3.3 V, I_{OUT} = 2 A

Figure 5 shows a bode plot of LM3477 open loop frequency response using the external components listed in Table 1.

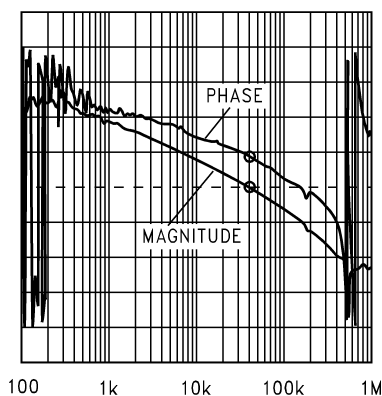

- (1) Magnitude = 20 dB/Decade Bandwidth = 39.8kHz
Phase = 45°/Decade Phase Margin = 41°

Figure 4. Open Loop Frequency Response
V_{IN} = 5 V, V_{OUT} = 3.3 V, I_{OUT} = 1.5 A

3 Hysteretic Mode

As the load current is decreased, the LM3477 will eventually enter a 'hysteretic' mode of operation. When the load current drops below the hysteretic mode threshold, the output voltage rises slightly. The over voltage protection (OVP) comparator senses this rise and causes the power MOSFET to shut off. As the load pulls current out of the output capacitor, the output voltage drops until it hits the low threshold of the OVP comparator and the part begins switching again. This behavior results in a lower frequency, higher peak-to-peak output voltage ripple than with the normal pulse width modulation scheme. The magnitude of the output voltage ripple is determined by the OVP threshold levels, which are referred to the feedback voltage and are typically 1.25 V to 1.31 V. For more information, see the *Electrical Characteristics* table in the *LM3477 High Efficiency High-Side N-Channel Controller for Switching Regulator Data Sheet* ([SNVS141](#)). In the case of a 3.3 V output, this translates to a regulated output voltage between 3.27 V and 3.43 V. The hysteretic mode threshold point is a function of R_{SN} and R_{SL}. Figure 5 shows the Hysteretic Threshold vs. V_{IN} for the LM3477 evaluation board with and without R_{SL}.

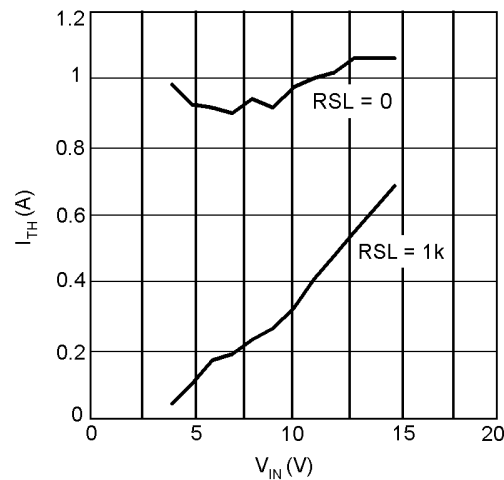


Figure 5. I_{TH} vs V_{IN}

4 Increasing Current Limit

The R_{SL} resistor offers flexibility in choosing the ramp of the slope compensation. Slope compensation affects the minimum inductance for stability (see the *Slope Compensation* section in the *LM3477 High Efficiency High-Side N-Channel Controller for Switching Regulator Data Sheet* ([SNVS141](#)), but also helps determine the current limit and hysteresis threshold. As an example, R_{SL} can be disconnected and replaced by a 0 ohm resistor so that no extra slope compensation is added to the current sense waveform to increase the current limit. A more conventional way to adjust the current limit is to change R_{SN} . R_{SL} is used here to change current limit for the sake of simplicity and to demonstrate the dependence of current limit to R_{SL} . By changing R_{SL} to 0 ohm, the following conditions may be met:


$$4.5\text{ V} \leq V_{IN} \leq 15\text{ V}$$

$$V_{OUT} = 3.3\text{ V}$$

$$0\text{ A} \leq I_{OUT} \leq 3\text{ A}$$

The current limit is a weak function of slope compensation and a strong function of the sense resistor. By decreasing R_{SL} , slope compensation is decreased, and as a result the current limit increases. The hysteretic mode threshold will also increase to about 1A (see [Figure 5](#)).

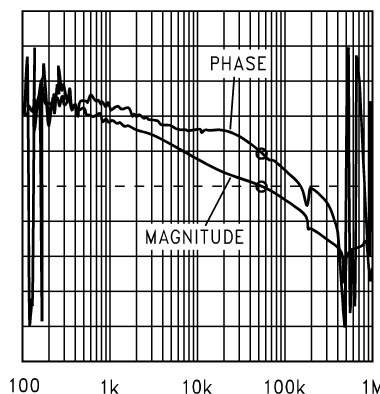Given below is a bode plot of LM3477 open loop frequency response using the modified ($R_{SL} = 0\Omega$) components to achieve higher output current capability.



(1) Magnitude = 20 dB/Decade
Phase = 45°/Decade

Bandwidth = 55.3kHz
Phase Margin = 42°

Figure 6. Open Loop Frequency Response

$V_{IN} = 5\text{ V}$, $V_{OUT} = 3.3\text{ V}$, $I_{OUT} = 3\text{ A}$

5 Layout Fundamentals

Good layout for DC-DC converters can be implemented by following a few simple design guidelines:

1. Place the power components (catch diode, inductor, and filter capacitors) close together. Make the traces between them short.
2. Use wide traces between the power components and for power connections to the DC-DC converter circuit.
3. Connect the ground pins of the input and output filter capacitors and catch diode as close as possible using generous component-side copper fill as a pseudo-ground plane. Then, connect this to the ground-plane with several vias.
4. Arrange the power components so that the switching current loops curl in the same direction.
5. Route high-frequency power and ground return as direct continuous parallel paths.
6. Separate noise sensitive traces, such as the voltage feedback path, from noisy traces associated with the power components.
7. Ensure a good low-impedance ground for the converter IC.
8. Place the supporting components for the converter IC, such as compensation, frequency selection and charge-pump components, as close to the converter IC as possible but away from noisy traces and the power components. Make their connections to the Converter IC and its pseudo-ground plane as short as possible.
9. Place noise sensitive circuitry, such as radio-modem IF blocks, away from the DC-DC converter, CMOS digital blocks, and other noisy circuitry.

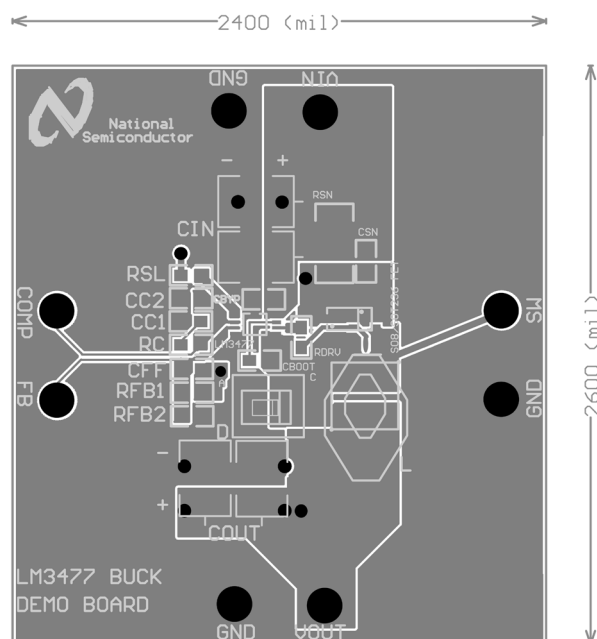


Figure 7. LM3477 Evaluation Board PCB Layout (Top Side)

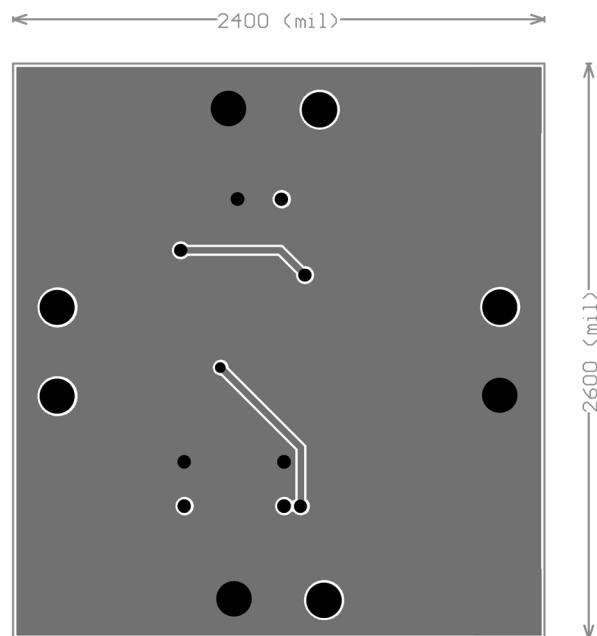


Figure 8. LM3477 Evaluation Board PCB Layout (Bottom Side)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com