

AN-1522 LM5069 Evaluation Board

1 Introduction

The LM5069EVAL evaluation board provides the design engineer with a fully functional hot swap controller board designed for positive voltage systems. This board contains an LM5069-2, the auto restart version of this IC. This application note describes the various functions of the board, how to test and evaluate it, and how to change the components for a specific application. For more information, view the *LM5069 Positive High Voltage Hot Swap / Inrush Current Controller with Power Limiting* ([SNVS452](#)) data sheet.

The board's specifications are:

- Input voltage range: +78V maximum, limited by the transient suppressor (Z1)
- Current limit: 5.5 Amps, $\pm 11.8\%$
- Q1 Power limit: 45W
- UVLO Thresholds: 34.4V, $\pm 4.4\%$ and 32.4V, $\pm 2\%$
- OVLO Thresholds: 77.7V, $\pm 2\%$ and 75.7V, $\pm 3.6\%$
- Insertion delay: 600 ms
- Fault timeout period: 38 ms
- Restart time: 7.7 seconds
- Size: 4.0" x 1.4"

2 Board Configuration

 


Figure 1. Evaluation Board - Top Side

The LM5069 evaluation board is shown in [Figure 1](#), and the schematic is shown in [Figure 2](#). The “BACKPLANE” section, at the left end of the board, represents the backplane voltage source. The vertical dashed line is the boundary between the backplane voltage source and the hot swap circuit input. In other words, it represents the edge connector in a card cage system. The toggle switch (SW1) provides a means to “connect” and “disconnect” the hot swap circuit from the backplane voltage source. The circuitry

to the right of the vertical dashed line is the hot swap circuit. The system voltage is to be connected to the input terminal block (J1). The external load is to be connected to the output terminal block (J2). Capacitors C3 and C4 represent capacitance which is typically present on the input of the load circuit, and are present on this evaluation board so the turn-on characteristics of the LM5069 may be tested without having to connect a load.

For a hot swap circuit to function reliably, capacitance is needed on the supply side of the system connector (C7). Its purpose is to minimize voltage transients which occur whenever the load current changes or is shut off. If the capacitance is not present, wiring inductance in the supply lines generate a voltage transient at shutoff which can exceed the absolute maximum rating of the LM5069, resulting in its destruction.

The LM5069EVB is supplied with pins 2-3 jumpered on JMP1, and pins 1-2 jumpered on JMP2.

 


Figure 2. Evaluation Board Schematic

3 Theory of Operation

The LM5069 provides intelligent control of the power supply connections of a load which is to be connected to a live power source. The two primary functions of a hot swap circuit are in-rush current limiting during turn-on, and monitoring of the load current for faults during normal operation. Additional functions include Under-Voltage Lock-Out (UVLO) and Over-Voltage Lock-Out (OVLO) to ensure voltage is supplied to the load only when the system input voltage is within a defined range, power limiting in the series pass FET (Q1) during turn-on, and a Power Good logic output (PGD) to indicate the circuit status.

Upon applying the input voltage to the LM5069 (for example, SW1 is switched on), Q1 is initially held off for the insertion delay (≈ 600 ms) to allow ringing and transients at the input to subside. At the end of the insertion delay, if the input voltage at VIN is between the UVLO and OVLO thresholds, Q1 is turned on in a controlled manner to limit the in-rush current. If the in-rush current were not limited during turn-on, the current would be high (very high!) as the load capacitors (C3, C4) charge up, limited only by the surge current capability of the voltage source, C7's characteristics, and the wiring resistance (a few milliohms). That very high current could damage the edge connector, PC board traces, and possibly the load capacitors receiving the high current. Additionally, the dV/dt at the load's input is controlled to reduce possible EMI problems.

The LM5069 limits in-rush current to a safe level using a two step process. In the first portion of the turn-on cycle, when the voltage differential across Q1 is highest, Q1's power dissipation is limited to a peak of 45W by monitoring its drain current (the voltage across R10) and its drain-to-source voltage. Their product is maintained constant by controlling the drain current as the drain-to-source voltage decreases (as the output voltage increases). This is shown in the constant power portion of [Figure 3](#) where the drain current is increasing to I_{LIM} . When the drain current reaches the current limit threshold (5.5 Amps), it is then maintained constant as the output voltage continues to increase. When the output voltage reaches the input voltage (V_{DS} decreases to near zero), the drain current then reduces to a value determined by the load. Q1's gate-to-source voltage then increases to $\approx 12V$ above the OUT voltage. The circuit is now in normal operation mode.

Monitoring of the load current for faults during normal operation is accomplished using the current limit circuit described above. If the load current increases to 5.5 Amps (55 mV across R10), Q1's gate is controlled to prevent the current from increasing further. When current limiting takes effect, the fault timer limits the duration of the fault. At the end of the fault timeout period (≈ 38 ms) Q1 is shut off, denying current to the load. The LM5069-2 then initiates a restart every 7.7 seconds. The restart consists of turning on Q1 and monitoring the load current to determine if the fault is still present. After the fault is removed, the circuit powers up to normal operation at the next restart.

In a sudden overload condition (the output is shorted to ground), it is possible the current could increase faster than the response time of the current limit circuit. In this case, the circuit breaker sensor shuts off Q1's gate rapidly when the voltage across R10 reaches ≈ 105 mV. When the current reduces to the current limit threshold, the current limit circuitry then takes over.

The PGD logic level output is low during turn-on, and switches high when the output voltage at OUT has increased to within 1.25V of the input voltage, signifying the turn-on procedure is essentially complete. If the OUT voltage decreases more than 2.5V below VIN due to a fault, PGD switches low. The high level voltage at PGD can be any appropriate voltage up to +80V, and can be higher or lower than the voltages at VIN and OUT.

The UVLO and OVLO thresholds are set by resistors R1-R3. The UVLO and OVLO thresholds are reached when the voltage at the UVLO and OVLO pins each reach 2.5V, respectively. The internal 21 μ A current sources provide hysteresis for each of the thresholds.

 


Figure 3. Power Up Using Power Limit and Current Limit

4 Board Layout and Probing Cautions

The [Figure 1](#) shows the placement of the circuit components. The following should be kept in mind when the board is powered:

1. High voltage, equal to V_{IN} , is present on C3, C4, C7, Q1, and various points within the circuit. Use CAUTION when probing the circuit to prevent injury, as well as possible damage to the circuit.
2. At maximum load current (5.5A), the wire size and length used to connect the power source and the load become important. The wires connecting this evaluation board to the power source **SHOULD BE TWISTED TOGETHER** to minimize inductance in those leads. The same applies for the wires connecting this board to the load. This recommendation is made in order to minimize high voltage transients from occurring when the load current is shut off.

5 Board Connections/Startup

The input voltage source is connected to the J1 connector, and the load is connected to the J2 connector at the OUT and GND terminals. USE TWISTED WIRES. A voltmeter should be connected to the input terminals, and one to the output terminals. The input current can be monitored with an ammeter or current probe. To monitor the status of the PGD output, connect a voltmeter from PGOOD to GND on the J2 terminal block. Put the toggle switch in the ON position.

Increase the input voltage gradually. The input current should remain less than 2 mA until the upper UVLO threshold is reached ($\approx 34.4V$). When the threshold is reached, Q1 is turned on as described in [Section 3](#). If viewed on an oscilloscope, the input current increases as shown in [Figure 3](#) before settling at the value defined by the load. The turn-on timing depends on the input voltage, power limit setting, current limit setting, and the final load current, and is between ≈ 3.0 ms with no load current, and ≈ 7.5 ms with a 4A load current, with $V_{IN} = 36V$. See [Figure 3](#), [Figure 9](#), and [Figure 10](#).

6 Circuit Parameter Changes

Current Limit

The current limit threshold is set by R10 according to the following equation:

$$I_{LIM} = 55 \text{ mV}/R_{10} \quad (1)$$

If the load current increases such that the voltage across R10 reaches 55 mV, the LM5069 then modulates Q1's gate to limit the current to that level. This evaluation board is supplied with a 10 mohm resistor for R10, resulting in a current limit of 5.5A. To change the current limit threshold replace R10 with a resistor of the required value and power capability.

Power Limit

The maximum power dissipated in Q1 during turn-on, or due to a fault, is limited by R9 and R10 according to the following equation:

$$P_{FET(LIM)} = \frac{R9}{1.25 \times 10^5 \times R10} \quad (2)$$

With the components supplied on the evaluation board, $P_{FET(LIM)} = 45W$. During turn-on, when the voltage across Q1 is high, its gate is modulated to limit its drain current so the power dissipated in Q1 does not exceed 45W. As the drain-to-source voltage decreases, the drain current increases, maintaining the power dissipation constant. When the drain current reaches the current limit threshold set by R10 (5.5A), the current is then maintained constant until the output voltage reaches its final value. The current then decreases to a value determined by the load. See [Figure 9](#) and [Figure 10](#).

Each time Q1 is subjected to the maximum power limit conditions it is internally stressed for a few milliseconds. For this reason, the power limit threshold must be set lower than the limit indicated by the FET's SOA chart. In this evaluation board, the power limit threshold is set at 45W, compared to $\approx 150W$ limit indicated in the Vishay SUM40N15-38 data sheet. The FET manufacturer should be contacted for more information on this subject.

Insertion Time

The insertion time starts when the input voltage at VIN reaches 7.6V, and its duration is equal to

$$t_{INSERTION} = C8 \times 7.24 \times 10^5 \quad (3)$$

During the insertion time, Q1 is held off regardless of the voltage at VIN. This delay allows ringing and transients at VIN subside before the input voltage is applied to the load via Q1. The insertion time on this evaluation board is ≈ 600 ms. See [Figure 8](#).

7 Fault Detection and Restart

If the load current increases to the fault level (the current limit threshold, 5.5A), an internal current source charges the timing capacitor at the TIMER pin. When the voltage at the TIMER pin reaches 4.0V, the fault timeout period is complete, and the LM5069 shuts off Q1. The restart sequence then begins, consisting of seven cycles at the TIMER pin between 4.0V and 1.25V, as shown in [Figure 4](#). When the voltage at the TIMER pin reaches 0.3V during the eighth high-to-low ramp, Q1 is turned on. If the fault is still present, the fault timeout period and the restart sequence repeat.

 


Figure 4. Fault Timeout and Restart Sequence

The fault timeout period and the restart timing are determined by the TIMER capacitor according to the following equations:

$$t_{FAULT} = C8 \times 4.7 \times 10^4 \quad (4)$$

$$t_{RESTART} = C8 \times 9.4 \times 10^6 \quad (5)$$

The waveform at the TIMER pin can be monitored at the test pad located between C8 and R9. In this evaluation board, the fault timeout period is ≈ 38 ms, and the restart time is ≈ 7.7 seconds. See Figures 11 and 12.

8 UVLO/OVLO Input Voltage Thresholds

As supplied, the input voltage UVLO thresholds on this evaluation board are approximately 34.4V increasing, and 32.4V decreasing. The OVLO thresholds are approximately 77.7V increasing, and 75.7V decreasing. The four thresholds are determined by resistors R1-R4. The threshold voltage at each pin is 2.50V, and internal 21 μ A current sources provide hysteresis for each threshold. See the device data sheet for more details.

Option A: This evaluation board is supplied with the jumper at JMP1 on pins 2-3, resulting in the configuration shown in Figure 5.

 


Figure 5. UVLO, OVLO Inputs (Option A)

To change the thresholds in this configuration, resistors R1-R3 are calculated using the following procedure:

- Choose the upper UVLO threshold (V_{UVH}), and the lower UVLO threshold (V_{UVL}).
- Choose the upper OVLO threshold (V_{OVH})

The lower OVLO threshold (V_{OVL}) cannot be chosen in advance in this case, but is determined after the values for R1-R3 are determined. If V_{OVL} must be accurately defined in addition to the other three thresholds, see Option B below.

The resistors are calculated as follows:

$$R1 = \frac{V_{UVH} - V_{UVL}}{21 \mu A} \quad (6)$$

$$R3 = \frac{2.5V \times R1 \times V_{UVL}}{V_{OVH} \times (V_{UVL} - 2.5V)} \quad (7)$$

$$R2 = \frac{2.5V \times R1}{(V_{UVL} - 2.5V)} - R3 \quad (8)$$

The lower OVLO threshold is calculated from:

$$V_{OVL} = [(R1 + R2) \times \frac{(2.5V)}{R3} - 21 \mu A] + 2.5V \quad (9)$$

Option B: If all four thresholds must be determined accurately, move the jumper at JMP1 to pins 1-2, and add R4, resulting in the configuration shown in Figure 6.

 


Figure 6. UVLO, OVLO Inputs (Option B)

The four resistor values are calculated as follows:

Choose the upper and lower UVLO thresholds (V_{UVH}) and (V_{UVL}).

$$R1 = \frac{V_{UVH} - V_{UVL}}{21 \mu A} \quad (10)$$

$$R4 = \frac{2.5V \times R1}{(V_{UVL} - 2.5V)} \quad (11)$$

Choose the upper and lower OVLO threshold (V_{OVH}) and (V_{OVL}).

$$R2 = \frac{V_{OVH} - V_{OVL}}{21 \mu A} \quad (12)$$

$$R3 = \frac{2.5V \times R2}{(V_{OVH} - 2.5V)} \quad (13)$$

CAUTION: The Absolute Maximum Rating for the OVLO pin is 7V. Do not let the voltage on OVLO exceed 7V when VIN is at its maximum value. The Absolute Maximum Rating for the UVLO pin is 100V.

Option C: The minimum UVLO level is obtained by positioning the jumper at JMP1 on pins 1-2, and leaving R4 open, resulting in the configuration shown in Figure 7. Q1 is switched on when the voltage at VIN reaches the POR_{EN} threshold ($\approx 8.4V$). The OVLO thresholds are set by R2 and R3, and their values are calculated using the procedure in Option B. The value for R1 is not critical, and can be as supplied. SEE THE CAUTION ABOVE.

 


Figure 7. Minimum UVLO Threshold, Adjustable OVLO

Option D: The OVLO function can be disabled by removing the jumper from JMP1. The UVLO thresholds are set by R1 and R4 using the procedure in option B or C above.

9 Shutdown

With the circuit in normal operation, the LM5069 can be shutdown by grounding the UVLO pin. Test point TP1, located next to JMP1, can be used for this purpose. See [Figure 13](#).

10 Power Good Output

The PGOOD logic output provides an indication of the circuit's condition. This output is high when the circuit is in normal operation - the OUT voltage is within 1.25V of the input. PGOOD is low when the circuit is shutdown, either intentionally or due to a fault. PGOOD is also high when VIN is less than 5V.


This EVB is supplied with pins 1-2 jumpered on JMP2, powering the PGD pin from the output voltage through a 100 k Ω pull-up resistor. To change the high level PGOOD voltage, move the jumper on JMP2 to pins 2-3, and supply the appropriate pull-up voltage to terminal P1 (located next to JMP2). If the UVLO pin is taken low to disable the LM5069, PGOOD switches low within 10 μ s without waiting for the OUT voltage to fall. See [Figure 14](#).

If a delay at the PGOOD output is desired, a resistor and capacitor can be added at positions R8 and C6.

11 LM5069-1 Latch Version


The LM5069-2 supplied on this evaluation board provides a restart attempt after a fault detection, as described above. The companion Hot-Swap IC, the LM5069-1, latches off after a fault detection, with external control required for restart. Restart is accomplished by momentarily taking the UVLO pin below 2.5V, or by removing and re-applying the input voltage at VIN. Contact the nearest Texas Instruments sales office to obtain samples of the LM5069-1.

12 Performance Characteristics

 


Horizontal Resolution: 100 ms/div
Trace 1: TIMER Pin, 2V/div
Trace 2: Vin, 50V/div
Trace 3: Vout, 50V/div
Ct = 0.82 μ F

Figure 8. Insertion Time Delay

 


Horizontal Resolution: 1 ms/div
Trace 1: GATE Pin, 20V/div
Trace 2: PGOOD Pin, 50V/div
Trace 3: Vout, 20V/div
Trace 4: Input Current, 2A/div
 $V_{IN} = 36V$

Figure 9. Turn-On Sequence with Zero Load Current

 


Horizontal Resolution: 2 ms/div
Trace 1: GATE Pin, 20V/div
Trace 2: PGOOD Pin, 50V/div
Trace 3: Vout, 20V/div
Trace 4: Input Current, 2A/div
 $V_{IN} = 36V$

Figure 10. Turn-On Sequence with 4A Load Current

 


Horizontal Resolution: 10 ms/div
Trace 1: TIMER Pin, 2V/div
Trace 2: GATE Pin, 50V/div
Trace 3: Vout, 50V/div
Trace 4: Input Current, 5A/div
 $C_t = 0.82 \mu\text{F}$
 $V_{IN} = 48\text{V}$

Figure 11. Fault Timeout

 


Horizontal Resolution: 1s/div
Trace 2: TIMER Pin, 2V/div
Trace 3: Vout, 5V/div
 $C_t = 0.82 \mu\text{F}$

Figure 12. Restart Timing

 

Horizontal Resolution: 2 ms/div
 Trace 1: UVLO Pin, 2V/div
 Trace 2: GATE Pin, 50V/div
 Trace 3: Vout, 50V/div
 Trace 4: Input Current, 5A/div
 $V_{IN} = 48V$

Figure 13. Output Shutdown Using the UVLO Pin

 

Horizontal Resolution: 5 μ s/div
 Trace 1: PGOOD Pin, 20V/div
 Trace 2: UVLO Pin, 2V/div
 Trace 3: Vout, 20V/div

Figure 14. Turn-Off Using the UVLO Pin

13 Bill of Materials

Table 1. Hot Swap Circuit

Item	Description	Mfg., Part No.	Package	Value
C1	Ceramic Capacitor	TDK C3216X7R2A102M	1206	1000 pF, 100V
C5	Ceramic Capacitor	TDK C3216X7R2A104M	1206	0.1 μ F, 100V
C6	Unpopulated			
C8	Ceramic Capacitor	MuRata GRM21BR71C824KCO1L or Panasonic ECJ2YB1A824K	0805	0.82 μ F, 16V or higher
Q1	N-Channel MOSFET	Vishay SUM40N15-38	TO-263	150V, 40A
R1	Resistor	Vishay CRCW12069532F	1206	95.3k, $\frac{1}{4}$ W
R2	Resistor	Vishay CRCW08054641F	0805	4.64k Ω
R3	Resistor	Vishay CRCW08053321F	0805	3.32k Ω
R4	Unpopulated			
R7	Resistor	Vishay CRCW12061003F	1206	100k Ω , $\frac{1}{4}$ W
R8	Resistor	Vishay CRCW08050000Z	0805	Zero ohms
R9	Resistor	Vishay CRCW08055602F	0805	56k Ω
R10	Resistor	Vishay WSL2010R0100F	2010	10 mohm, $\frac{1}{2}$ W
U1	Hot Swap IC	Texas Instruments LM5069	VSSOP-10	
Z1	Trans. Suppressor	Diodes Inc. SMBJ70A	SMB	70V

Table 2. Backplane and Load Sections

Item	Description	Mfg., Part No.	Package	Value
C3, 4, 7	Alum. Electrolytic Capacitor	Panasonic EEV-EB2D101M	Surf. Mount	100 μ F, 200V
SW1	Toggle switch			

14 PC Board Layout

 


Figure 15. Board Silkscreen

 


Figure 16. Board Top Layer

 


Figure 17. Board Bottom Layer (viewed from top)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com