

Demonstration board user guidelines for low-side current sensing with the TS507 operational amplifier

Introduction


This application note describes the STEVAL-ISQ013V1, a demonstration board specifically designed for low-side current sensing with the TS507 operational amplifier.

Power management mechanisms are found in most electronic systems. Current sensing is useful for protecting your applications. The low-side current sensing method consists in placing a sense resistor between the load and the circuit's ground. The resulting voltage drop is amplified using the TS507.

This document describes how to accurately measure the current in your applications. It provides:

- the advantages of the low-side current sense method.
- the schematics and layout of the demonstration board.
- a description of the TS507's main features.
- a method for selecting the most appropriate components for your application.
- theoretical and practical results.

Figure 1. Demonstration board

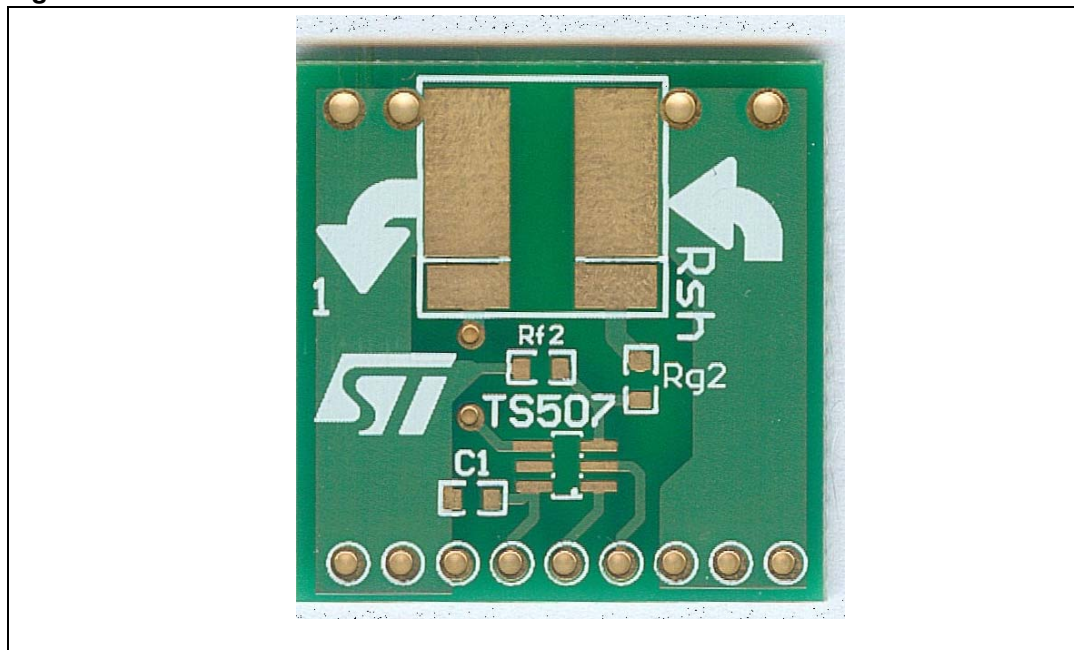


1 Advantages of the low-side current sense method

The common-mode voltage is close to ground, despite the voltage of the power source. Therefore, the current sense voltage can be amplified by a low-voltage operational amplifier (no Vicm restriction).

2 Schematic and layout of the demonstration board

Figure 2 represents the board's schematics.

Figure 2. Demonstration board schematics

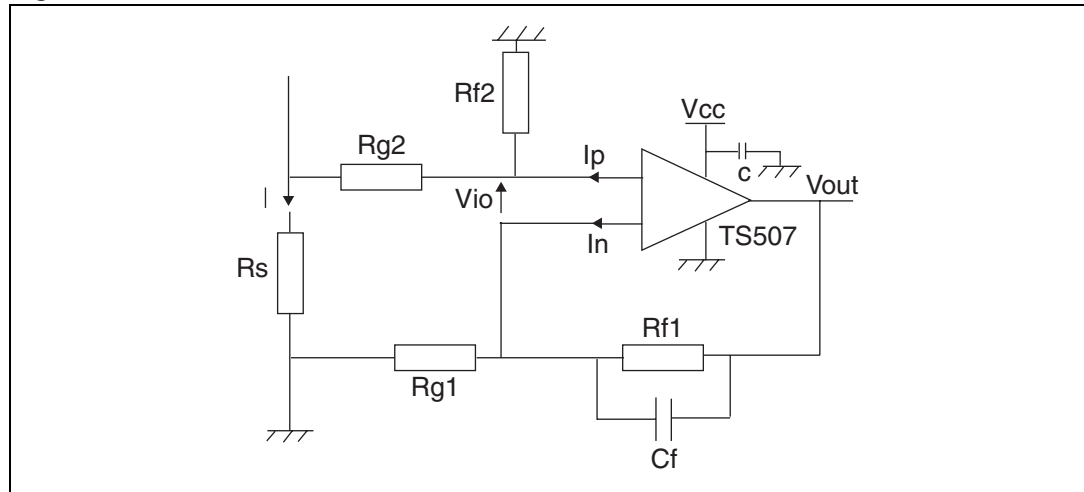

The demonstration board has the following features.

- Board dimensions: 27 x 24 mm
- 2-layer PCB
- PCB thickness: 0.8 mm
- FR4 material
- Copper thickness: 18 μm

Figure 3. Demonstration board: top view


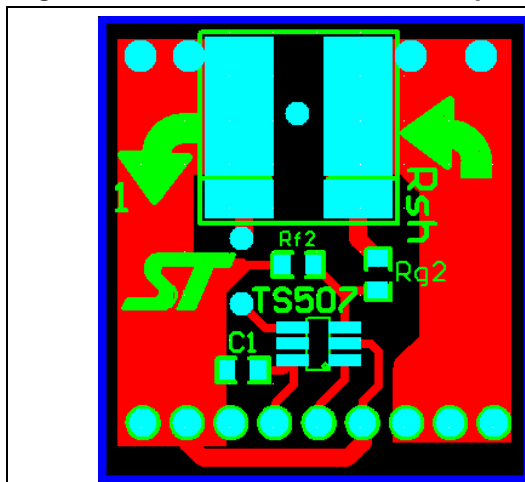


Figure 4. Demonstration board: bottom view

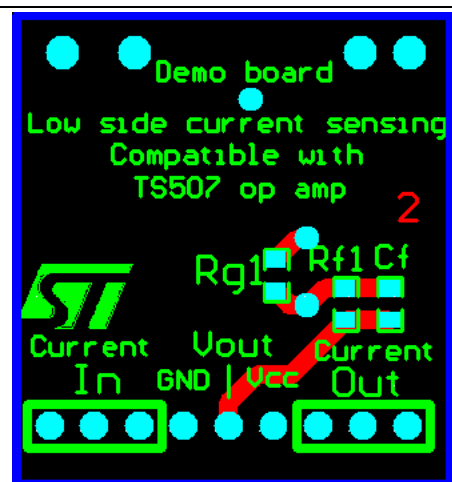

3 TS507 features

The TS507 operates from 2.7 to 5.5 V. The device has a rail-to-rail configuration on both its input and output. At 25°C it demonstrates the following features.

- $V_{io} = 25 \mu\text{V typ, } 100 \mu\text{V max}$
- $AVD = 131 \text{ dB (typical } V_{cc} = 5 \text{ V)}$
- $GBP = 1.9 \text{ MHz}$
- $V_{ol} = 4 \text{ mV typ, } 15 \text{ mV max, with } R_L = 10 \text{ k}\Omega$

Additional information on the TS507 can be found at:

http://www.st.com/stonline/products/families/amplifiers_comparators/opamps/ts507amp.htm

4 Selecting the components

Depending on the type of application, various component values can be selected, such as *Rshunt* or resistors for the amplifier gain.

To select the correct component values:

1. **Find the maximum current.**

This is the maximum current that goes through the sensing resistor (the maximum current to sense in your system).

For example:

$$I_{\max} = \text{Power}_{\max} / \text{voltage} = 5 \text{ W} / 5 \text{ V} = 1 \text{ A}$$

2. **Find the correct shunt resistor.** This value must be limited to avoid a significant voltage drop (such as 1%) and to limit power dissipation. It must, however, be high enough to obtain better accuracy.

For example: $V_{\text{sense_max}} = 1\% \text{ voltage}$, with $\text{voltage} = 5 \text{ V}$ and $I_{\max} = 1 \text{ A}$

$$R_{\text{shunt}} \times I_{\max} \leq V_{\text{sense_max}}$$

$$\Rightarrow R_{\text{shunt}} \leq \frac{1\% \cdot 5 \text{ V}}{1 \text{ A}}$$

So R_{shunt} must be lower than or equal to 50 mΩ. In the current example, R_{shunt} has been set to 30 mΩ

3. **Calculate the maximum power dissipation in the shunt resistor.** To avoid damaging the sensing resistor, the shunt resistor has to sustain a suitable wattage.

For example:

$$P_{\max} = R_{\text{shunt}} \cdot I_{\max}^2 = 0.03 \cdot 1^2 = 0.03 \text{ W}$$

In this case, a 1 W shunt resistor is sufficient.

4. **Choose the appropriate configuration gain.**

$$V_{\text{out}} = (R_f / R_g) \cdot V = (R_f / R_g) \cdot R_{\text{shunt}} \cdot I$$

To avoid saturation:

$$V_{\text{out}} \leq V_{\text{oh}} \Rightarrow R_f < \frac{V_{\text{oh}} \cdot R_g}{R_{\text{shunt}} \cdot I_{\max}}$$

In the current configuration, $R_g = 100 \text{ } \Omega$ and $V_{\text{oh}} = 4.985 \text{ V}$ (TS507 at 25°C, $V_{\text{cc}} = 5 \text{ V}$).

$$R_f \text{ max} = \frac{4.985 \cdot 100}{0.03 \cdot 1} = 16.6 \text{ k}\Omega$$

R_f must therefore be lower than 16.6 kΩ to avoid saturation of the TS507 at maximum currents. It is recommended to choose the highest possible R_f to benefit from the output voltage capability of the amplifier. Selecting R_f in the E192 series leads to $R_f = 16.2 \text{ k}\Omega$

To minimize the offset caused by the input currents, the feedback resistors must be minimized; the higher R_f , the higher the error on I_{io} (see [Equation 2 on page 7](#)). As such, an R_g of 100 Ω must be considered (the lower R_g , the lower R_f).

Note that if the accuracy obtained is not sufficient, you can go back to step [2](#). and increase the R_{shunt} value.

5 Theoretical and practical measurements

5.1 Theoretical results

Cf helps to stabilize the operational amplifier and can be ignored for the DC analysis.

Using [Figure 2](#) as reference for the components:

Equation 1

$$V_{out} = R_s \cdot I \left(1 - \frac{R_{g2}}{R_{g2} + R_{f2}} \right) \cdot \left(1 + \frac{R_{f1}}{R_{g1}} \right) + I_p \left(\frac{R_{g2} \cdot R_{f2}}{R_{g2} + R_{f2}} \right) \cdot \left(1 + \frac{R_{f1}}{R_{g1}} \right) - I_n \cdot R_{f1} - V_{io} \left(1 + \frac{R_{f1}}{R_{g1}} \right)$$

Equation 2

$$V_{out} = R_s \cdot I \frac{R_f}{R_g} - V_{io} \cdot \left(1 + \frac{R_f}{R_g} \right) + R_f \cdot I_{io}$$

This equation can be simplified assuming $R_{f2} = R_{f1} = R_f$, and $R_{g2} = R_{g1} = R_g$.

Only errors due to V_{io} and I_{io} remain.

If we also consider the errors due to inaccuracies of the resistors, we obtain with a first-order limited development and with:

$$V_{th} = R_s \cdot I \cdot \frac{R_f}{R_g}$$

Equation 3

$$V_{out} = V_{th} \left(1 + \frac{\Delta R_s}{R_s} + \frac{R_f}{R_f + R_g} \left(\frac{\Delta R_{f1}}{R_{f1}} - \frac{\Delta R_{g1}}{R_{g1}} \right) + \frac{R_g}{R_f + R_g} \left(\frac{\Delta R_{f2}}{R_{f2}} - \frac{\Delta R_{g2}}{R_{g2}} \right) \right) + R_f \cdot I_{io} - V_{io} \left(1 + \frac{R_f}{R_g} \right)$$

As you can see, with correct resistor matching (R_f and R_g) on the inputs, I_{io} does not have any influence on V_{out} .

$\frac{\Delta R}{R}$ is the resistance tolerance.

For example: 0.1% in our case for R_g and R_f , and 1% for R_{shunt} .

If the accuracy of the resistors R_{f1} , R_{f2} , R_{g1} and $R_{g2} = \varepsilon_1$ and the accuracy of $R_{shunt} = \varepsilon_2$, these inaccuracies create a maximum deviation of $(2 \cdot \varepsilon_1 + \varepsilon_2) V_{th}$ as shown in [Equation 4](#).

Equation 4

$$V_{th} \left(\frac{\Delta R_s}{R_s} + \frac{R_f}{R_f + R_g} \left(\frac{\Delta R_{f1}}{R_{f1}} + \frac{\Delta R_{g1}}{R_{g1}} \right) + \frac{R_g}{R_f + R_g} \left(\frac{\Delta R_{f2}}{R_{f2}} + \frac{\Delta R_{g2}}{R_{g2}} \right) \right) = V_{th} \left(\varepsilon_2 + \frac{R_f}{R_f + R_g} 2 \cdot \varepsilon_1 + \frac{R_g}{R_f + R_g} 2 \cdot \varepsilon_1 \right) \\ = V_{th} (\varepsilon_2 + 2 \cdot \varepsilon_1)$$

[Equation 3](#) can be simplified to become:

Equation 5

$$V_{out} = V_{th} + \varepsilon \% \cdot V_{th} + R_f \cdot I_{io} - V_{io} \left(1 + \frac{R_f}{R_g} \right)$$

[Figure 5 on page 8](#) depicts the theoretical behavior of the above-defined application.

V_{out_th} , V_{out_min} and V_{out_max} are represented from the left Y-axis.


V_{out_min} and V_{out_max} take into consideration V_{oh} , V_{ol} and errors caused by inaccuracies of the input currents, V_{io} or the resistors. The measured values should therefore be between these curves.

The error on output (in yellow) is represented from the right Y-axis and is defined as follows.

Equation 6

$$\text{Error}(\%) = \frac{\text{Max}(|V_{out_max} - V_{out_th}|, |V_{out_min} - V_{out_th}|)}{V_{out_th}} \cdot 100$$

Figure 5. Theoretical output voltage and error vs. I_s/I_{max}

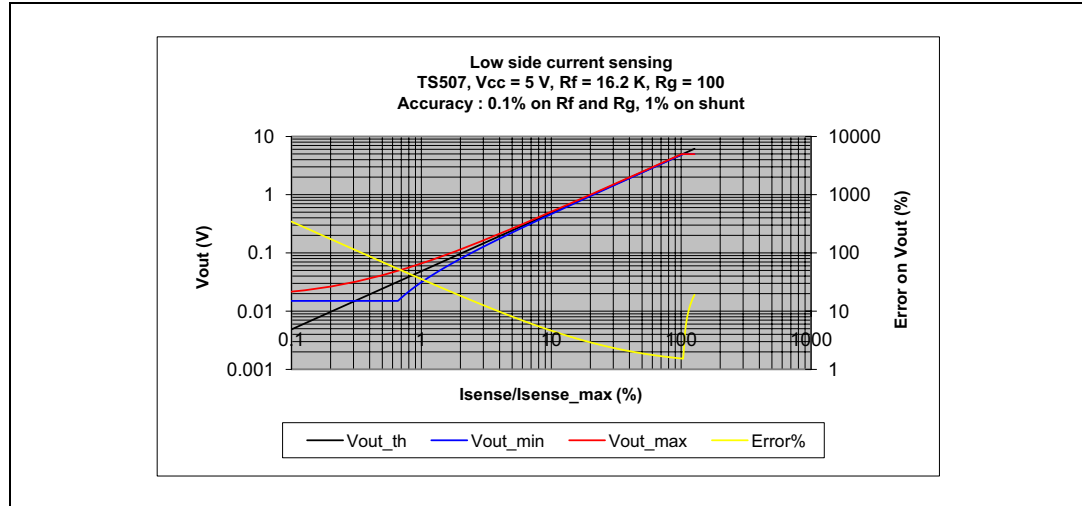

Example: if $I_{max} = 1\text{ A}$, with the same conditions on the resistors as in [Figure 5](#):

- $I_{sense} = 0.1\text{ A}$, $I_{sense}/I_{max} = 10\%$
=> the error on the measured voltage is lower than 5% at 10% full scale of I_{sense} .
- $I_{sense} = 0.5\text{ A}$, $I_{sense}/I_{max} = 50\%$
=> the error on the measured voltage is lower than 2% at 50% of the full-scale I_{sense} .

Note that when I_{sense} is used to its full scale, the offset caused by V_{io} and the input bias current is limited and the errors on the output voltage converge towards the predicted value of $2 \times 0.1\% + 1\% = 1.2\%$

The accuracy of the measured value depends on the accuracy of the resistors R_f , R_g and R_{shunt} but also on V_{sense_max} and of course the amplifier. [Table 1](#) shows the maximum error for various configurations of the TS507 while applying the method described in this application note.

Table 1. Maximum error on measured value depending on I_{max} for TS507

I _{max}	R _s (Ω)	R _g (Ω)	R _f (Ω)	I _{sense} /I _{max} (%)				
	ε = 1%	ε = 0.1%	ε = 0.1%	1	3	10	30	100
1	0.05	100	9k76	21	7.6	3.1	1.7	1.4
2	0.02	100	12k1	25.5	9.3	3.6	2	1.4
3	0.01	100	16k2	32	12	4.3	2.3	1.5
4	0.01	100	12k1	25.2	9.2	3.5	2	1.5
5	0.01	100	9k76	22	8.1	3.3	1.9	1.4
7	0.005	100	14k	30.7	11	4.1	2.2	1.5
10	0.005	100	9k76	21.9	8.1	3.3	1.9	1.4
12	0.003	100	13k5	30	10.8	4.1	2.2	1.5
15	0.003	100	10k9	24.2	8.9	3.5	2	1.4
20	0.002	100	12k1	27	9.7	3.8	2.1	1.5
				Max Error (%)				

R_s has been calculated for a maximum sense voltage of 50 mV (it represents 1% of the voltage drop for a 5 V voltage source).

5.2 Practical results

This section summarizes the results of four practical measurements ([Figure 6](#) to [Figure 9](#)).

- Case 1: R_{shunt} = 3 mΩ, R_g = 100 Ω, R_f = 150 kΩ, max = 1 A
- Case 2: R_{shunt} = 10 mΩ, R_g = 100 Ω, R_f = 47,5 kΩ, max = 1 A
- Case 3: R_{shunt} = 30 mΩ, R_g = 100 Ω, R_f = 16,2 kΩ, max = 1 A
- Case 4: R_{shunt} = 100 mΩ, R_g = 100 Ω, R_f = 4,75 kΩ, max = 1 A

For each condition, five TS507 operational amplifiers have been measured with the same board. All resistors have an accuracy of 0.1% except for the shunt resistors, which have an accuracy of 1%.

The left part of the figure shows the output voltage versus I_{sense}/I_{max}. The maximum and minimum theoretical output voltages are shown in red and blue respectively. These have been calculated using [Equation 3 on page 7](#). You can see that the output voltage of the operational amplifiers is as predicted between these two trends.

The right part of the figure shows the absolute error on the output voltage versus I_{sense}/I_{max}. The red trend shows the maximum theoretical error that can occur. As expected, all of our measurements are below this trend. The main error is due to V_{io}: the lower V_{io} is, the more accurate the results will be.

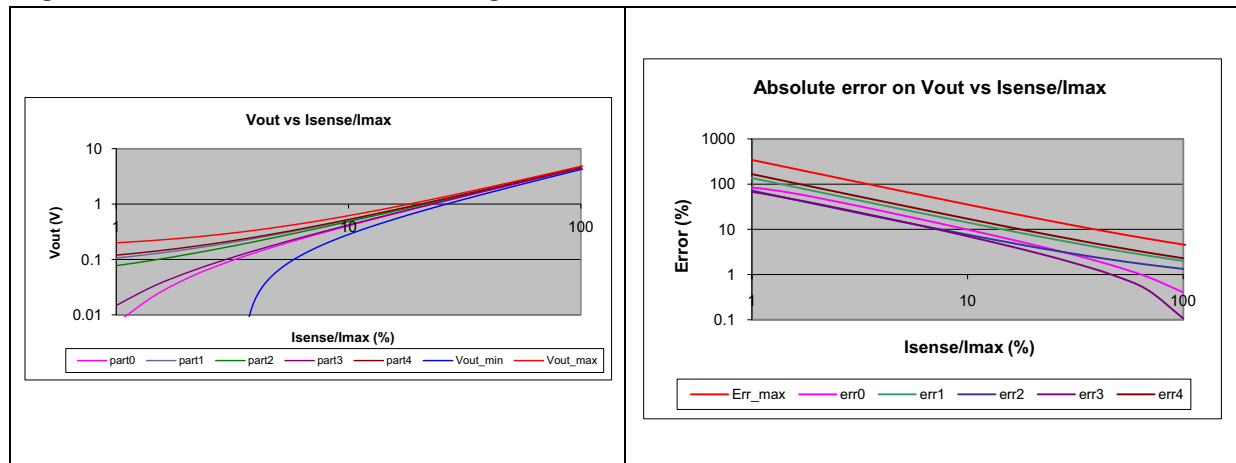
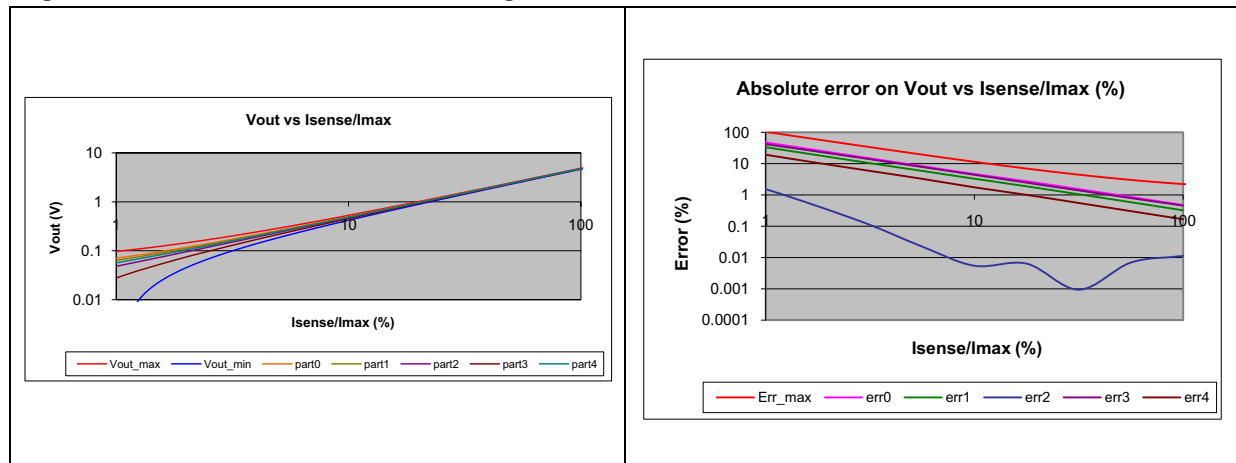
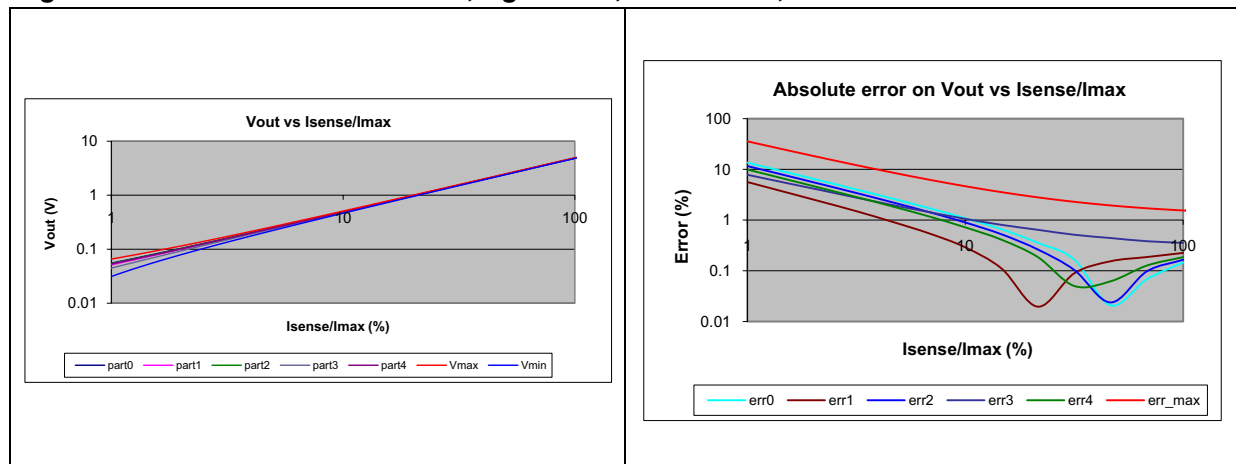
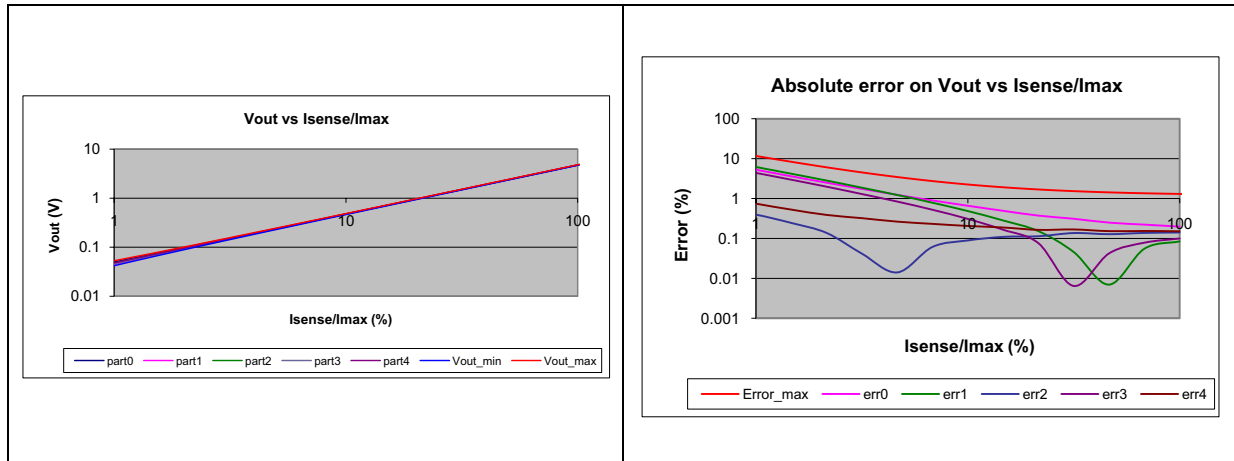
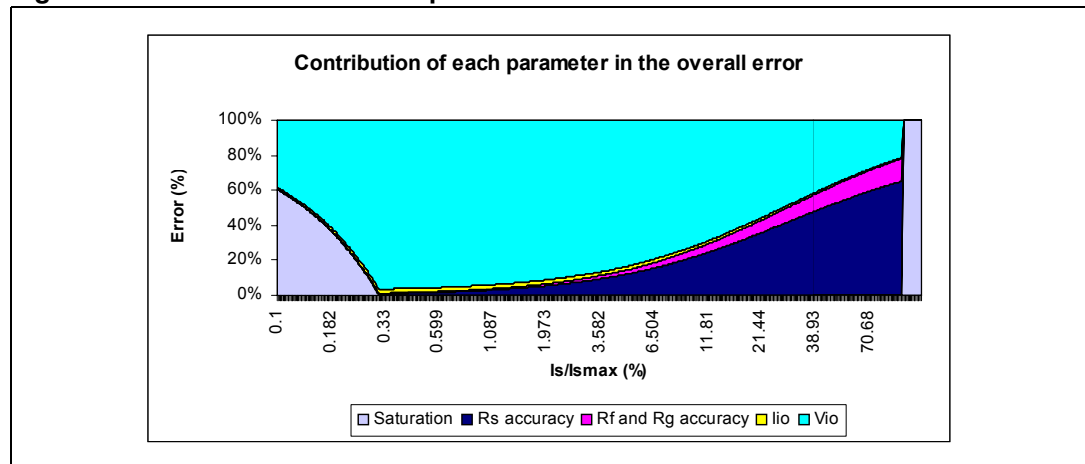
Figure 6. Case 1: $R_{shunt} = 3\text{ m}\Omega$, $R_g = 100\text{ }\Omega$, $R_f = 150\text{ k}\Omega$, $I_{max} = 1\text{ A}$ **Figure 7. Case 2: $R_{shunt} = 10\text{ m}\Omega$, $R_g = 100\text{ }\Omega$, $R_f = 47.5\text{ k}\Omega$, $I_{max} = 1\text{ A}$** **Figure 8. Case 3: $R_{shunt} = 30\text{ m}\Omega$, $R_g = 100\text{ }\Omega$, $R_f = 16.2\text{ k}\Omega$, $I_{max} = 1\text{ A}$** 

Figure 9. Case 4: $R_{shunt} = 100\text{ m}\Omega$, $R_g = 100\text{ }\Omega$, $R_f = 4.75\text{ k}\Omega$, $I_{max} = 1\text{ A}$ 

The graphs show that the higher R_{shunt} is for the same I_{sense_max} , the more accurate the results are. This is due to the fact that if the shunt resistor is small, the schematic gain is high, so V_{io} is more amplified than with a bigger shunt resistor.

Figure 10 shows the error contribution of each parameter in the overall error for Case 3.

You can see that for a low I_{sense}/I_{max} the maximum error is due to the saturation. Then, when I_{sense}/I_{max} increases, the maximum error is caused by the V_{io} . After this, the most significant error is caused by the inaccuracy of the shunt resistor. To finish, when I_{sense}/I_{max} is high, you are close to the upper rail of the amplifier, therefore the maximum error contribution is due to the saturation.

Figure 10. Contribution of each parameter in the overall error

The error due to the AVD parameter has not been taken into consideration in these equations, but it is negligible. If the schematic gain equals 162 (in Case 3) and the AVD equals 100 dB, there is an inaccuracy of 0.16%.

The following equation demonstrates this.

Equation 7

$$\frac{V_{out}}{V_s} = \frac{\frac{R_f}{R_g}}{1 + \frac{R_f}{R_g \cdot AVD}} \quad \text{when } \frac{R_f}{R_g} \ll AVD: \quad \frac{V_{out}}{V_s} = \frac{\frac{R_f}{R_g}}{1 + \varepsilon} = \frac{R_f}{R_g} (1 - \varepsilon)$$

$$\text{Error} = \frac{R_f}{R_g \cdot AVD} \cdot 100\%$$

For example:

$$\text{Case 3: } \frac{R_f}{R_g} = 162 \quad AVD = 100 \text{ dB}$$

$$\text{Error} = \frac{162}{10^5} \cdot 100\% = 0.16\%$$

You can see that the higher the gain of the schematics, the higher the inaccuracy. Nevertheless, the typical AVD for the TS507 equals 131 dB. With this value, the error is divided by more than 35.

6 Frequency behavior

This chapter provides different AC cases permitting the filtering of the measurements.

To sense in a large bandwidth, the gain of the application must not exceed the capability of the amplifier. If the gain is too big, you will be limited by the gain-bandwidth product or by the amplifier's slew rate. As such, for test purposes, we have selected the same conditions as in Case 4 ([Figure 9](#)).

$$R_{\text{shunt}} = 100 \text{ m}\Omega \quad R_g = 100 \text{ }\Omega \text{ and } R_f = 4.75 \text{ k}\Omega$$

The two first cases deal with the filtering of the measurement for a current source which should be constant. The easiest way to achieve it is to add the capacitor named C_f in [Figure 2](#).

In [Figure 11](#) and [Figure 12](#), you can see that the period of oscillations is $T = 300 \text{ }\mu\text{s}$, so the frequency equals 3.33 kHz.

The following equation demonstrates how to select the value of C_f to filter the oscillations.

Equation 8

$$F = \frac{1}{2\pi \cdot R_f \cdot C_f} \text{ so } C_f = \frac{1}{2\pi \cdot F \cdot R_f} = \frac{1}{2\pi \cdot 3330 \cdot 4750} = 10 \text{ nF}$$


To efficiently cut this frequency, you have to cut one decade earlier, so you have to set C_f to 100 nF.

On the left part of [Figure 11](#), the measurement has been performed without the capacitor, and on the right part a capacitor of 100nF has been added. A current of about 1 A is applied.



You can see that the signal is correctly filtered by the capacitor.

Figure 11. Filtering: first example without capacitor

with capacitor: $C_f = 100 \text{ nF}$

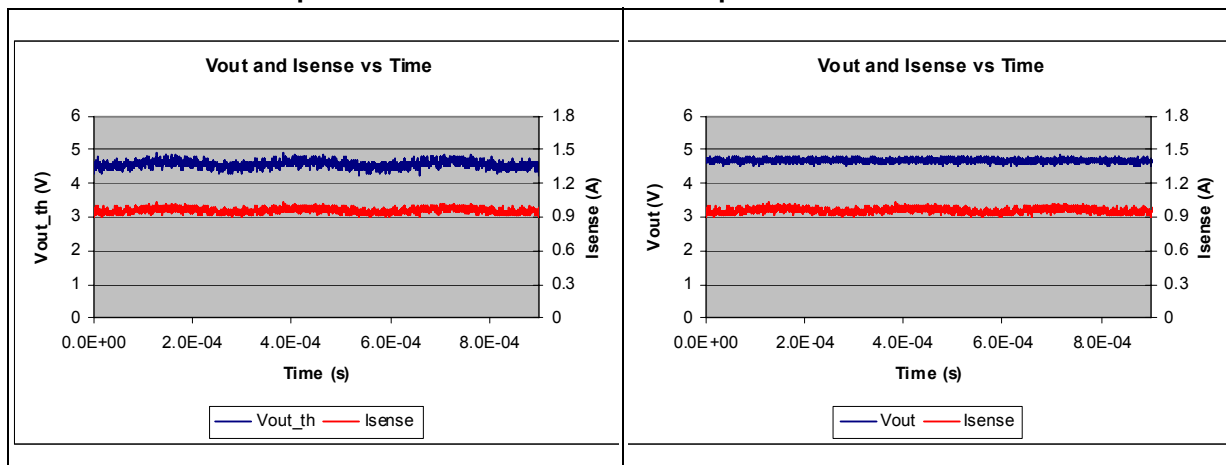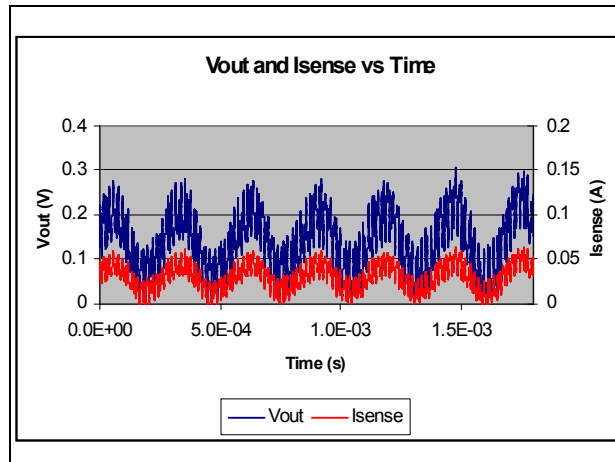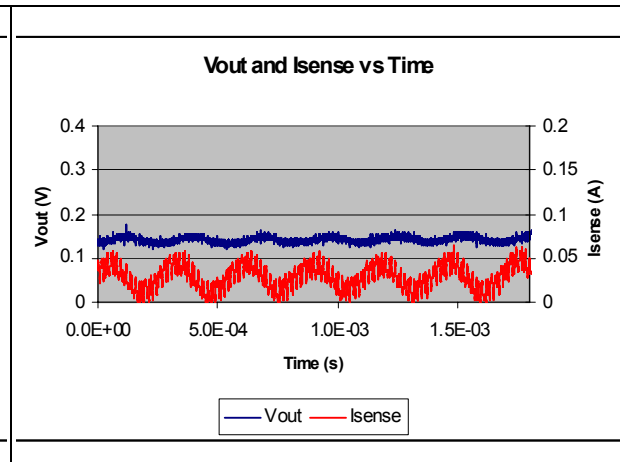

[Figure 12](#) shows another example with a lower I_{sense} .

**Figure 12. Filtering: second example
without capacitor****with capacitor: Cf = 100 nf**

As you can see, the signal is filtered. If you increased the capacitor to 1 μF instead of 100 nF you would obtain an even smoother response.

This application note shows the theoretical and practical results, but verifying the behavior with the spice model and, above all, checking the results on bench is recommended.

7 Bill of materials

Table 2. Bill of materials

Part	Footprint	Description	Value	Qty
TS507	SOT23-5	Precision amplifier	TS507	1
Rf	0603	Resistor 0.1%	16.2 k Ω ⁽¹⁾	2
Rg	0603	Resistor 0.1%	100 Ω	2
Rs ⁽²⁾	2512	Resistor 1%	30 m Ω ⁽¹⁾	1
	9.4 x 9.1 mm	Resistor 1%	30 m Ω ⁽¹⁾	
	Strap	Resistor 1%	30 m Ω ⁽¹⁾	
Cf	0603	Capacitor	1 nF ⁽¹⁾	1
C	0603	Decoupling capacitor	1 μ F	1

1. To choose the correct component values, refer to [Chapter 4](#). The default value has been chosen for a power source of 5 V, sourcing a maximum current of 1 A.
2. Only one shunt resistor is required, several footprints are available.

8 Conclusion

This document provides the information necessary to develop your low-side current sensing application using the TS507. You can accurately measure current with a limited number of components even if the sense current is noisy. With the theoretical equations provided, you can easily predict the maximum error on the output voltage. To minimize errors, you must select the components correctly according to the parameters described in this application note.

9 Revision history

Table 3. Document revision history

Date	Revision	Changes
25-Oct-2010	1	Initial release.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2010 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com