

AN–1247 LM2727 Evaluation Board

1 Introduction

The LM2727 evaluation board has been designed for a wide variety of components in order to show the flexibility of the LM2727 chips. The input voltage limitations are the same as the chip: 2.2 to 16 VDC. The regulated output voltage range is from 0.6 V up to 85% of the input voltage. Output current is limited by the components chosen, however, the size of this board and the limitation to SOIC-8 MOSFETs means a realistic limit of about 10A.

The example design steps 12 V down to 3.3 V at 4A, with a switching frequency of 800 kHz. This design can be modified by following the *Design Considerations* section of the *LM2727/LM2737 N-Channel FET Synchronous Buck Regulator Controller for Low Output Voltages Data Sheet* ([SNVS205](#)).

The board is four layers, consisting of signal/power traces on top and bottom, with one internal ground plane and an internal split power plane. All planes are 1oz. copper, and the board is 62mil FR4 laminate.

2 Boot Voltage

The default circuit that comes with the LM2727 demo board uses a bootstrap diode and small capacitor (D1 and Cboot) to provide enough gate-to-source voltage on the high side MOSFET to drive the FET. If a separate rail is available that is more than twice the value of V_{IN} , this higher voltage can be connected directly to the BOOT pin, via the BOOT connector, with a 0.1 μ F bypass capacitor, Cc. In this case, D1 and Cboot should be removed from the board. Do not connect both Cc and Cboot/D1 at the same time.

3 Dual MOSFET Footprints

The LM2727 demo board has two extra footprints for dual N-channel MOSFETs in SOIC-8 packages. Footprint Q3 corresponds to devices with footprints such as the Si4816DY "LITTLEFOOT Plus" from Vishay Siliconix. Footprint Q4 corresponds to devices with footprints such as the Si4826DY, also from Vishay Siliconix.

4 Low-Side Diode

A footprint D2 is available for a Schottky diode to be placed in parallel with the low side FET. This can improve efficiency because a discrete Schottky will have a lower forward voltage than the low side FET's body diode. The footprint fits SMA size devices. If desired, the low side FET can be removed entirely, and the LM2727 will run as an asynchronous Buck controller.

5 Additional Footprints

The 1206 footprints Rc2 and Cc3 are available for designs with more complex compensation needs.

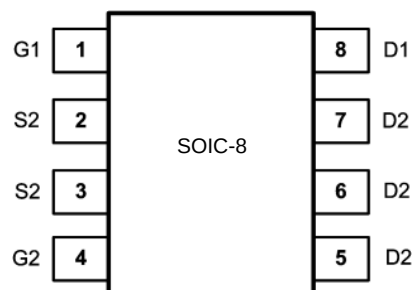


Figure 1. Pinout for Dual FET for Footprint Q3

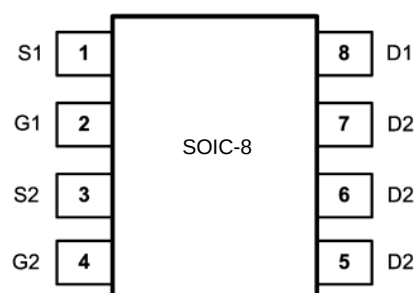


Figure 2. Pinout for Dual FET for Footprint Q4

6 Layout Optimization

The LM2727 PCB layout could be improved with several techniques used in switching converter design. The traces that run from the HG and LG pins of the IC to the gates of the high and low side MOSFETs should be shorter and thicker, reducing their parasitic inductance and resistance. The mid-frequency decoupling capacitor C_{inx} should be placed as close to the pins of the high side MOSFET as possible. The bulk input capacitors C_{in1} and C_{in2} should also be placed close, keeping the loop between the input capacitors and the high side MOSFET small. Likewise, the Schottky diode D2 should be located as close as possible to the pins of the low side MOSFET. The local capacitors C_{in} , C_{boot} , and C_c (if used) should be close to the pins of the LM2727 IC. These techniques help reduce parasitic inductance throughout the PCB.

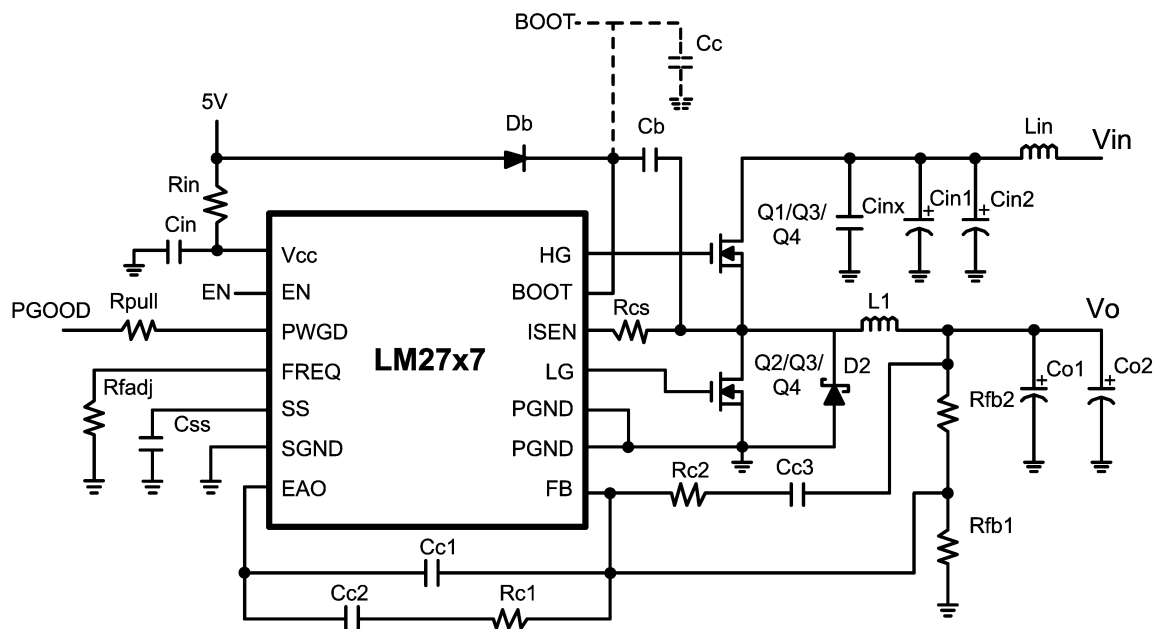


Figure 3. Circuit Schematic

Table 1. Bill of Materials for Typical Application Circuit

ID	Part Number	Type	Size	Parameters	Qty.	Vendor
U1	LM2727	Synchronous Controller	TSSOP-14		1	NSC
Q1	Si4884DY	N-MOSFET	SOIC-8	13.5 mΩ, @ 4.5 V, 15.3 nC	1	Vishay
Q2	Si4884DY	N-MOSFET	SOIC-8	13.5 mΩ, @ 4.5 V, 15.3 nC	1	Vishay
Db	BAT-54	Schottky Diode	SOT-23	30 V	1	ON
Lin	P1168.162T	Inductor	12x12x4.5mm	1.6 μH, 8.5A 5.4 mΩ	1	Pulse
L1	P1168.162T	Inductor	12x12x4.5mm	1.6 μH, 8.5A 5.4 mΩ	1	Pulse
Cin1	C4532X5R1E106M	Capacitor	1812	10 μF 25 V 3.3Arms	2	TDK
Cinx	C3216X7R1E105K	Capacitor	1206	1 μF, 25 V	1	TDK
Co1	6TPB470M	Capacitor	7.3x4.3x3.8mm	470 μF 2.5 V 55 mΩ	2	Sanyo
Cin	C3216X7R1E225K	Capacitor	1206	2.2 μF, 25 V	1	TDK
Css	VJ1206X123KXX	Capacitor	1206	12 nF, 25 V	1	Vishay
Cc1	VJ1206A3R9KXX	Capacitor	1206	3.9 pF 10%	1	Vishay
Cc2	VJ1206A391KXX	Capacitor	1206	390 pF 10%	1	Vishay
Rin	CRCW1206100J	Resistor	1206	10 Ω 5%	1	Vishay
Rfadj	CRCW12063052F	Resistor	1206	30.5 kΩ 1%	1	Vishay
Rc1	CRCW12069532F	Resistor	1206	95.3 kΩ 1%	1	Vishay
Rfb1	CRCW12064871F	Resistor	1206	4.87 kΩ 1%	1	Vishay
Rfb2	CRCW12062181F	Resistor	1206	21.8 kΩ 1%	1	Vishay
Rcs	CRCW1206272J	Resistor	1206	2.7 kΩ 5%	1	Vishay

7 PCB Layout

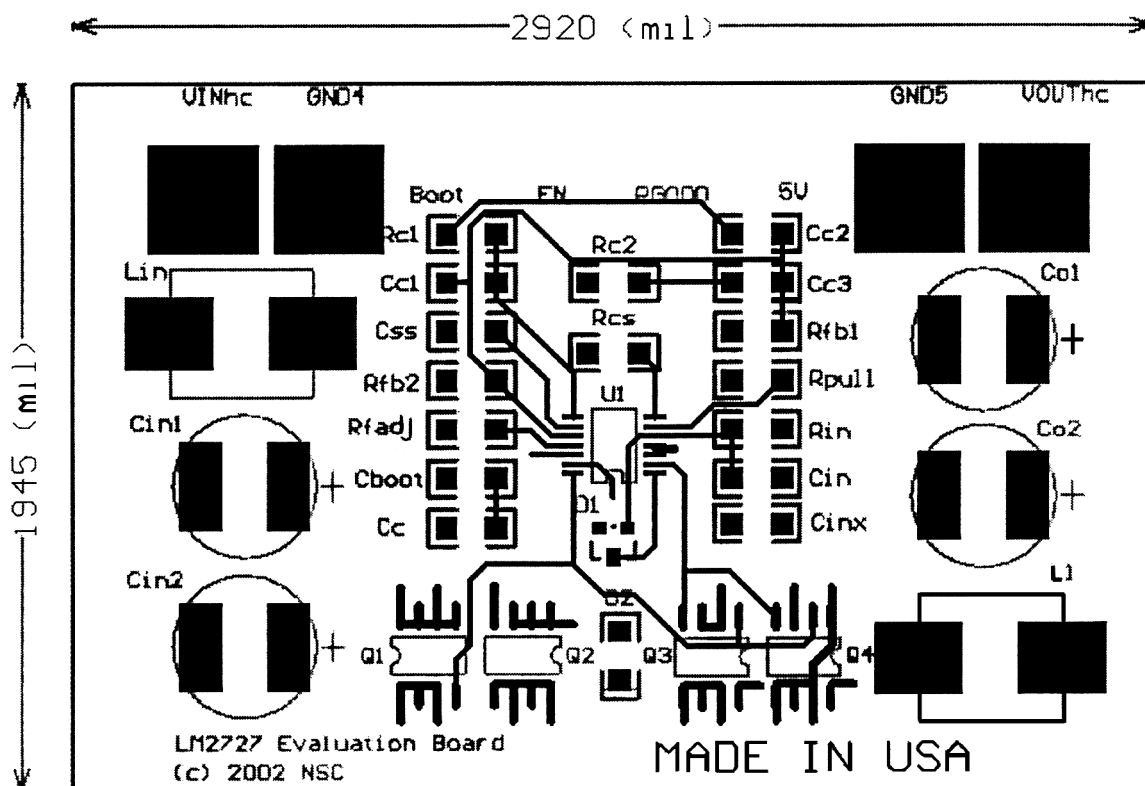


Figure 4. PCB Top Layer and Top Overlay

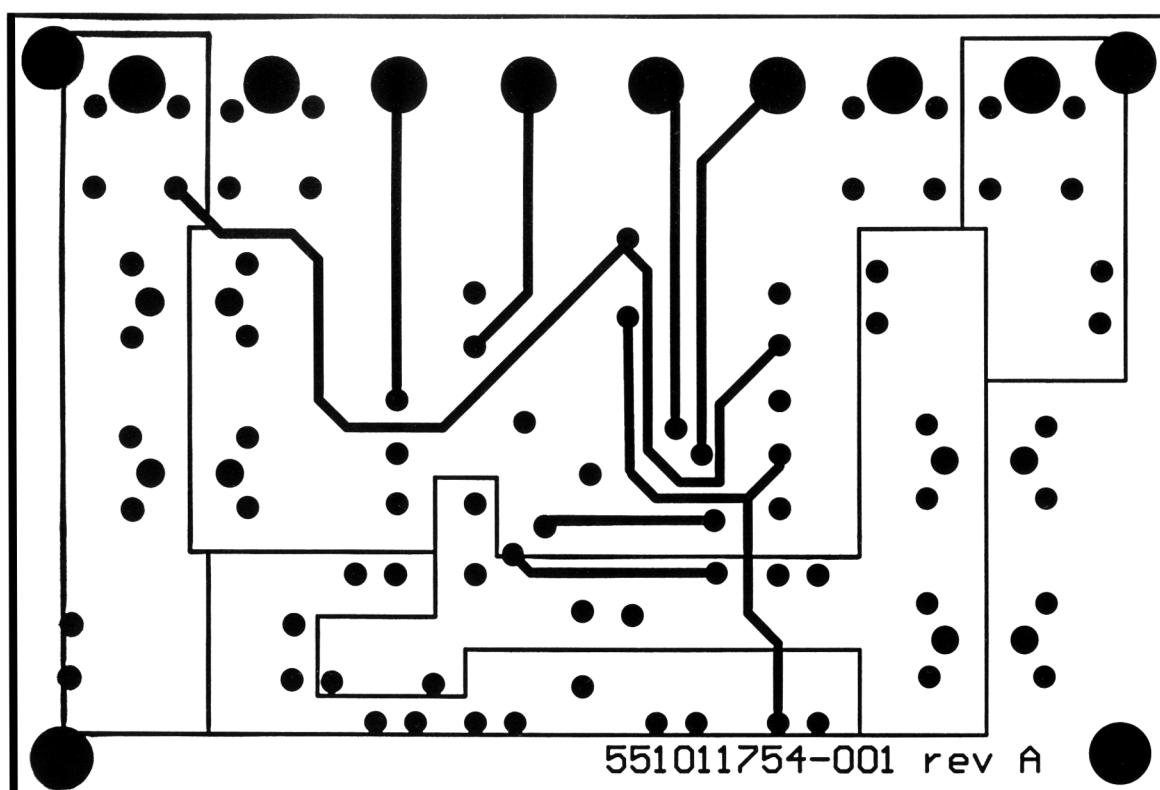


Figure 5. PCB Bottom Layer and Internal Power Plane

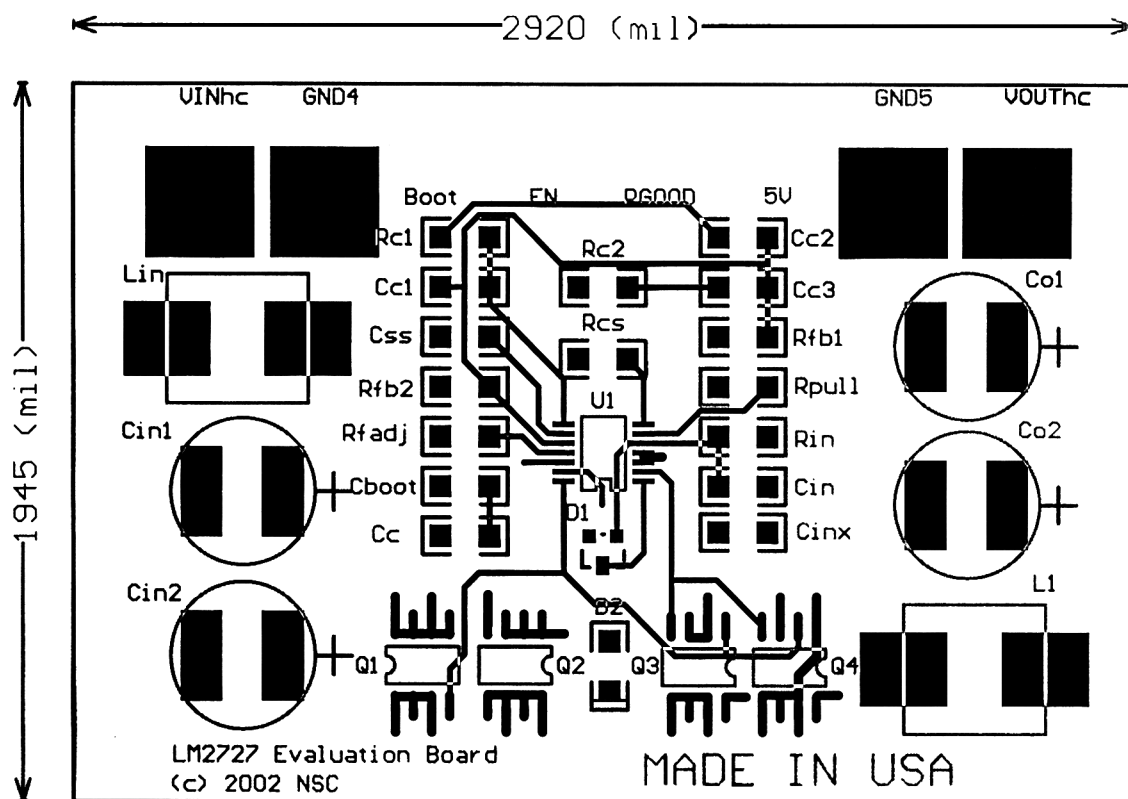


Figure 6. PCB Overall

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com