

Keywords: positive supply current, monitoring, load current, power supply, opamp, operational amplifiers, op amps

APPLICATION NOTE 69

Micropower Circuit Monitors Positive Supply Current

Jul 09, 1998

Abstract: The following application note shows a circuit that converts the load current of a positive power supply into a ground referenced signal voltage using the ICL7612 operational amplifier.

The inexpensive circuit of **Figure 1** converts the load current of a positive power supply to a ground-referenced signal voltage, without recourse to the instrumentation amplifier, extra power supply, and matched sets of resistors typical of such circuits. The output current I_O (proportional to supply current) flows through R_O to produce V_O . Because I_O is generated by a true current source, you can reference V_O to ground or to any reasonable level within the supply range. The measurement is independent of variations in the supply voltage.

Because the op amp's common-mode range includes the supply rails, it can sense small voltages near the positive rail, such as those across R_S . Feedback resistor R_F should equal $100R_S$ or $1000R_S$. The op amp drives P-channel MOSFET Q_1 , whose drain-source current produces a voltage across R_F equal to that across R_S , subject to an error of $\pm V_{OS}$. As a result,

$$I_O = (I_L R_S)(1/R_F) \text{ and,}$$
$$V_O = (I_L R_S)(R_O/R_F).$$

The component values shown provide a V_O range of 0 to 1V for the supply-current range 0 to 1A. You can add a trimming potentiometer to null V_{OS} . The remaining gain error depends on the tolerance of R_S , R_F or R_O . The op amp draws 20 μ A and operates with a voltage as low as 2.5V. This op amp supply is produced by the five diodes, which are biased by R_Z and the input supply voltage as shown in the table.

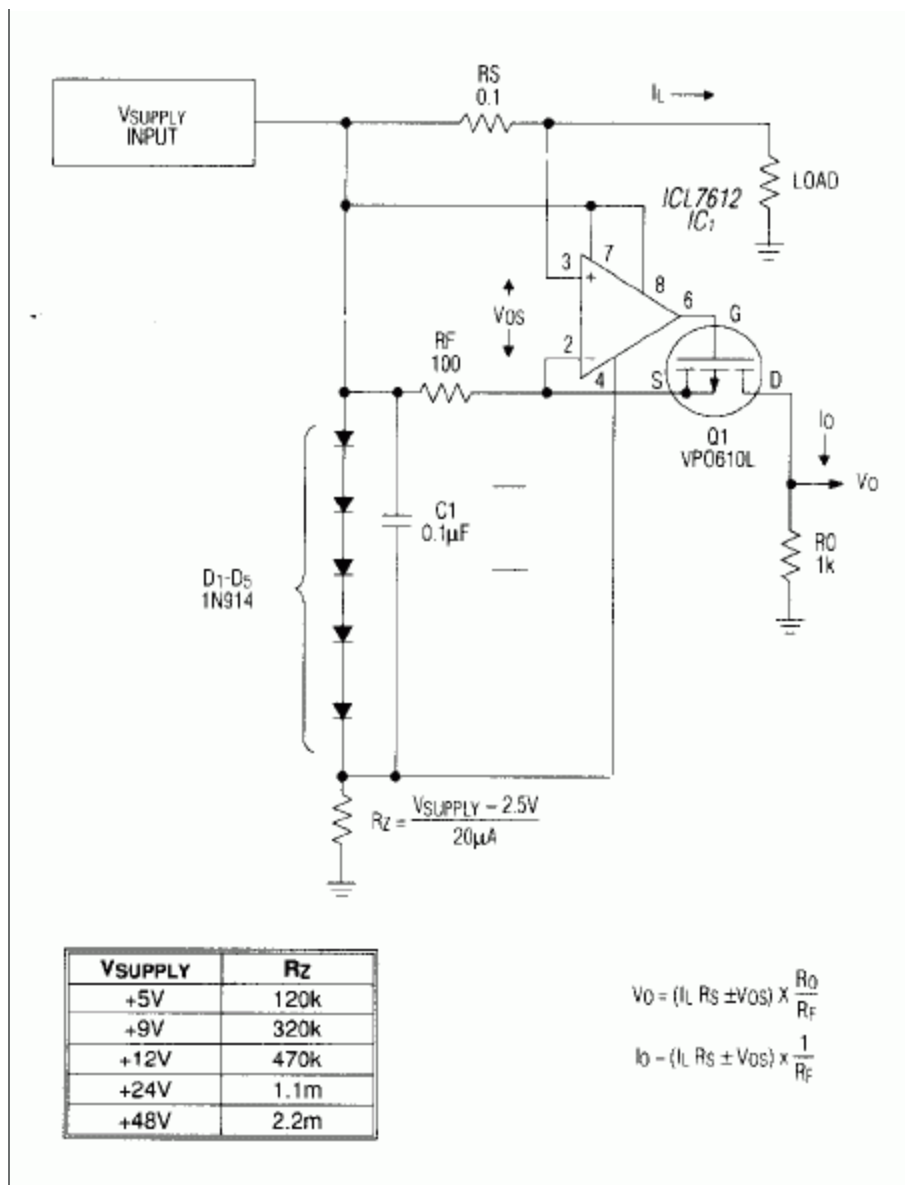


Figure 1. This simple load-current monitor produces a proportional signal voltage V_O .

Related Parts

ICL7612

Single/Dual/Triple/Quad Operational Amplifiers

[Free Samples](#)

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 69: <http://www.maximintegrated.com/an69>

APPLICATION NOTE 69, AN69, AN 69, APP69, Appnote69, Appnote 69

Copyright © by Maxim Integrated Products
Additional Legal Notices: <http://www.maximintegrated.com/legal>