

AN-1996 LM3410X 190mA, LED Driver 6-Pin LLP Evaluation Board

1 Introduction

This evaluation board showcases the LM3410X as a boost LED driver. It is designed to drive four, on-board LEDs ($V_{OUT} = 11.4\text{ V}$) in series at an average LED current (I_{LED}) of 190mA. The circuit can accept an input voltage of 3.3 V-5.5 V. The switching frequency of the LM3410X converter is 1.6MHz allowing the use of small surface mount inductors and chip capacitors. This evaluation board also features the PWM capability of the LM3410 by enabling the user to apply a periodic pulse signal to the DIM terminal of varying duty cycle.

This is a 2-layer board using the bottom layer as a ground plane. A schematic and layout are shown below along with measured performance characteristics. A bill of materials is also provided that describes the parts used on this evaluation board. The above restrictions for the input voltage are valid only for the evaluation board as shipped with the evaluation board schematic shown in [Figure 1](#).

Operating Conditions:

- $V_{IN} = 3.3\text{ V to }5.5\text{ V}$
- $V_{OUT} \approx V_F \times 4 + V_{FB} \approx 2.8\text{ V} \times 4 + 0.190\text{ V} \approx 11.4\text{ V}$
- $I_{LED} \approx 190\text{ mA}$

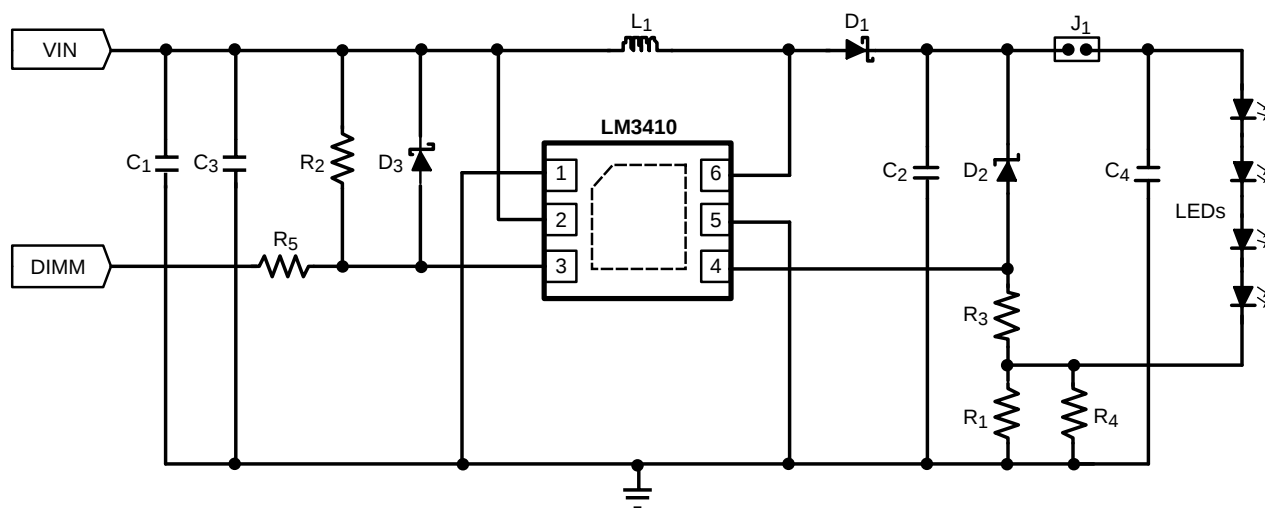


Figure 1. Schematic

Table 1. Pin Descriptions

Pin	Name	Function
1	PGND	Power ground pin. Place PGND and output capacitor GND close together.
2	V _{IN}	Supply voltage for power stage, and input supply voltage.
3	DIM	Dimming & shutdown control input. Logic high enables operation. Duty Cycle from 0 to 100%. Do not allow this pin to float or be greater than V _{IN} + 0.3 V.
4	FB	Feedback pin. Connect FB to external resistor divider to set output voltage.
5	AGND	Signal ground pin. Place the bottom resistor of the feedback network as close as possible to this pin & pin 4.
6	SW	Output switch. Connect to the inductor, output diode.
DAP	GND	Signal & Power ground. Connect to pin 1 and pin 5 on top layer. Place 4-6 vias from DAP to bottom layer GND plane.

Table 2. Bill of Materials

Part ID	Part Value	Manufacturer	Part Number
U1	2.8A I _{SW} LED Driver	TI	LM3410X
C1, Input Cap	10μF, 6.3 V, X5R	TDK	C2012X5R0J106M
C2, Output Cap	2.2μF, 25 V, X7R	TDK	C3225X7R1E225K
C3, Input Cap	Placeholder (not stuffed)	-	-
C4, Output Cap	4.7μF, 25 V, X7R	TDK	C3225X7R1E475K
D1, Catch Diode	0.4 V _f Schottky, 500mA	ON Semiconductor	MBR0530T1G
D2	15 V Zener Diode	Central Semiconductor	CMHZ4702
D3	0.4 V _f Schottky, 500mA	ON Semiconductor	MBR0530T1G
L1	3.3μH, 5.4A	Coilcraft	DO3316P-332
R1	1Ω, 1%	Vishay	CRCW12061R00FNEA
R2	Placeholder (not stuffed)	-	-
R3	100Ω, 1%	Vishay	CRCW0603100RFKEA
R4	Placeholder (not stuffed)	-	-
R5	6.8kΩ, 1%	Vishay	CRCW08056K80FKEA
J1	Jumper	Samtec	TSW-102-07-T-S
SH-J1	Jumper shunt	Tyco Electronics	2-382811-1
LEDs	700mA, V _f ≈ 3.4 V	Cree	XPEWHT-L1-0000-008E5

2 Setting the LED Current

The default forward current I_{LED} delivered to the LED array is 190mA. To adjust this value, the current setting resistors R1 and R4 can be changed according to the following equation:

$$I_{LED} = (V_{FB}) / (R1 \parallel R4)$$

The feedback voltage V_{FB} is regulated at 0.190 V typically. The resistors R1 and R4 should be rated to handle the power dissipation of the LED current.

3 PWM Dimming

The default set-up of the DIM terminal is to enable PWM dimming. If PWM dimming is not required, then the DIM pin can be tied to V_{IN} through a resistor, R2, using the existing 0805 sized resistor footprint. This enables the LM3410 whenever V_{IN} is applied and allows the set I_{LED} current to flow through the LEDs continuously. A recommended value for R2 is 100kΩ.

A periodic pulse signal at different frequencies and/or duty cycle can be applied to the evaluation board's DIM terminal for PWM dimming. The voltage measured at the DIM package lead must not be higher than 0.3 V above V_{IN} for proper operation. Diode D3 and resistor R5 have been placed in the circuit to clamp the signal at the DIM lead to no greater than 0.3 V above V_{IN}. Although not recommended, a PWM signal can therefore be applied to the evaluation board DIM terminal with a peak voltage greater than V_{IN}.

4 Over-Voltage Protection

The evaluation board includes over-voltage protection (OVP) circuitry, in the combination of zener diode D4 and resistor R3, to protect the LM3410 device in a situation where the output load is suddenly removed from the rest of the converter (i.e. an LED goes open). A header (J1) on the board allows the user to activate the OVP function by removing the associated jumper. The switching voltage at the SW pin will then be clamped to approximately the zener diode voltage of 18 V. Current will then flow through D4, R3 and sense resistor R1. This generates a voltage greater than 0.190 V at the FB pin that forces the LM3410's internal switching power FET to turn off, thereby, preventing an over-voltage condition at the SW pin and damaging the LM3410.

5 Typical Performance Characteristics

$T_A = +25^\circ\text{C}$, $V_{\text{OUT}} = 11.4\text{ V}$, unless otherwise specified.

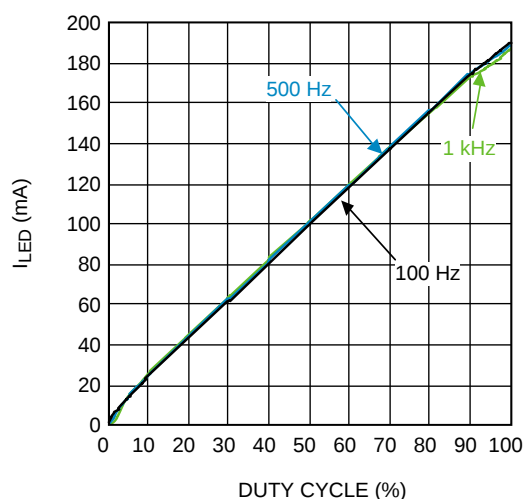


Figure 2. PWM Dimming, $V_{\text{IN}} = 3.3\text{ V}$

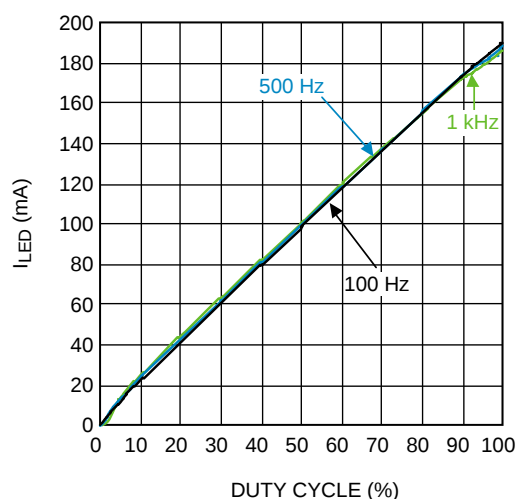


Figure 3. PWM Dimming, $V_{\text{IN}} = 5.5\text{ V}$

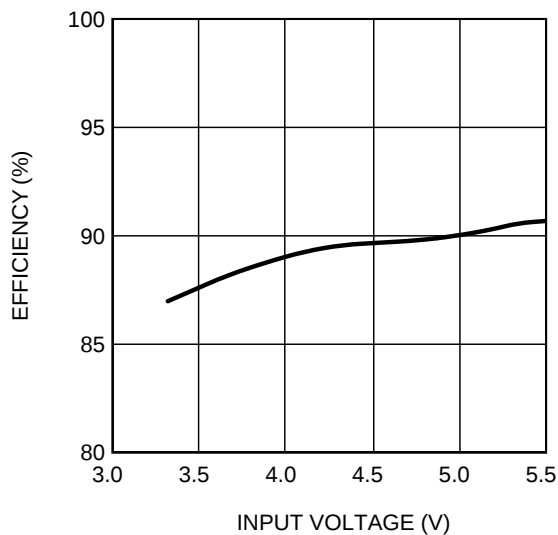


Figure 4. Efficiency vs. Input Voltage,
 $I_{LED} = 190 \text{ mA}$

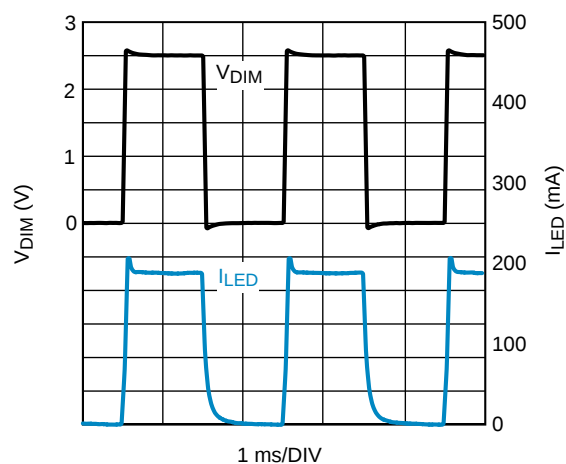


Figure 5. 500Hz PWM Dimming,
50% Duty Cycle, $V_{IN} = 3.3 \text{ V}$

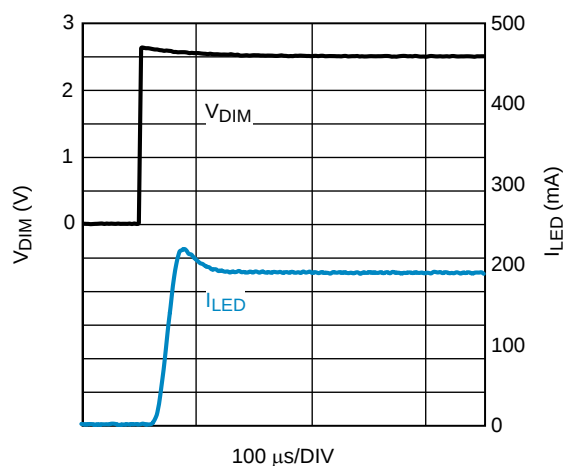


Figure 6. 500Hz PWM Dimming (Rising Edge),
50% Duty Cycle, $V_{IN} = 3.3 \text{ V}$

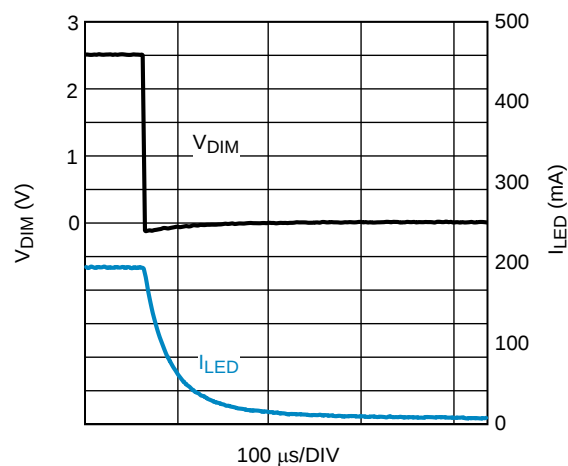


Figure 7. 500Hz PWM Dimming (Falling Edge)
50% Duty Cycle, $V_{IN} = 3.3 \text{ V}$

6 Two Power Supply Design with $12\text{ V} > V_{PWR} > 5.5\text{ V}$

The evaluation board can be modified to allow the user to derive the power from an input supply that is larger than 5.5 V. In Figure 8, two separate supplies are needed. V_{IN} must be between 3.3 V minimum to 5.5 V maximum, but V_{PWR} can be as great as 12 V. The recommended power-up sequence is V_{IN} then V_{PWR} . Power-down should be in the reverse order.

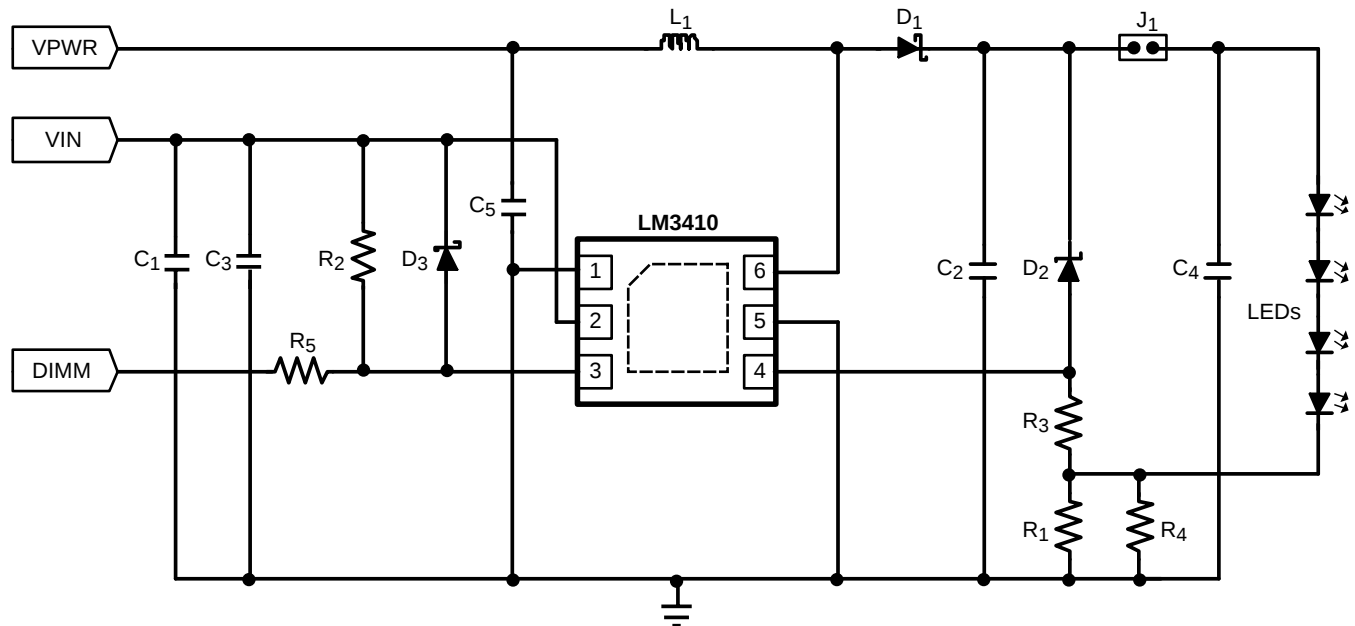


Figure 8. Two Power Supply Schematic

Table 3. Bill of Materials (BOM) - Two Power Supply Design

Part ID	Part Value	Manufacturer	Part Number
U1	2.8A I_{SW} LED Driver	TI	LM3410X
C1, V_{IN} , Input Cap	10 μ F, 6.3 V, X5R	TDK	C2012X5R0J106M
C2, Output Cap	2.2 μ F, 25 V, X7R	TDK	C3225X7R1E225K
C3, Input Cap	Placeholder (not stuffed)	-	-
C4, Output Cap	4.7 μ F, 25 V, X7R	TDK	C3225X7R1E475K
C5, V_{PWR} , Input Cap	10 μ F, 25 V, X5R	TDK	C3225X5R1E106M
D1, Catch Diode	0.4 V _f Schottky, 500mA	ON Semiconductor	MBR0530T1G
D2	15 V Zener Diode	Central Semiconductor	CMHZ4702
D3	0.4 V _f Schottky, 500mA	ON Semiconductor	MBR0530T1G
L1	3.3 μ H, 5.4A	Coilcraft	DO3316P-332
R1	1 Ω , 1%	Vishay	CRCW12061R00FNEA
R2	Placeholder (not stuffed)	-	-
R3	100 Ω , 1%	Vishay	CRCW0603100RFKEA
R4	Placeholder (not stuffed)	-	-
R5	6.8k Ω , 1%	Vishay	CRCW08056K80FKEA
J1	Jumper	Samtec	TSW-102-07-T-S
SH-J1	Jumper shunt	Tyco Electronics	2-382811-1
LEDs	700mA, $V_f \approx 3.4\text{ V}$	Cree	XPEWHT-L1-0000-008E5

7 PCB Layout

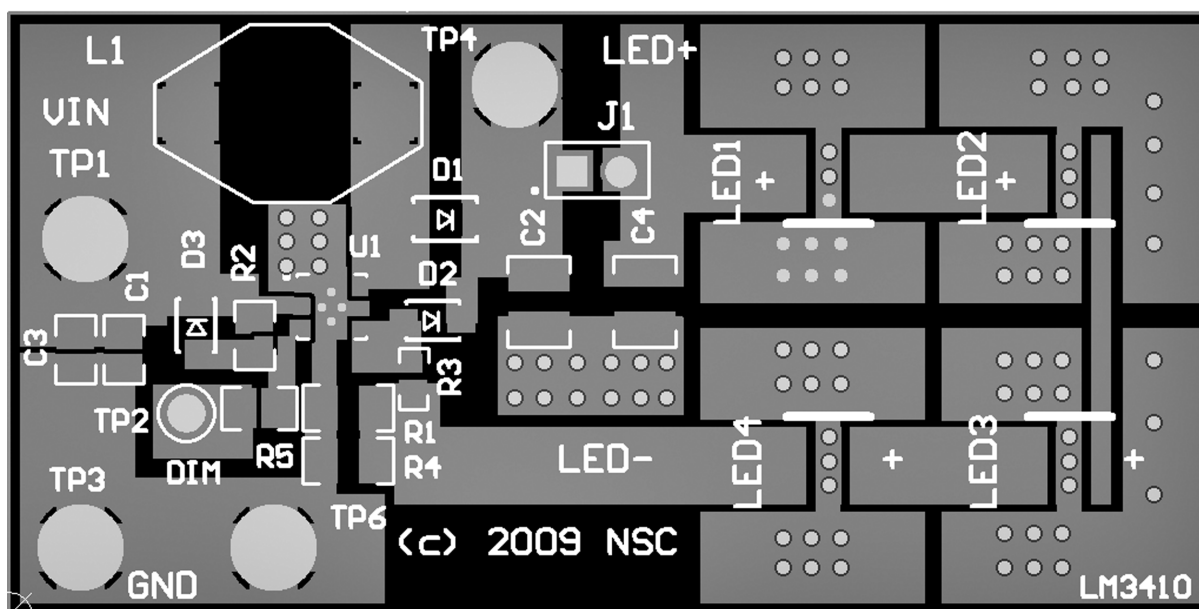


Figure 9. Top Layer

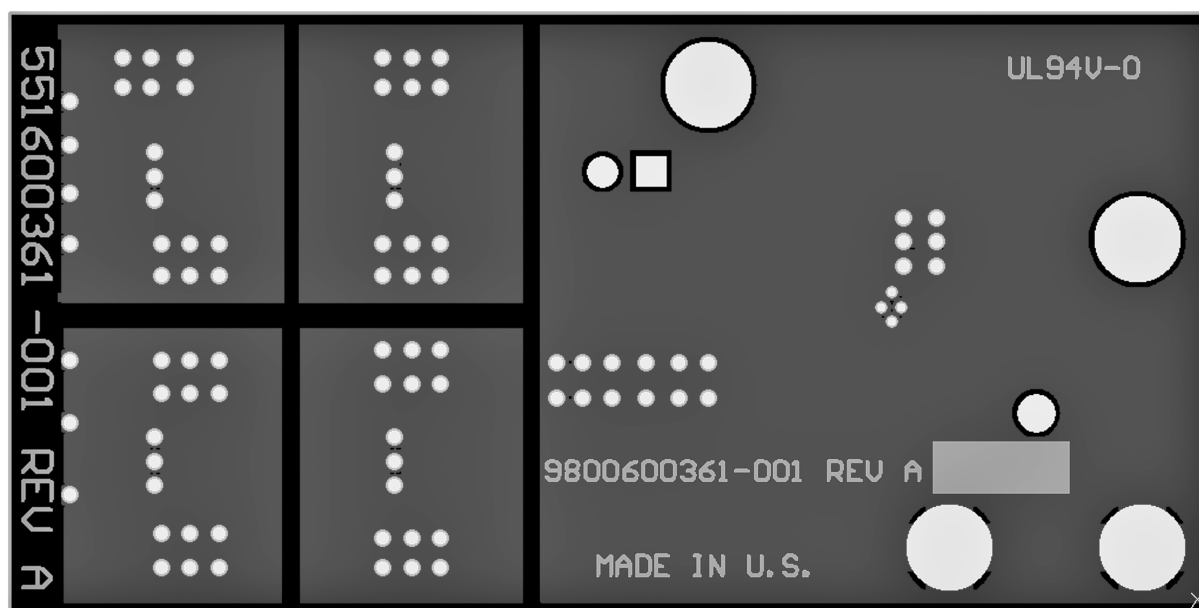


Figure 10. Bottom Layer

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com