

# Produce Negative Voltages Using the Buck Controller

Victor Khasiev  
Analog Devices, Inc.

## Introduction

Negative voltages are used to power an expanding number of LCD screens in automobile infotainment systems. Likewise, in industrial and railroad environments, negative rails satisfy the needs of instrumentation and monitoring applications. In all cases, the negative voltage rail must be produced from a positive source, but positive-to-negative ICs are not as readily available as buck controllers. Manufacturers are unlikely to have tested and qualified negative output converters, but probably already have a number of approved buck controllers, such as the [LTC3892](#) dual output controller. To avoid the extra time and cost of testing a dedicated negative output converter, the LTC3892 dual output buck controller can be used to produce a negative output voltage with a Ćuk topology.

## Dual Output Converter: -12 V at 3 A and 3.3 V at 10 A

The LTC3892 is a dual output controller, where one output can be used for a positive voltage and the other channel for a negative voltage, as shown in Figure 1. The input voltage range of this solution is 6 V to 40 V, with  $V_{OUT1}$  equal to 3.3 V at 10 A and  $V_{OUT2}$  equal to -12 V at 3 A.  $V_{OUT1}$  is configured as a straightforward buck converter topology with power train components Q2, Q3, L1, and the output filter capacitors. No voltage divider is required at the VFB pin (tied directly to the output) to set the output to 3.3 V, as the [LTC3892-2](#) features fixed 3.3 V or 5 V outputs set by the grounding or by tying VPRG1 to  $INTV_{CC}$ , respectively.

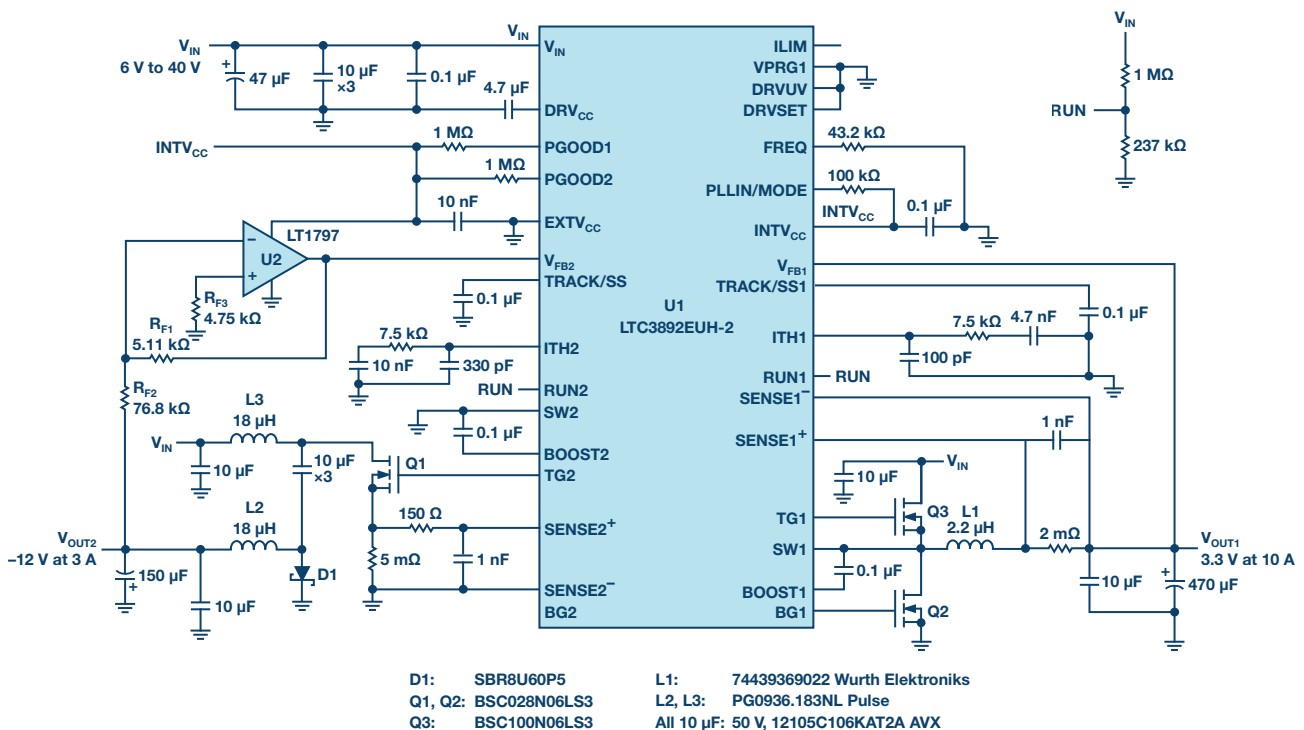


Figure 1. A solution for generating positive and negative voltages.  $V_{OUT1}$  is 3.3 V at 10 A and  $V_{OUT2}$  is -12 V at 3 A.

$V_{OUT2}$  is a negative output voltage relative to GND. The op amp U2 (LT1797) is wired as a differential amplifier that is employed to sense the negative voltage and scale it to the 0.8 V reference of the LTC3892 error amplifier (EA). In this approach, both the EA of the LTC3892 and the op amp are referenced to system GND, which simplifies power supply control and functionality. The seed formulas for setting the negative output voltage are:

$$KR = \frac{0.8 \text{ V}}{|V_0|}$$

$$R_{F1} = 5.11 \text{ k}\Omega$$

$$R_{F2} = \frac{R_{F1}}{KR}$$

$$R_{F3} = \frac{R_{F1} \times R_{F2}}{R_{F1} + R_{F2}}$$

The  $V_{OUT2}$  employs a nonsynchronous Ćuk topology and includes power train components of Q1, D1, L2, and output filter capacitors. The Ćuk topology is widely covered in other technical literature, so it is not covered at length here. The stress on the power train components can be summed up by:

$$D = \frac{|V_0|}{|V_0| + V_{IN}}$$

$$V_C = \frac{V_{IN}}{1 - D}$$

$$V_{DS} = V_D = V_C$$

$$I_{L2} = \frac{I_0 \times V_0}{V_{IN}} + \Delta I_{L2}$$

$$I_{L3} = I_0 + \Delta I_{L3}$$

A DC2727A demonstration board was used to evaluate this solution, with the  $V_{OUT2}$  efficiency shown in Figure 2. This approach is also available in our LTspice® simulation model of the LTC3892-2.

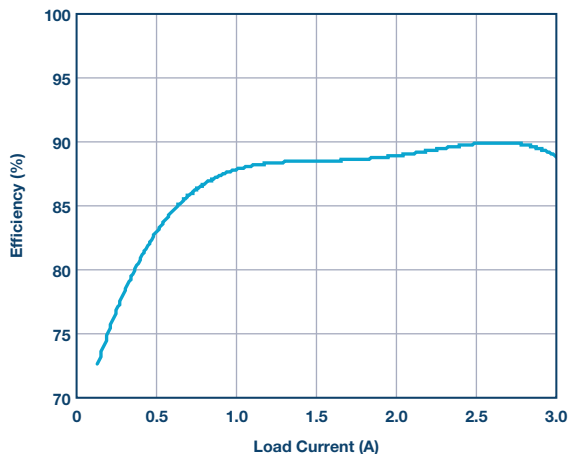


Figure 2. Efficiency for the negative output ( $V_{OUT2}$ ) at 14 V input.

## Conclusion

The LTC3892 is a versatile and flexible controller ostensibly designed for synchronous step-down conversion, but it can be used in a Ćuk topology to generate positive and negative voltages for automotive, industrial, and other applications.

## About the Author

Victor Khasiev is a senior applications engineer at Analog Devices. Victor has extensive experience in power electronics both in ac-to-dc and dc-to-dc conversion. He holds two patents and wrote multiple articles. These articles relate to the use of ADI semiconductors in automotive and industrial applications. They cover step-up, step-down, SEPIC, positive-to-negative, negative-to-negative, flyback, and forward converters, as well as bidirectional backup supplies. His patents are about efficient power factor correction solutions and advanced gate drivers. Victor enjoys supporting ADI customers: answering questions about ADI products, design and verification power supplies schematics, layout of the print circuit boards, troubleshooting, and participating in testing final systems. He can be reached at [victor.khasiev@analog.com](mailto:victor.khasiev@analog.com).

## Online Support Community



Engage with the Analog Devices technology experts in our online support community. Ask your tough design questions, browse FAQs, or join a conversation.

Visit [ez.analog.com](http://ez.analog.com)

### Analog Devices, Inc. Worldwide Headquarters

Analog Devices, Inc.  
One Technology Way  
P.O. Box 9106  
Norwood, MA 02062-9106  
U.S.A.  
Tel: 781.329.4700  
(800.262.5643, U.S.A. only)  
Fax: 781.461.3113

### Analog Devices, Inc. Europe Headquarters

Analog Devices GmbH  
Ott-Aicher-Str. 60-64  
80807 München  
Germany  
Tel: 49.89.76903.0  
Fax: 49.89.76903.157

### Analog Devices, Inc. Japan Headquarters

Analog Devices, KK  
New Pier Takeshiba  
South Tower Building  
1-16-1 Kaigan, Minato-ku,  
Tokyo, 105-6891  
Japan  
Tel: 813.5402.8200  
Fax: 813.5402.1064

### Analog Devices, Inc. Asia Pacific Headquarters

Analog Devices  
5F, Sandhill Plaza  
2290 Zuchongzhi Road  
Zhangjiang Hi-Tech Park  
Pudong New District  
Shanghai, China 201203  
Tel: 86.21.2320.8000  
Fax: 86.21.2320.8222

©2019 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners. Ahead of What's Possible is a trademark of Analog Devices.  
DN21065-0-1/19

[analog.com](http://analog.com)



AHEAD OF WHAT'S POSSIBLE™