

AN-1929 LM27342 Demonstration Board

1 Introduction

The LM27342 demonstration board is designed to provide the power supply design engineer with a fully functional regulator design, which can be synchronized to an external clock between 1000 kHz and 2350 kHz. The evaluation board provides a 3.3V output with a 2A current capability. The wide input voltage ranges from 5V to 20V. Without an external synchronization signal, the design operates at 2000 kHz reducing the solution size and keeping switching noise out of the AM radio band. The printed circuit board (PCB) consists of four layers of copper on FR4 material. There is a ground plane on the internal layer directly beneath the LM27342, and a ground plane on the bottom layer. The LM27342 is thermally tied to the ground planes by thermal vias directly underneath the device. The second internal layer is tied half to V_{IN} and half to V_{OUT} . This application report contains the evaluation board schematic, a quick setup procedure, and a Bill-of-Materials (BOM). For complete circuit design information, see the *LM27341/LM27342/LM27341Q/LM27342Q 2 MHz 1.5A/2A Wide Input Range Step-Down DCDC Regulator with Frequency Synchronization* ([SNVS497](#)) data sheet.

The performance of the evaluation board is as follows:

Input Range: 5 to 20V


Output Voltage: 3.3V

Output Current: 0 to 2A

Frequency of Operation: 1000 kHz - 2350 kHz

Board Size: 1.1 X 1.3 inches

2 Evaluation Board Schematic

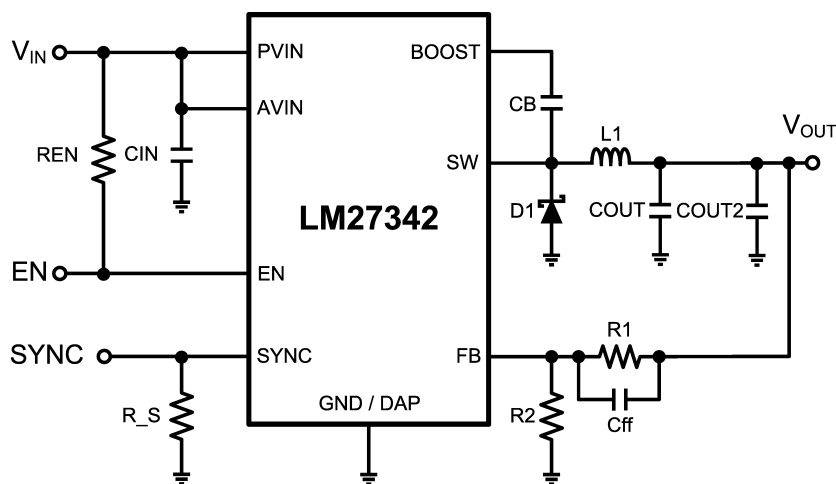

3 Powering and Loading Considerations

Read this entire page prior to attempting to power the evaluation board.

3.1 Quick Start Procedure

1. Set the bench power supply current limit to 2A. Set the power supply voltage to 12V. Turn off the power supply output. Connect the power supply to the LM27342 demo board. Positive connection to V_{IN} and negative connection to GND.
2. Connect a load, as high as 2A, to the V_{OUT} terminal. Positive connection to V_{OUT} and negative connection to GND.
3. Connect a signal generator to provide a synchronization signal to the SYNC terminal. Positive connection to SYNC and negative connection to GND.
4. The EN pin should be left open for normal operation.
5. Turn on the bench power supply with no load applied to the LM27342. V_{OUT} should be in regulation with a nominal 3.3V output.
6. Slowly increase the load while monitoring the output voltage, V_{OUT} should remain in regulation with a nominal 3.3V output as the load is increased up to 2 Amps
7. Slowly sweep the input voltage from 5 to 20V and back to 12V, V_{OUT} should remain in regulation with a nominal 3.3V output.
8. Turn on the signal generator, and synchronize the LM27342 to a 3.3V square wave at 1 MHz. V_{OUT} should remain in regulation with a nominal 3.3V output. Monitor SYNC and SW to observe the synchronization behavior.

3.1.1 Starting Up

The EN pin is tied to V_{IN} to simplify start-up. The pull-up resistor allows the power supply design engineer to toggle EN independently, if desired, and observe the start-up behavior of the LM27342.

3.2 Over Current Protection

The evaluation board is configured with over-current protection. The inductor current is limited to 4.0A (max).

3.3 Synchronization

A SYNC pin has been provided on the evaluation board. This pin can be used to synchronize the regulator to an external clock or multiple evaluation boards can be synchronized together by connecting their SYNC pins together. Refer to the LM27342 datasheet for complete information

3.4 Adjusting the Output Voltage

The output voltage is set using the following equation where R2 is connected between the FB pin and GND, and R1 is connected between V_{OUT} and FB.

$$R1 = \left(\frac{V_{OUT}}{V_{REF}} - 1 \right) \times R2 \quad (1)$$

Adjusting the output voltage will affect the performance of the LM27342. In addition, output capacitors might not be rated for the new output voltage. Refer to the LM27342 datasheet for more information.

4 Performance Characteristics

Efficiency Plots

Figure 1 shows the conversion efficiency versus output current for several input voltage conditions.


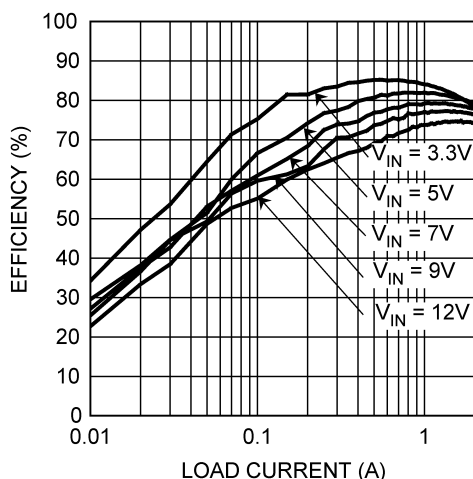


Figure 1. Conversion Efficiency Versus Output Current

Turn-on Waveform

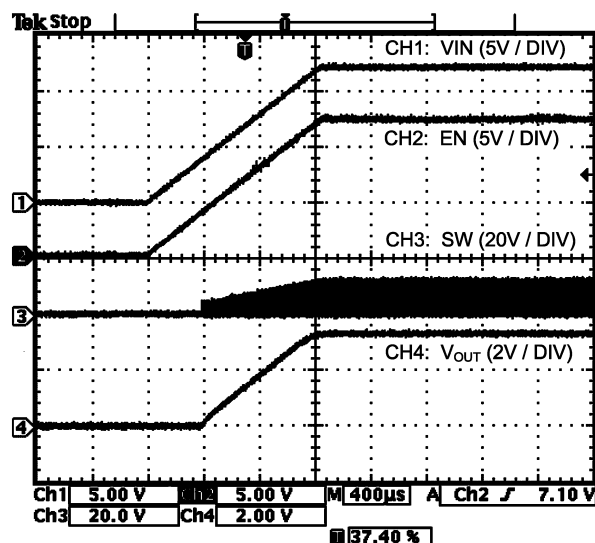When applying power to the LM27342 evaluation board a soft-start sequence occurs. Figure 2 shows the output voltage during a typical start-up sequence.



Output Current = 1A

Figure 2. Output Voltage During a Typical Start-Up Sequence

5 Layout and Bill of Materials

The Bill of Materials is shown in [Table 1](#), including the manufacturer and part number.

Table 1. Bill of Materials

Part Name	Part ID	Part Value	Part Number	Manufacturer
Buck Regulator	U1	2A Buck Regulator	LM27342	Texas Instruments
C _{IN}	CIN	10 μ F	TMK325B7106MM-T	Taiyo Yuden
C _{BOOST}	CB	0.1 μ F	C0603C104K8RACTU	Kemet
C _{OUT}	COU1	22 μ F	GRM32ER71A226KE20L	Murata
C _{OUT2}	COU2	22 μ F	GRM32ER71A226KE20L	Murata
Catch Diode	D1	Schottky Diode Vf = 0.32V	CMS06	Toshiba
Inductor	L1	2.7 μ H	CDRH5D18BHPNP-2R7M	Sumida
Feedback Resistor	R1	430 Ω	MCR03EZPFX4300	Rohm
Feedback Resistor	R2	187 Ω	MCR03EZPFX1870	Rohm
Pull-up Resistor	REN	4.7 k Ω	MCR03EZPFX4701	Rohm
Pull-down Resistor	R_S	4.7 k Ω	MCR03EZPFX4701	Rohm
Connectors	VIN, GND, GND, VOUT, EN, SYNC	Turret	160-2043-02-01-00	Cambion
Test Point	SW	Miniature Test Point	5000	Keystone

6 PCB Layout

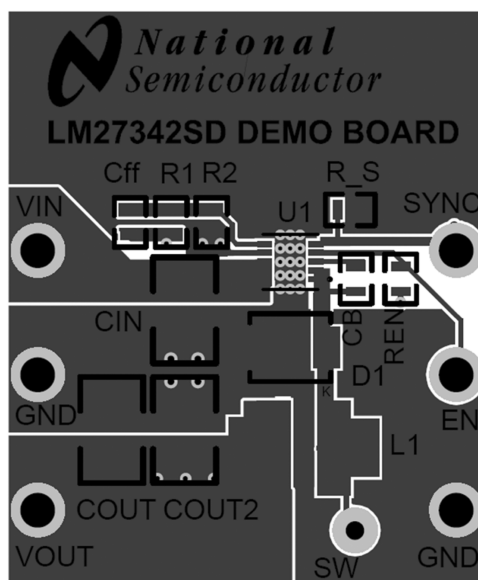


Figure 3. Top Layer and Overlay

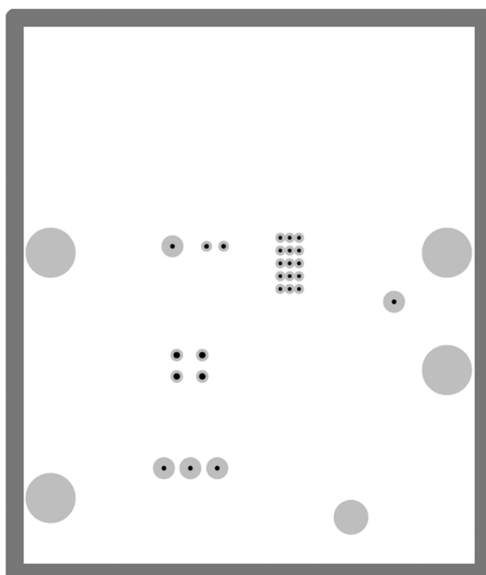


Figure 4. Internal Layer 1

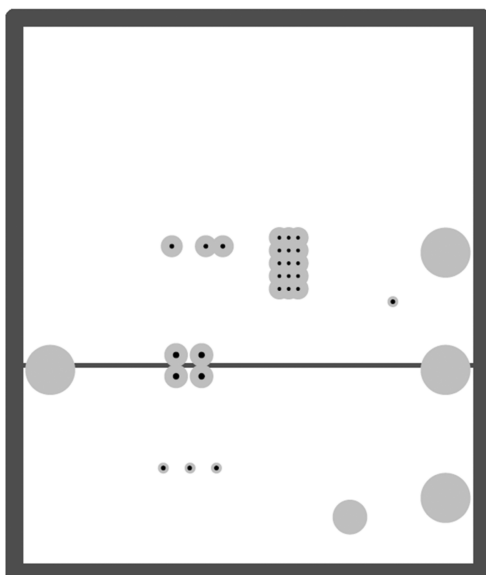


Figure 5. Internal Layer 2

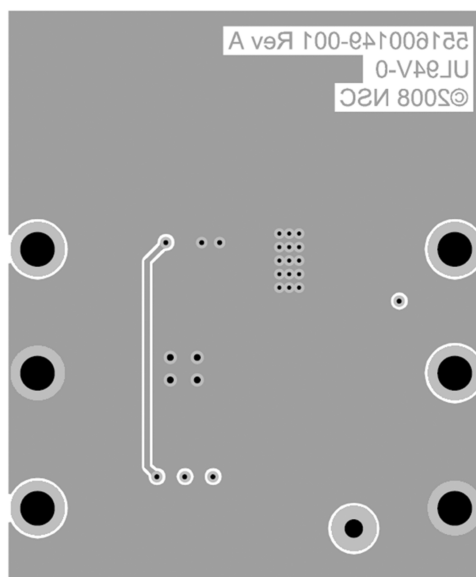


Figure 6. Bottom Layer

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com