

# Brushless-DC Made Simple – Sensored Motor Control

Matt Hein, Analog Motor Drive



## Introduction

Brushless-DC (BLDC) motors remain an important and fast-growing motor type with many performance benefits over brushed-DC (BDC) and stepper motors. BLDC motors are more efficient, higher power, higher torque, quieter, longer lifetime, and higher speed compared to their BDC counterparts. Today, we see many different products that specifically advertise themselves as having “brushless” technology. Being able to keep up with the market trends is important in order to design a product that is relevant and successful on the market. Some examples of these products are cordless power & garden tools, cordless vacuums, drones & remote-control toys, fans & air purifiers, and automated window blinds.

However, the difficulty of implementing a BLDC motor in a customer system remains a large barrier to entry for many product design teams, especially when comparing the complexity of BLDC control versus a BDC motor. This even applies to systems using sensored trapezoidal control which will be the main topic of this document.

## Brushed-DC Systems

If we look at a typical medium-power brushed-DC motor system, we have four external MOSFETs and an associated H-bridge gate driver (e.g. [DRV8701](#)). A low-dropout regulator (LDO) generates 3.3V from the main motor supply for the microcontroller (MCU) and Hall-effect sensor (the LDO may be integrated into the gate driver). The system MCU takes inputs (buttons, commands, etc) and controls the motor using two output, a direction signal (clockwise or counterclockwise spinning) and a PWM signal (0% to 100% duty cycle at a fixed frequency). The Hall-effect sensor is used for motor speed feedback to the MCU.

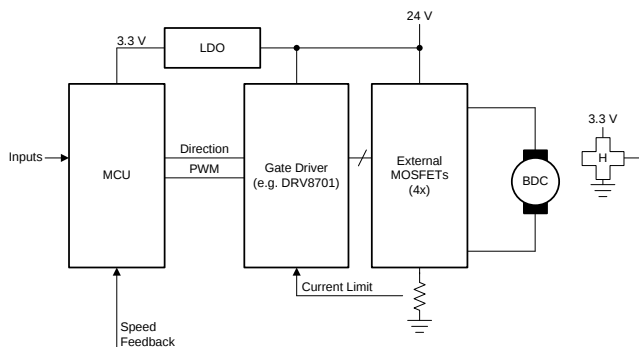


Figure 1. Brushed-DC motor system

The control loop used in such a system can be either a speed control loop or a position/servo control loop. The Hall-effect sensor output frequency is directly proportional to the motor speed and is used to close the speed control loop. If we apply an integrator/accumulator to the Hall-effect sensor signal, we can determine the motor position and perform a position control loop.

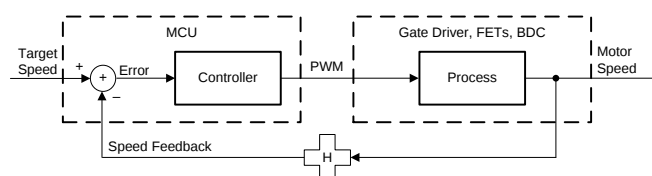


Figure 2. Brushed-DC motor speed control loop

## Traditional Brushless-DC Systems

Looking at a similar BLDC system, we can understand why engineers would be concerned about the complexity of implementing a brushless-DC motor in the same way. The traditional solution for BLDC control involves three  $\frac{1}{2}$  H-bridge gate drivers and six external MOSFETs. These gate drivers feature a 6x PWM interface, such that each FET requires a controlling signal (six input signals in total). The brushless-DC motor requires electrical commutation, meaning that it is the system's responsibility to keep the motor spinning by energizing the phases in the correct sequence. For a sensored control scheme, three Hall-effect sensors are integrated in the motor to give position feedback. In some motors, the Hall-effect sensors are replaced by Hall elements, which have analog outputs and require additional comparators to implement proper feedback. As seen in [Figure 3](#), the MCU requirements increase dramatically in terms of inputs and output required compared to a brushed-DC motor scheme.

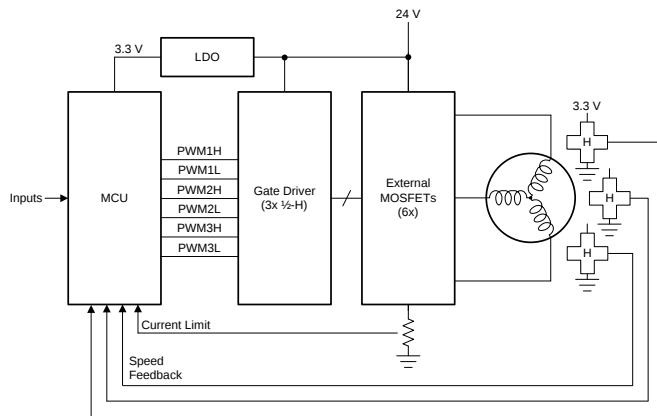


Figure 3. Traditional brushless-DC motor system

### Simplified Brushless-DC Systems

In order to “simplify” the brushless-DC system, let’s examine [DRV8306](#), a three-phase Smart Gate Driver. This device integrates a six-step (trapezoidal) commutation table in order for the [DRV8306](#) to control the brushless-DC motor commutation. This offloads processing requirements from the MCU, as well as reduces the number of GPIOs required on the MCU. The integration of the commutation table allows the [DRV8306](#) device to implement a BLDC design as simple as a brushed-DC motor system: a direction and PWM command. The [DRV8306](#) also integrates Hall element comparators, which allow it to be used with either Hall-effect sensors or Hall elements without additional comparators or circuits. All three Hall signals are combined in the [DRV8306](#) to send one speed feedback signal to the MCU.

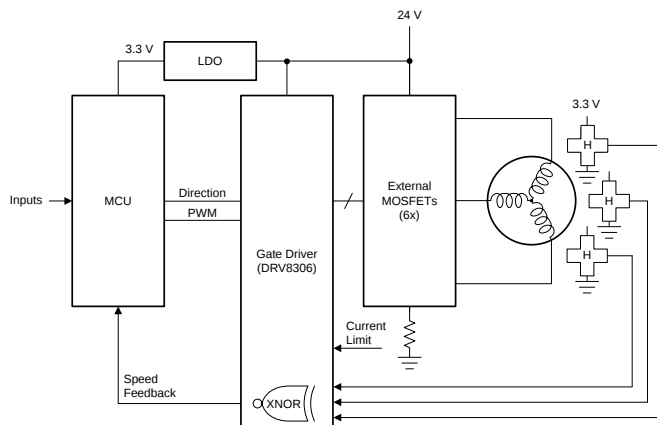


Figure 4. Simplified brushless-DC motor system

We see in [Figure 5](#) that the control loop is similar to that of a brushed-DC motor once the motor commutation is handled by the gate driver.

This allows for a system with reduced complexity and simple control. The motor control requirements from the MCU are identical between the brushed-DC Motor system example given earlier and this simplified brushless-DC motor example.

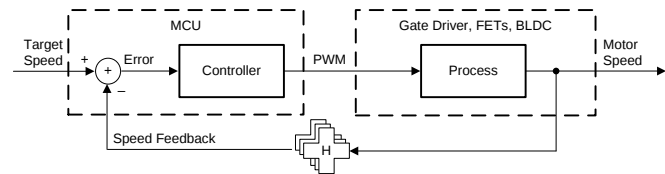


Figure 5. Simplified brushless-DC motor speed control loop

### Conclusion

Design complexity is cited as a common reason for not implementing brushless-DC motors in products, and while this is true for the traditional brushless-DC system, devices like [DRV8306](#) allow brushless-DC motor control to be simplified so that the control complexity is similar to a brushed-DC system.

### Device Recommendation

The [DRV8306](#) is not the only device that can execute trapezoidal control of a sensed motor, other devices may be selected based on the necessary system requirement; however the [DRV8306](#) can support Hall element inputs while other devices only support Hall-effect sensors without external comparators (in 1x PWM mode).

Table 1. Alternative Device Recommendations

| Device                  | Optimized Parameters                                                                  | Performance Trade-Off                                      |
|-------------------------|---------------------------------------------------------------------------------------|------------------------------------------------------------|
| <a href="#">DRV8304</a> | 40-V abs max voltage<br>150mA / 300 mA (Source / Sink)<br>3x Current Sense Amplifiers | No Hall element comparators                                |
| <a href="#">DRV8320</a> | 65-V abs max voltage<br>1 A / 2 A (Source / Sink)                                     | No Hall element comparators<br>No current sense amplifiers |
| <a href="#">DRV8350</a> | 100-V abs max voltage<br>1 A / 2 A (Source / Sink)                                    | No Hall element comparators<br>No current sense amplifiers |
| <a href="#">DRV8323</a> | 65-V abs max voltage<br>1 A / 2 A (Source / Sink)<br>3x Current Sense Amplifiers      | No Hall element comparators                                |
| <a href="#">DRV8353</a> | 100-V abs max voltage<br>1 A / 2 A (Source / Sink)<br>3x Current Sense Amplifiers     | No Hall element comparators                                |

Table 2. Adjacent Tech Notes

|                         |                                                                                                          |
|-------------------------|----------------------------------------------------------------------------------------------------------|
| <a href="#">SLVA960</a> | <i>Reduce Motor Drive BOM and PCB Area with TI Smart Gate Drive</i>                                      |
| <a href="#">SLVA939</a> | <i>Field Oriented Control (FOC) Made Easy for Brushless DC (BLDC) Motors Using TI Smart Gate Drivers</i> |

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated