

AN-1343 LM2852 Evaluation Board (500kHz version)

1 Introduction

In this evaluation board for the LM2852Y, three output voltage options are available and all three come with the same bill of materials. The board may be configured in multiple ways providing various enabling schemes, split-rail operation and filtering options. The LM2852 is a 2A step-down buck converter belonging to TI's SIMPLE SYNCHRONOUS® family. The LM2852 input voltage can range from 2.85V to 5.5V. Output voltages are factory set from 0.8V to 3.3V in 100mV increments. On-chip type-three compensation facilitates low component count power supply design. This evaluation board enables the power supply designer to investigate various functional configurations.

2 PVIN and AVIN

The input voltage to the LM2852 is connected to two PVIN pins and an AVIN pin. PVIN is the supply connected to the output power switches; AVIN powers the controller logic of the switcher. Since PVIN and AVIN are dedicated pins on the chip, split rail operation is possible. For example, AVIN can be set to 5V and PVIN to 3.3V. Jumper J₁ on the evaluation board is used to short together the AVIN and PVIN board inputs.

3 Enable (EN)

The LM2852 enable pin is internally pulled up so that the part is enabled anytime the input voltage exceeds the UVLO threshold. The evaluation board includes an input for enable so the user may set the voltage on the enable pin. Jumper J2 also may be used to short the enable pin to AVin. Resistor, R_p may be used as a pull down resistor to set the enable input to low.

4 C_f and R_f

Components C_f and R_f may be used to low-pass-filter the AVIN input. Filtering AVIN may improve line and load regulation by reducing interfering signals on AVIN. 10 Ω and 1 μF are typical filter components for AVIN.

5 C_{IN} and C_{INX}

This evaluation board provides two capacitor footprints for the C_{IN} function. The larger footprint holds the bulk of the C_{IN} capacitor, for example 47 μF. Additional high frequency filtering may also be accomplished by adding a smaller capacitor – C_{INX}. A 1 μF or 100 nF capacitor is commonly used for high frequency filtering.

6 C_{SS}

The soft-start capacitor is used to control the start up behavior of the switching regulator. A 2.7 nF capacitor yields approximately a 3 ms start up time.

7 Output Filter - L₁, C_{O1} and C_{O2}

Since the LM2852 uses on-chip compensation, the output filter component values must be restricted to a certain range. The data sheet includes a table and information on component selection. Generally, the output capacitors must have ESR values commonly found in Tantalum and non-Tantalum solution, Niobium Oxide capacitors.

All trademarks are the property of their respective owners.

8 Board Schematic

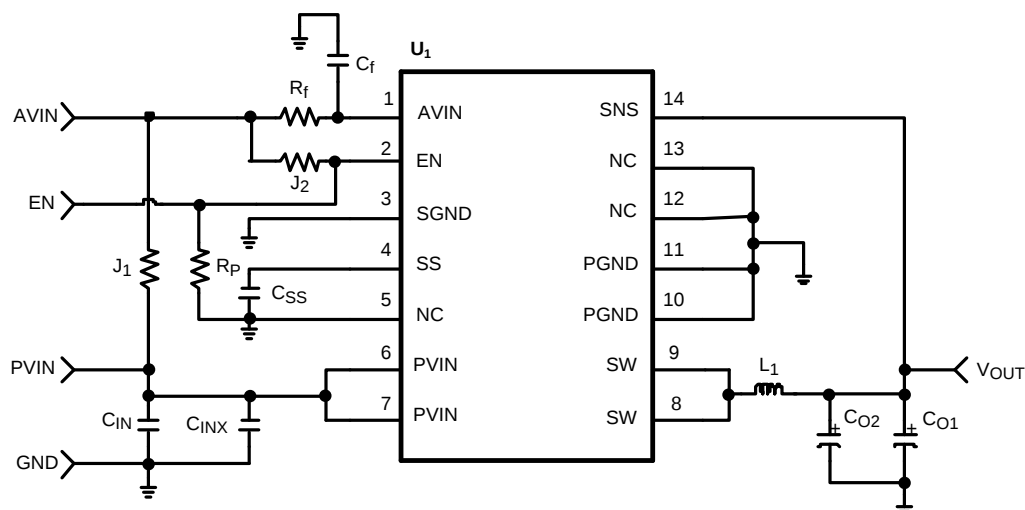


Table 1. Bill of Materials

ID	Part Number	Type	Size	Parameters	Qty	Vendor
U ₁	LM2852, LM2852 or LM2852	2A Buck	HTSSOP-14		1	TI
L ₁	DO3316P-153	Inductor		15 μ H	1	Coilcraft
C _{O1}	NOSD107M006R0100	Capacitor		100 μ F	1	AVX
C _{O2}	Not Populated				0	
C _{IN}	GRM32ER60J476ME20B	Capacitor	1210	47 μ F/X5R/6.3V	1	Murata
C _{INX}	GRM21BR71C105KA01B	Capacitor	0805	1 μ F/X7R/16V	1	Murata
C _{SS}	VJ0805Y272KXXA	Capacitor	0805	2.7nF/X7R/25V	1	Vishay-Vitramon
R _f	CRCW060310R0F	Resistor	0603	10 Ω $\pm$ 10%	1	Vishay-Dale
C _f	GRM21BR71C105KA01B	Capacitor	0805	1 μ F/X7R/16V	1	Murata
J ₁	CRCW06030R0F	Resistor	0603	0 Ω	1	Vishay-Dale
J ₂	Not Populated				0	
R _p	Not Populated				0	

9 PCB Layouts

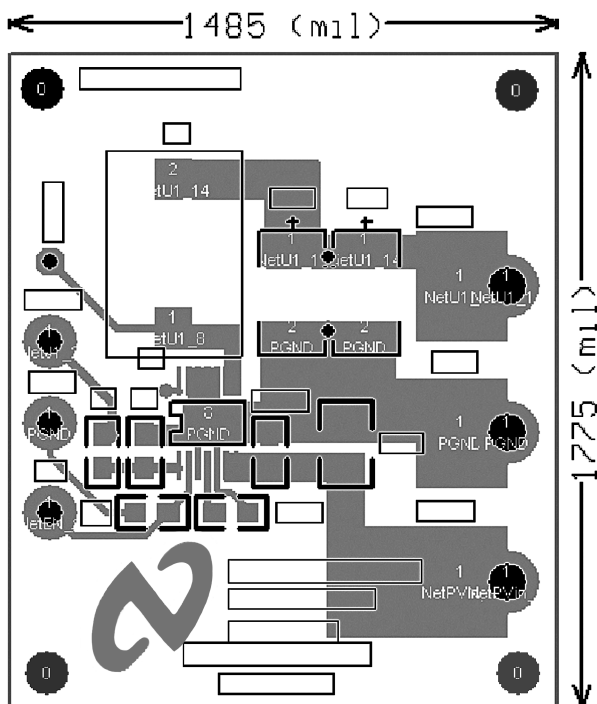


Figure 1. Top Layer

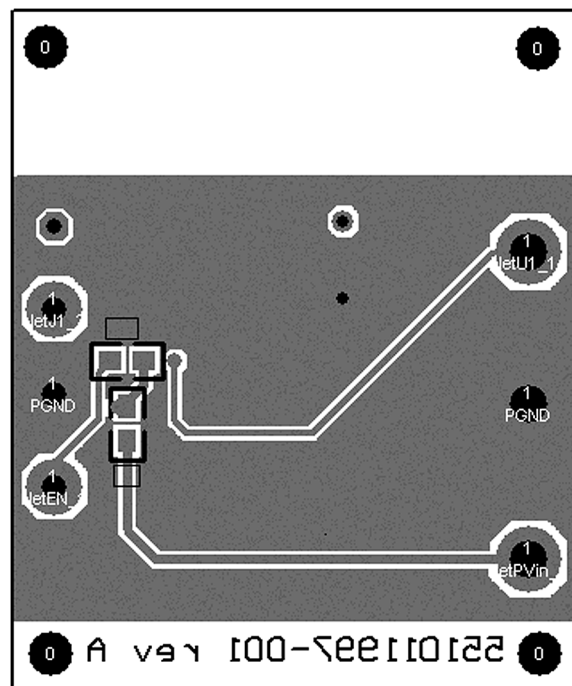


Figure 2. Bottom Layer

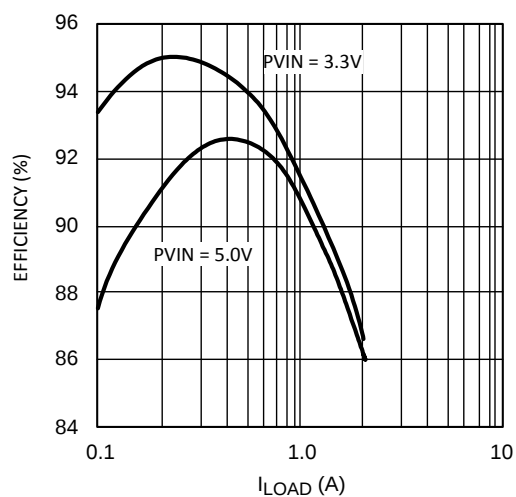


Figure 3. Typical Efficiency for 2.5V Output

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com