High-Frequency Amplifier Transistor (20V, 50mA, 1.5GHz)

2SC5661 / 2SC4725 / 2SC4082 / 2SC3837K

●Features

1) High transition frequency. (Typ. f_T = 1.5GHz)
2) Small rbb'·Cc and high gain. (Typ. 6ps)
3) Small NF.

●Packaging specifications and h_{FE}

Type	2SC5661	2SC4725	2SC4082	2SC3837K
Package	VMT3	EMT3	UMT3	SMT3
h_{FE}	NP	NP	NP	NP
Marking	AC*	AC*	1C*	AC*
Code	T2L	TL	T106	T146
Basic ordering unit (pieces)	8000	3000	3000	3000


* Denotes h_{FE}

● Absolute maximum ratings (Ta=25°C)

Parameter		Symbol	Limits	Unit
Collector-base voltage		V_{CBO}	30	V
Collector-emitter voltage		V_{CEO}	20	V
Emitter-base voltage		V_{EBO}	3	V
Collector current		I_C	50	mA
Collector power dissipation	2SC5661, 2SC4725	P_C	0.15	W
	2SC4082, 2SC3837K		0.2	
Junction temperature		Tj	150	°C
Storage temperature		Tstg	−55 to +150	°C

●Dimensions (Unit : mm)


2SC5661

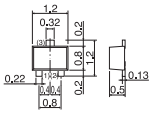

ROHM : VMT3

(1) Base
(2) Emitter
(3) Collector


2SC4725

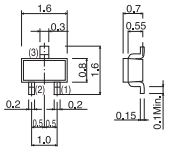

ROHM : EMT3
EIAJ : SC-75A

(1) Emitter
(2) Base
(3) Collector

2SC4082

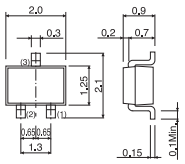


ROHM : UMT3
EIAJ : SC-70

(1) Emitter
(2) Base
(3) Collector

Each lead has same dimensions

2SC3837K

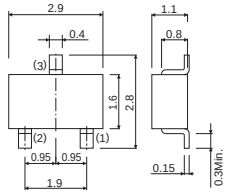

ROHM : SMT3
EIAJ : SC-59

(1) Emitter
(2) Base
(3) Collector

Each lead has same dimensions

●Electrical characteristics (Ta=25°C)

Parameter	Symbol	Min.	Typ.	Max.	Unit	Conditions
Collector-base breakdown voltage	BV_{CBO}	30	–	–	V	I_C = 10μA
Collector-emitter breakdown voltage	BV_{CEO}	20	–	–	V	I_C = 1mA
Emitter-base breakdown voltage	BV_{EBO}	3	–	–	V	I_E = 10μA
Collector cutoff current	I_{CBO}	–	–	0.5	μA	V_{CB} = 15V
Emitter cutoff current	I_{EBO}	–	–	0.5	μA	V_{EB} = 2V
Collector-emitter saturation voltage	$V_{CE(sat)}$	–	–	0.5	V	I_C/I_B = 20mA/4mA
DC current transfer ratio	h_{FE}	82	–	180	–	V_{CE}/I_C = 10V/10mA
Transition frequency	f_T	600	1500	–	MHz	V_{CE} = 10V , I_E = −10mA , f = 200MHz
Output capacitance	Cob	–	0.9	1.5	pF	V_{CB} = 10V , I_E = 0A , f = 1MHz
Collector-base time constant	rbb'·Cc	–	6	13	ps	V_{CB} = 10V , I_C = 10mA , f = 31.8MHz
Noise factor	NF	–	4.5	–	dB	V_{CE} = 12V , I_C = 2mA , f = 200MHz , Rg = 50Ω

This product might cause chip aging and breakdown under the large electrified environment.
Please consider to design ESD protection circuit.

© 2009 ROHM Co., Ltd. All rights reserved.

●Electrical characteristic curves

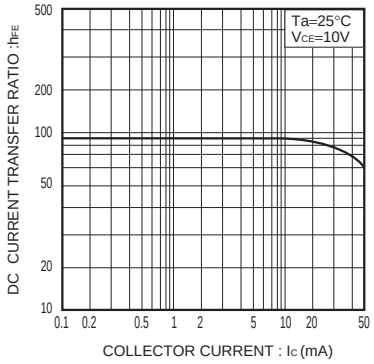


Fig.1 DC current gain vs. collector current

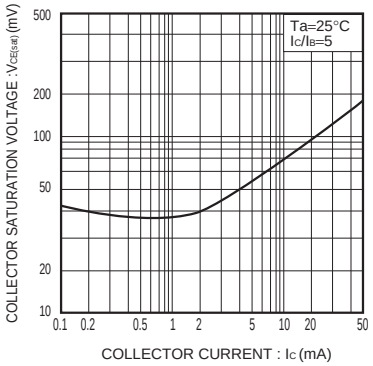


Fig.2 Collector-emitter saturation voltage vs. collector current

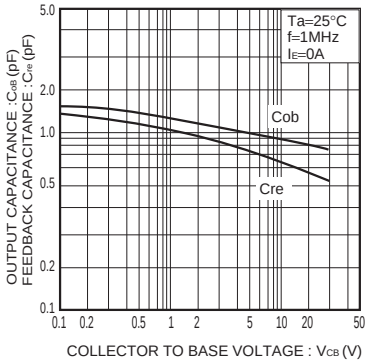


Fig.3 Capacitance vs. reverse bias voltage

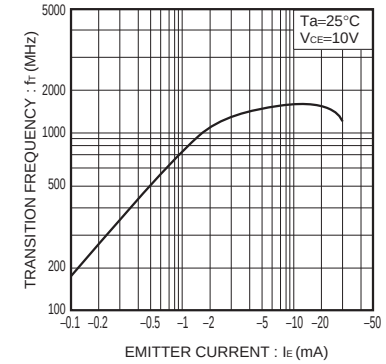


Fig.4 Gain bandwidth product vs. emitter current

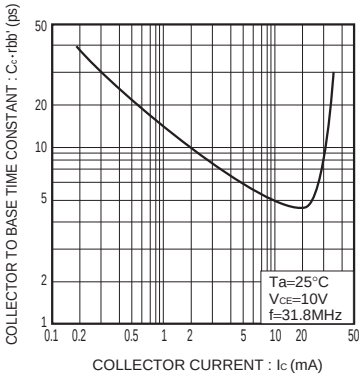


Fig.5 Collector to base time constance vs. collector current

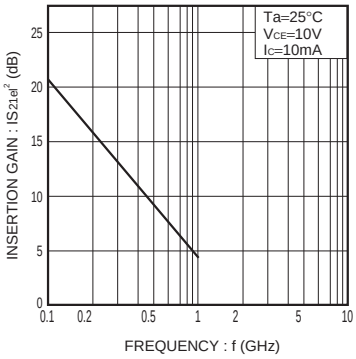


Fig.6 Insertion gain vs. frequency

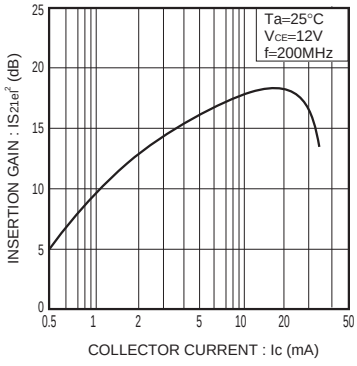


Fig.7 Insertion gain vs. collector current

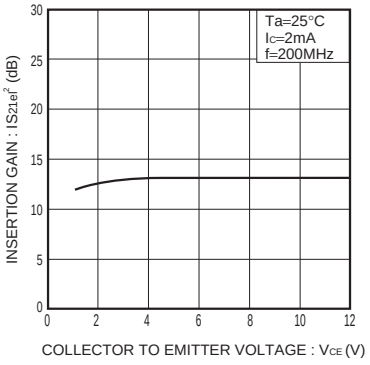


Fig.8 Insertion gain vs. collector voltage

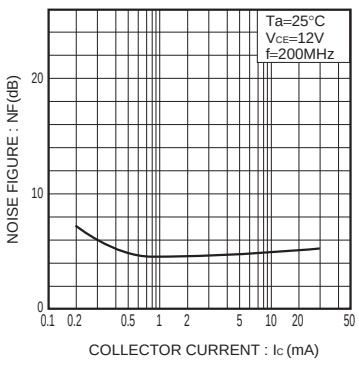


Fig.9 Noise factor vs. collector current

© 2009 ROHM Co., Ltd. All rights reserved.

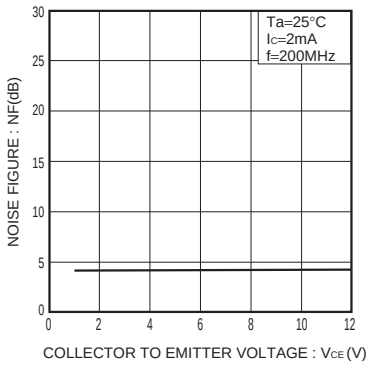


Fig.10 Noise factor vs. collector voltage

© 2009 ROHM Co., Ltd. All rights reserved.

Notes

No copying or reproduction of this document, in part or in whole, is permitted without the consent of ROHM Co.,Ltd.

The content specified herein is subject to change for improvement without notice.

The content specified herein is for the purpose of introducing ROHM's products (hereinafter "Products"). If you wish to use any such Product, please be sure to refer to the specifications, which can be obtained from ROHM upon request.

Examples of application circuits, circuit constants and any other information contained herein illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.

Great care was taken in ensuring the accuracy of the information specified in this document. However, should you incur any damage arising from any inaccuracy or misprint of such information, ROHM shall bear no responsibility for such damage.

The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM and other parties. ROHM shall bear no responsibility whatsoever for any dispute arising from the use of such technical information.

The Products specified in this document are intended to be used with general-use electronic equipment or devices (such as audio visual equipment, office-automation equipment, communication devices, electronic appliances and amusement devices).

The Products specified in this document are not designed to be radiation tolerant.

While ROHM always makes efforts to enhance the quality and reliability of its Products, a Product may fail or malfunction for a variety of reasons.

Please be sure to implement in your equipment using the Products safety measures to guard against the possibility of physical injury, fire or any other damage caused in the event of the failure of any Product, such as derating, redundancy, fire control and fail-safe designs. ROHM shall bear no responsibility whatsoever for your use of any Product outside of the prescribed scope or not in accordance with the instruction manual.

The Products are not designed or manufactured to be used with any equipment, device or system which requires an extremely high level of reliability the failure or malfunction of which may result in a direct threat to human life or create a risk of human injury (such as a medical instrument, transportation equipment, aerospace machinery, nuclear-reactor controller, fuel-controller or other safety device). ROHM shall bear no responsibility in any way for use of any of the Products for the above special purposes. If a Product is intended to be used for any such special purpose, please contact a ROHM sales representative before purchasing.

If you intend to export or ship overseas any Product or technology specified herein that may be controlled under the Foreign Exchange and the Foreign Trade Law, you will be required to obtain a license or permit under the Law.

ROHM SEMICONDUCTOR

Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

http://www.rohm.com/contact/

© 2009 ROHM Co., Ltd. All rights reserved.