

TI Over-Current Detection Products

Protecting from Over-Current in Multiple Applications



TEXAS INSTRUMENTS

Over-Current Products

Overview

TI- Over-Current Products

Current is one of the more common signals that is measured in electronic systems. What varies from system to system is how that current information is utilized once it is collected. Current information can be used in active feedback circuitry, system performance data logging as well as used in diagnostic and fault detection.

Many applications require that either indication or control of system performance be added in the event that an out-of-range condition could occur. This can range from ground faults and short-circuit events to heavier than expected loading conditions. Regardless of the source, systems often need protection circuitry added to ensure that potentially damaging conditions are not allowed to persist for extended periods of time.

The most common implementation for protecting a system from excessive out-of-range conditions is the addition of a fuse in the design. This is an extremely simple component that's use-case is obvious in that the device's sole purpose is to open in the event of an extended over-current condition.

While this approach to system protection is extremely simple and effective in protecting the system from gross, over-current events, there are a few draw-backs and trade-offs to this over-current protection approach.

A fuse protection scheme has a single event life-span requiring that once the component is blown, the board must be repaired to replace this device with a new one in order for the system to return to normal operation. Another characteristic of a fuse is that in order for a quick open to occur the current must significantly exceed by four to five times or more the current rating of the fuse in order to blow making the precise level the fuse opens difficult to predict.

The sole use of a fuse as a protection component also does not enable the ability to provide information on the actual operating conditions of the system. This is where other options for system

Table of Contents

2 Overview

Featured Products


3 Current Sense Amplifier plus Comparator
4 Single-Chip Over-Current Detection Solution
5 Footprint Requirements Comparison
6 Resources

protection can be employed with TI leading the charge in providing targeted solutions to meet customer needs. TI provides over-current detection solutions that can be optimized base on the key care-about of a particular application whether that be based on cost, solution size, measurement accuracy or alert response time.

Historically, an over-current detection solution has been created using a simple operational amplifier, external gain setting resistors and a low-cost comparator. The operational amplifier and external gain setting resistors are configured to create a difference amplifier configuration to amplify the voltage developed across the current sensing shunt resistor to create a single-ended output voltage that is routed to the comparator.

The threshold level of the comparator reference is set to equal to the output voltage level of the current sense amplifier corresponding to the current level needing to be monitored for.

There are several options for the circuitry used to create the comparator's threshold reference signal depending on the accuracy and stability required by the application. This reference signal can vary from a simple resistor divider network (lowest cost & least accurate) to a precision low-drift voltage reference (most expensive & highest accuracy). While this solution can be implemented using low-cost operational amplifiers, this will adversely affect the accuracy of the results or require expensive discrete external components to increase the performance.

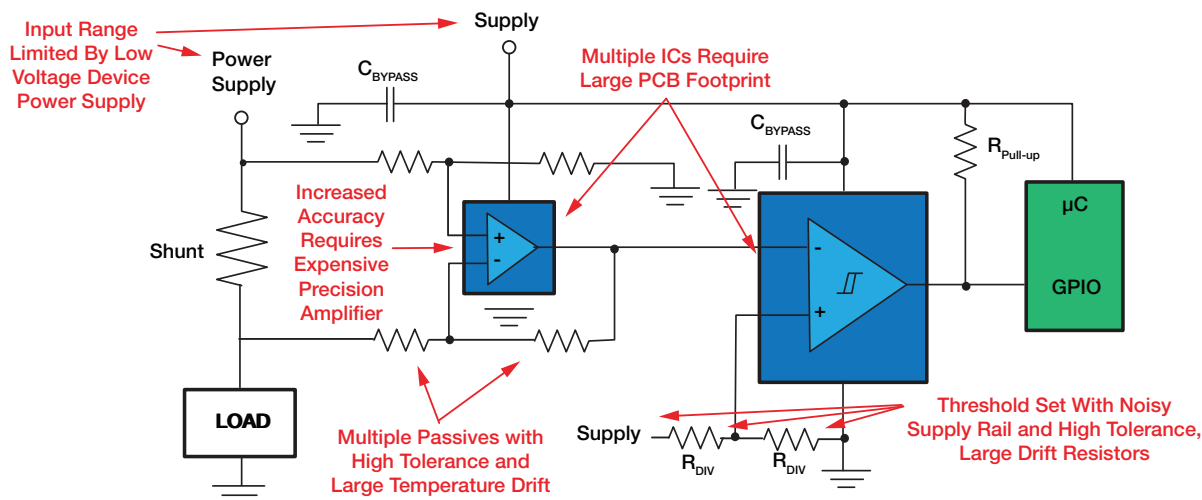

Discrete Current Detection – Op Amp plus Comparator Block Diagram

Featured Products

Current Sense Amplifier plus Comparator

Current Sense Amplifier plus Comparator

TI Part INA199 & LMV331

An over-current detection solution using a dedicated current-sense amplifier (CSA) paired with a comparator optimizes this protection function further.

The current-sense amplifier's integration of the operational amplifier and external gain setting resistors incorporate all of the discrete components in the measurement portion of this solution enabling both a more accurate measurement with a smaller board space requirement. The output of the current sense amplifier can be measured directly or routed to the comparator to form the detection portion of the over-current detection function.


The threshold level of the comparator reference is set to equal to the output voltage level of the current sense amplifier corresponding to the current level needing to be monitored for. There are several options for the circuitry used to create the comparator's threshold reference signal depending on the accuracy and stability required by the application. This reference signal can vary from a simple resistor divider network (lowest cost & least accurate) to a precision low-drift voltage reference (most expensive & highest accuracy).

Strengths

- Enables both over current detection as well as current monitoring
- Response time down to as low as 2 μ s

Weaknesses

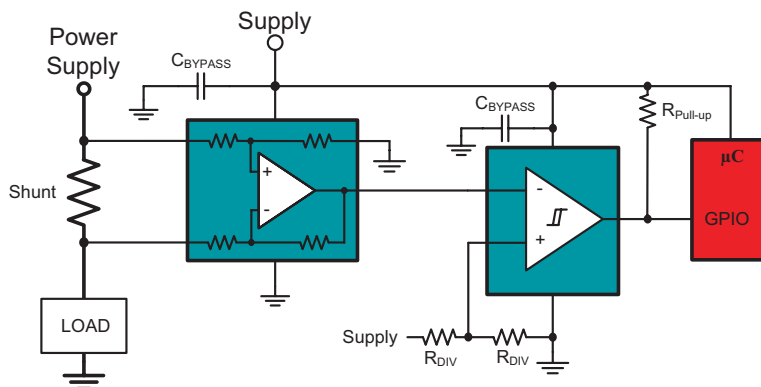- Multiple chips require large footprint / board space
- Requires precise external reference for precision threshold setting



Current Sense Amplifier plus Comparator Block Diagram

Get more information: <http://www.ti.com/product/ina199a1>

Featured Products

Single-Chip Over-Current Detection Solution

Single-Chip Over-Current Detection Solution

INA300

The INA300 is a dedicated current-sensing comparator that is optimized for detecting over-current conditions. This device integrates both the precision measurement circuitry as well as the comparison portion creating an all-in-one over-current detection solution.

The INA300 features an adjustable threshold range to detect an over-current event that is set using a single external limit-setting resistor. The output can be configured to operate in either a transparent mode where the output status follows the input state or in a latched mode where the alert output is cleared when the latch is cleared indicating that the over-current alert has been received.


The device response time setting is also selectable, enabling overcurrent alerts to be issued in as quickly as 10 μ s.

Strengths

- Small footprint saves greater than 50% compared to discrete operational amplifier solution
- Integrated precision reference sets threshold trip point via single external resistor.
- Response time adjustable from 10 μ s to 100 μ s

Weaknesses

- Does not report current value

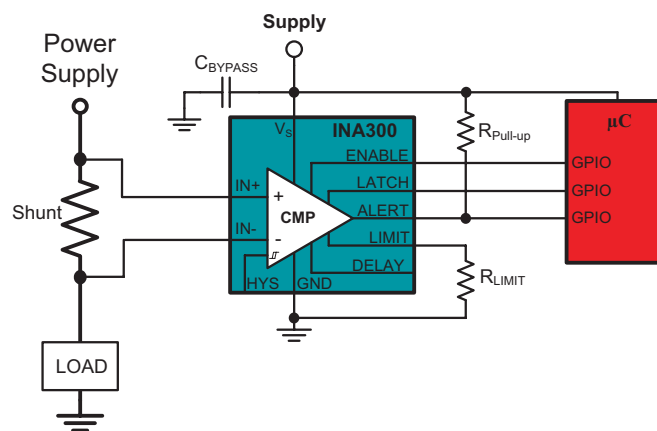

Single-Chip Over-Current Detection Solution Block Diagram



INA300 is in a tiny 2mm x 2mm QFN package minimizing footprint requirements.


Get more information: www.ti.com/product/INA300

Featured Products


Footprint Requirements Comparison

One of the most significant advantages of the INA300 implementation is the integration offered and the resulting footprint savings. The different alternatives discussed for over-current detection have very different footprint requirements. The size of the implementation will vary depending on the actual components chosen. The discussion below is based on very typical components for each of the solutions. Many typical op amps and comparators utilize the SOT23 package. The historical implementation in addition to being complex and difficult to achieve high precision with requires two such packages, as well as 9 discrete resistors, for which we will use the 0603 size. This leads to a total component footprint (not counting the routing) of just


under 47 mm². The INA199 plus comparator implementation offers savings of around 37% over the op amp plus comparator. The INA199 is offered in a SC-70 package, which requires about half the area of the op amp. the comparator remains the same size and this implantation only requires five discrete resistors, or again an almost 50% savings. The footprint for this implementation totals just over 29 mm².The INA300 is in a very small SON package and eliminates the need for the additional comparator as well as reducing the number of external resistors. This totals a solution footprint of just over 14 mm². This is a 70% savings over the op amp plus comparator solution and a 36% savings over the INA199 plus comparator.

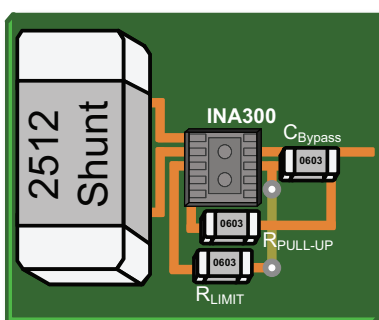

INA300 footprint is approx. 14mm²

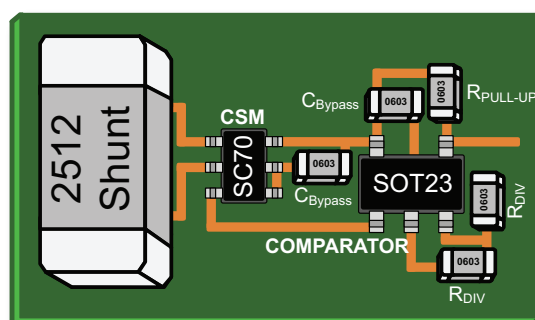

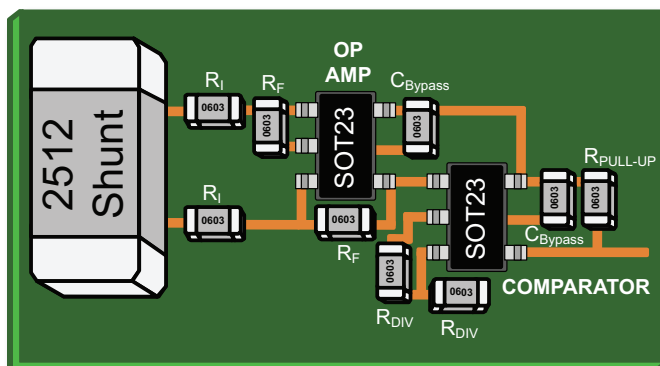INA199 + Comp. footprint is approx. 29mm²



Op-Amp + Comp. footprint is approx. 47mm²

Total Component Footprint Required not including trace routing & RSHUNT

Device	Op-Amp + Comparator	INA199 + Comparator	INA300
Integrated Circuits	16.2 mm ²	12.3 mm ²	4.0 mm ²
Discrete Components	30.7 mm ²	17.0 mm ²	10.2 mm ²
# of discretes	9	5	3
Area	46.9 mm ²	29.4 mm ²	14.2 mm ²
% Savings	n/a	37% smaller than op-amp implementation	70% smaller than op-amp implementation 52% smaller than INA199 implementation

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas Phone +1(512) 434-1560

Brazil Phone 0800-891-2616

Mexico Phone 0800-670-7544

Fax +1(972) 927-6377
Internet/Email support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone

European Free Call 00800-ASK-TEXAS
(00800 275 83927)
International +49 (0) 8161 80 2121
Russian Support +7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +(49) (0) 8161 80 2045
Internet www.ti.com/asktexas
Direct Email asktexas@ti.com

Japan

Phone Domestic (toll-free number) 0120-92-3326
Fax International +81-3-3344-5317
Domestic 0120-81-0036
Internet/Email International support.ti.com/sc/pic/japan.htm
Domestic www.tij.co.jp/pic

Asia

Phone

Toll-Free Number

Note: Toll-free numbers may not support mobile and IP phones.

Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010

International +86-21-23073444

Fax +86-21-23073686

Email tiasia@ti.com or ti-china@ti.com

Internet support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A012014

The platform bar and E2E are trademarks of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com