

AN-1975 LMP8640/LMP8645 Evaluation Board

1 Introduction

This evaluation board shows a bidirectional high-side current sense made using LMP8640 (LMP8645) and optional differential amplifier in order to have a single output.

2 Connectors

2.1 Power Supply

There are two banana plugs labeled GND and V_{CC} to power the evaluation board. Moreover, a banana plug labeled VCC_Amp is used to power an optional operational amplifier that makes the difference between the outputs of the two LMP8640 (LMP8645).

2.2 Signal Connectors

There are five connectors for signals.

Table 1. Input signals

IN	It connects the non inverting input of U1 and inverting input of U2.
LOAD	It connects the non inverting input of U2 and inverting input of U1.

The device U1 is able to sense the current when it flows in the shunt resistor from the LOAD pin to the IN pin. The device U2 is able to sense the current when it flows in the shunt resistor from IN pin to LOAD pin.

Table 2. Output signals

OUT+	Output of device U2, the voltage at this pin is related to the current that flows from the IN pin to the LOAD pin.
OUT-	Output of device U1, the voltage at this pin is related to the current that flows from the LOAD pin to the IN pin.
OUT	Optional Output of the difference amplifier that makes the difference between OUT+ and OUT-

3 Hardware Setup

3.1 Power Supply Setup

- High side current sense LMP8640 (LMP8645)
 - Connect a supply voltage in the range between 2.7 V and 12 V to the V_{CC} and GND turrets.
- Optional difference amplifier
 - Connect a supply according to the specs of the amplifier to the VCC_Amp and GND turrets.

3.2 Source and Load Setup

First case: Current flows from IN to LOAD plugs.

A voltage supply can be connected between the IN and the GND banana plugs, while a load is connected between the LOAD and the GND banana plugs. The voltage applied at the IN pin should not exceed the maximum common mode voltage allowed by the LMP8640/HV (LMP8645/HV). The maximum allowed common mode voltages are listed in [Table 3](#).

Second case: Current flows from LOAD to IN plugs.

In this case, the voltage supply is connected between the LOAD and the GND banana plugs, while the load is connected between the IN and GND banana plugs. The voltage applied at LOAD pin should not exceed the maximum common mode voltage allowed by the LMP8640/HV (LMP8645/HV). The maximum allowed common mode voltages are listed in [Table 3](#).

Table 3. Max Common Mode Voltage

DEVICE	MAX VCM
LMP8640	42V
LMP8645	42V
LMP8640HV	76V
LMP8645HV	76V

According to the shunt resistor (Rsns), to the gain of LMP8640 (LMP8645) and to the supply voltage different ranges of currents can be sensed with this evaluation board.

3.3 Components

On the evaluation board, there are already the circuit and the footprint of a standard dual op amp (U3) to implement a differential op amp (U3.B) with reference (U3.A) in order to provide a single ended output of the bidirectional current.

Table 4. Optional Differential Circuit

U3	Standard Dual Op Amp 8 pin. U3.1 OUT A U3.2 -IN A U3.3 +IN A U3.4 V ⁻ U3.5 +IN B U3.6 -IN B U3.7 OUT B U3.8 V ⁺
R1, R2, R3, R4	resistors that implement the differential circuit according to Equation 1 :
$OUT = -\frac{R4}{R1} * OUT^- + \left(1 + \frac{R4}{R1}\right) * \left(\frac{R2}{R2 + R3} * Vref + \frac{R3}{R2 + R3} * OUT^+\right)$	
(1)	
R5, R6, C5	components for voltage reference and its filter. The voltage reference is calculating according to Equation 2 :
$Vref = \frac{R5}{R5 + R6} * VCC_Amp$	
(2)	

4 Using the Evaluation Board

4.1 Input and Output Signals

The evaluation board allows you to measure a bidirectional current, so the IN and LOAD banana connectors can act either as the Source or LOAD pin. If the current flows from the IN pin to the LOAD pin, a simple way to test the performance of the LMP8640 (LMP8645) is shown in [Figure 1](#).

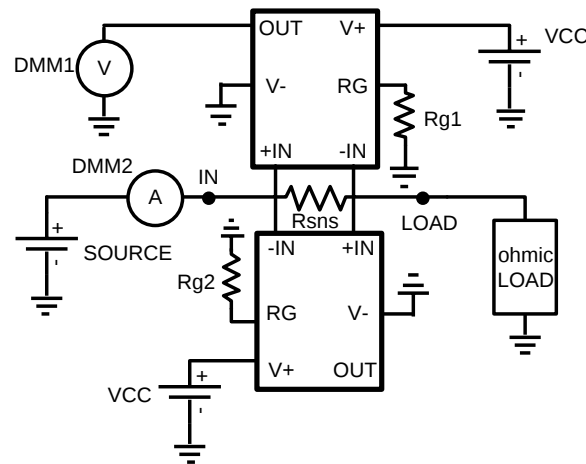


Figure 1. LMP8640 (LMP8645) Measurement Setup

The DMM1 is configured as a voltmeter, which measures the output of the LMP8640 (LMP8645), while the DMM2 is configured as an Ammeter, which measures the current that flows in the LOAD. The source is a voltage supply that makes sure to set a voltage in the range of -2 V to +46 V for LMP8640 (LMP8645) or -2 V to +76 V for LMP8640HV (LMP8645HV).

4.2 Gain Selection of LMP8645

The evaluation board is provided with a shunt resistor R_{sns} (10 mΩ, @ 1%, 1W), while two gain resistors R_{g1} and R_{g2} (10 kΩ, @1%) ensure a gain of 2 V/V for each current sense. The Gain is evaluated according to formula in [Equation 3](#):

$$\text{Gain} = \frac{R_g}{5k\Omega} \text{ V/V} \quad (3)$$

The gain resistor must be chosen such that the max output voltage does not exceed the LMP8645 max output voltage rating for a given common mode voltage (further details in the Datasheet).

4.3 Single Output

In the applications where a single measurement of a bidirectional current sense is needed is possible to populate the evaluation board with two amplifiers and some resistors (see [Section 3.3](#)).

For instance, in the following configuration:

$$R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega,$$

$$R_5 = R_6 = 10 \text{ k}\Omega$$

$$\text{OUT} = V_{\text{REF}} + (\text{OUT}^+ - \text{OUT}^-)$$

$$V_{\text{REF}} = 0.5 \cdot V_{\text{CC_Amp}}.$$

The V_{REF} level represents the zero level; the voltages greater than V_{REF} are related to a current that flows from IN pin to the LOAD pin while the voltages less than V_{REF} are related to a current that flows from the LOAD pin to the IN pin. To ensure good results in the measurements, the resistors R4 and R3 and the resistors R1 and R2 need to be well matched.

5 Bill Of Materials (BOM)

Table 5. Bill Of Materials ⁽¹⁾, ⁽²⁾

Designator	Component	Value	Tolerance	Package Type
C1, C3	Capacitor	0.01 μ F	5%	0603
C2, C6*	Capacitor	1 μ F	10%	3216–18
C4	Capacitor	0.1 μ F	10%	0805
C5*, C7	Capacitor	0.1 μ F	10%	0603
C_Filt1*, C_Filt2*	Capacitor			0805
CG1*, CG2*	Capacitor			0805
R1*, R2*, R3*, R4*, R5*, R6*	Resistor	min 10 k Ω	1%	0603
RG1**, RG2**	Resistor	10.0 k Ω	1%	0603
Rsns**	Resistor	0.01 Ω	1%, 1W	2010
Rsns	Resistor	0.01 Ω	0.1%, 1W	2512
R_Filt_1, R_Filt2	Resistor		5%	0805
U3*	Dual Op Amp			SOT-8

⁽¹⁾ Components Marked With (*) are not soldered on the board.

⁽²⁾ Components marked with (**) are soldered only on LMP8645 board.

Appendix A Schematic

This schematic shows the evaluation board with a LMP8645 mounted on the PCB. The only difference for the version of the PCB stuffed with LMP8640 will be the gain resistors RG1, RG2. The LMP8640 is a current sense with fixed gain, so it doesn't require any external gain resistor.

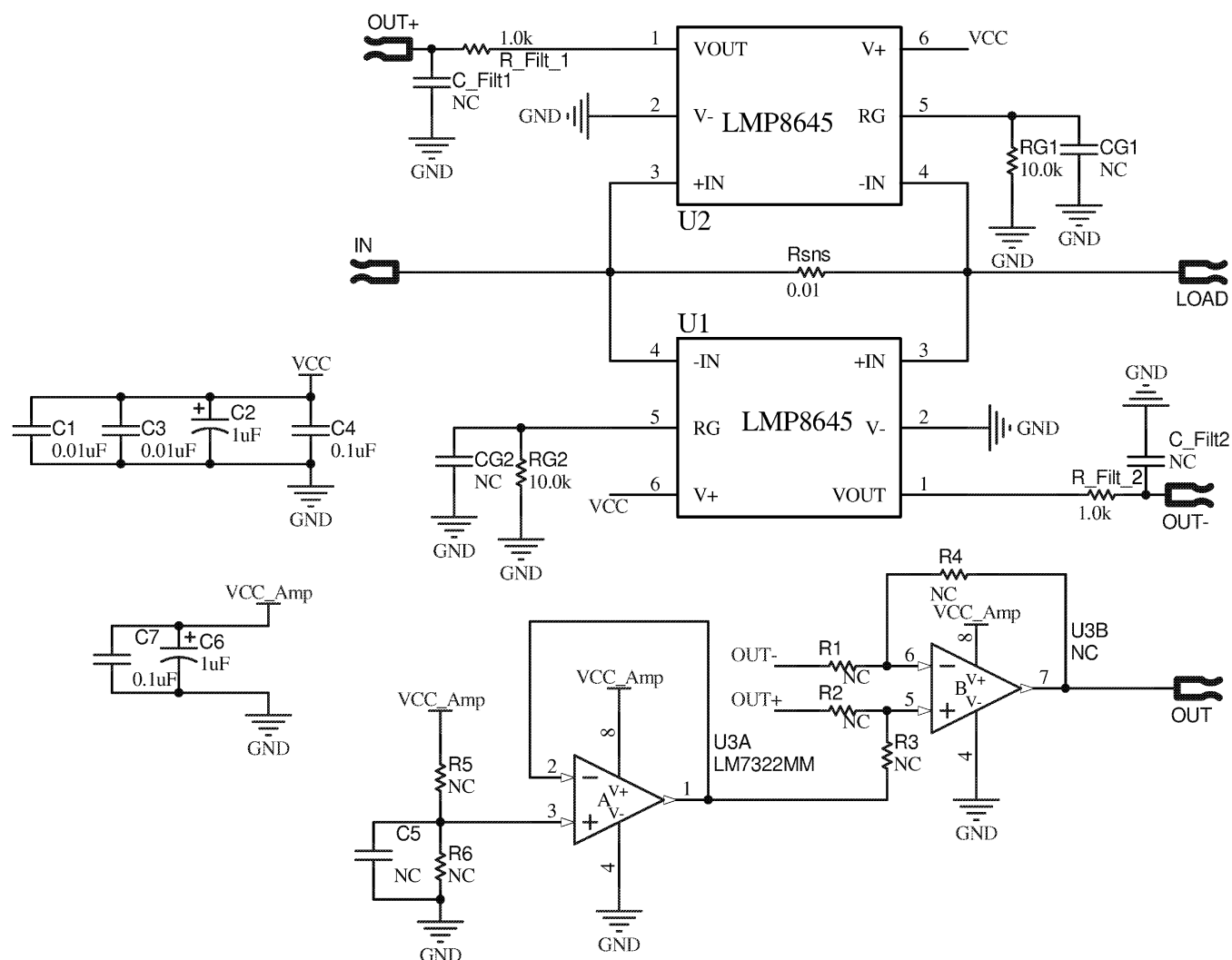


Figure 2. Schematic Diagram

Appendix B Layout


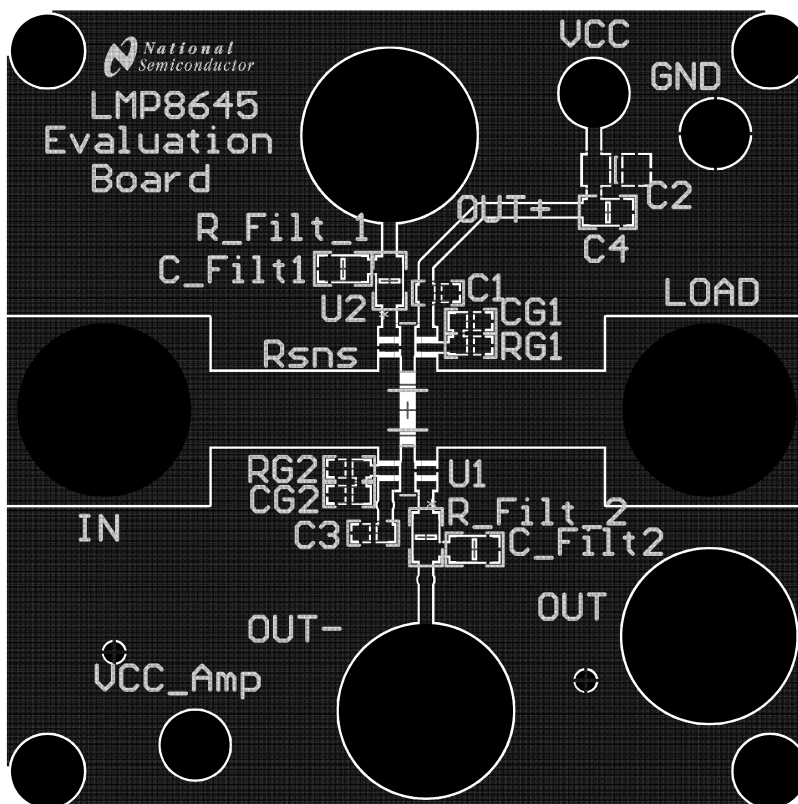


Figure 3. Top Layer

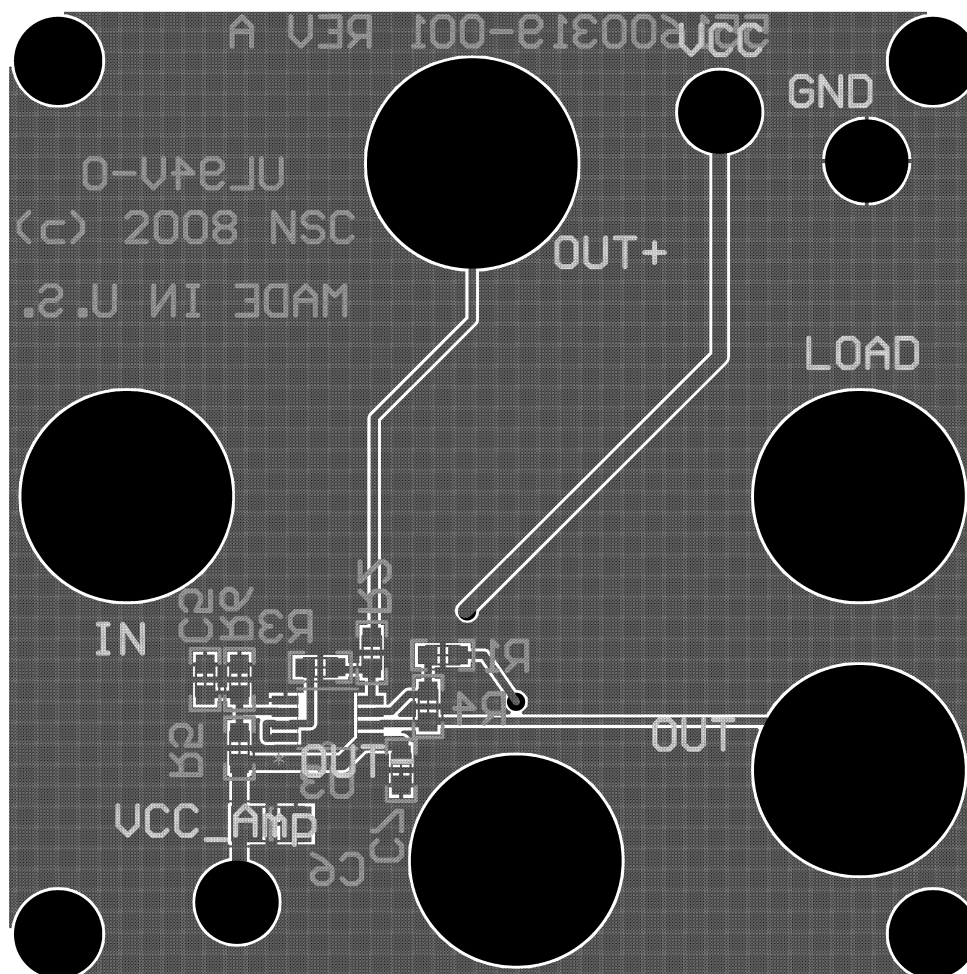

**Figure 4. Bottom Layer
PCB Layout**

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com